EE2S11 Signals and Systems Chapter 12.6 Discrete-time filter structures (realizations)

Alle-Jan van der Veen

19 January 2024



Contents

- FIR filters (direct form tapped delay line)
- IIR filters (direct form 1, 2)
- Cascade and parallel structure
- Transposition



Minimal and canonical realizations

A structure which implements an N-th order transfer function is called minimal if it uses exactly N delay elements.

A canonical realization is a "textbook structure", the typical structure for a certain class of transfer functions (e.g. FIR, IIR, allpass, \cdots). It is usually minimal, with also a minimal number of operations (multiplications with coefficients).

Generally, each filter coefficient should appear only *once* in the realization. This is important for zero-phase FIR filters,


$$H(z) = b_0 + b_1 z^{-1} + b_1 z^{-2} + b_0 z^{-3}$$

and allpass filters,

$$H(z) = \frac{a_2 + a_1 z^{-1} + z^{-2}}{1 + a_1 z^{-1} + a_2 z^{-2}}$$




Examples

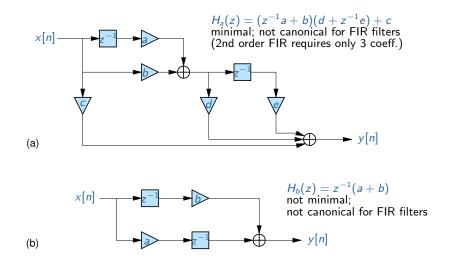



Transversal filter

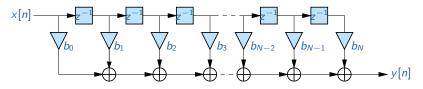An FIR filter can be realized using a *transversal filter*:



 $y[n] = b_0 x[n] + b_1 x[n-1] + \dots + b_N x[n-N]$

- Minimal and canonical for the class of N-th order FIR filters: N delays; N + 1 multipliers for N + 1 coefficients
- The coefficients $h[n] = b_n$ are directly used in the realization
- The transfer function is

$$H(z) = \frac{Y(z)}{X(z)} = b_0 + b_1 z^{-1} + \dots + b_N z^{-N}$$




Recursive implementation of an FIR filter

An FIR filter can sometimes also be implemented recursively: e.g.,

$$y[n] = \frac{1}{M+1} \sum_{k=0}^{M} x[n-k] = \frac{1}{M+1} (x[n] + x[n-1] + \dots + x[n-M])$$

can be written as
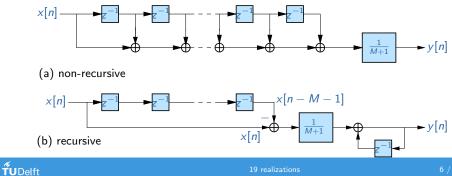
$$y[n] = y[n-1] + \frac{1}{M+1} (x[n] - x[n-M-1])$$




Recursive filter: direct form no. 1

ŤUDelft

Realization for a general rational filter (IIR, $a_0 = 1$):

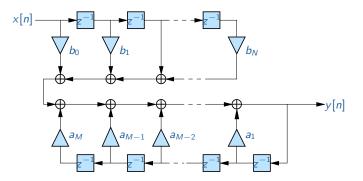
$$H(z) = \frac{b_0 + b_1 z^{-1} + \dots + b_N z^{-N}}{1 - a_1 z^{-1} - \dots - a_M z^{-M}} \iff y[n] = b_0 x[n] + \dots + b_N x[n - N] + a_1 y[n - 1] + \dots + a_M y[n - M]$$



This is not a minimal structure: M + N delays instead of $\max(M, N)$.

Recursive filter: direct form no. 2

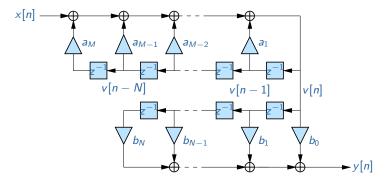Use the commutative property of the convolution: $h_1 * h_2 = h_2 * h_1$. We may reverse the order of both partial systems.




It is seen that the delay lines can be merged (they transport the same signal v[n])

ŤUDelft

Recursive filter: direct form no. 2 (cont'd)

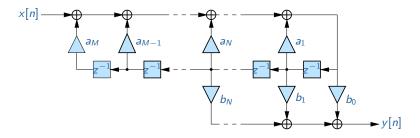
The resulting filter (minimal and canonical):



- Also in this realization the filter coefficients are directly related to the parameters in the difference equation.
- This realization is very sensitive to small disturbances (quantization) of the coefficients: the poles/zeros can move a lot. [See EE2S31]




Cascade structure

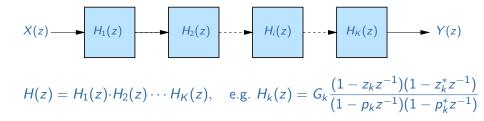

- Usually second order sections: less sensitive.
 Second order sections are needed for a canonical realization of transfer functions with *real-valued* coefficients.
- Used if the $H_k(z)$ all have the same passband (otherwise, large gains are needed).



Parallel structure

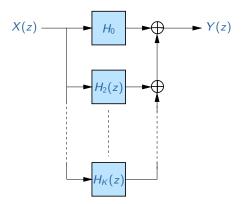

 $H(z) = H_1(z) + H_2(z) + \dots + H_K(z)$ e.g. $H_k(z) = \frac{A_k}{1 - p_k z^{-1}} + \frac{A_k^*}{1 - p_k^* z^{-1}}$ (2nd order section for complex conj. poles)


Less control over the location of zeros.



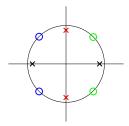Example

$$H(z) = G \frac{(1 - e^{j\pi/4}z^{-1})(1 - e^{-j\pi/4}z^{-1})(1 - e^{j3\pi/4}z^{-1})(1 - e^{-j3\pi/4}z^{-1})}{(1 - 0.9z^{-1})(1 + 0.9z^{-1})(1 - 0.9jz^{-1})(1 + 0.9jz^{-1})}$$

There are several possibilities to split this into 2nd order sections with real-valued coefficients. For a cascade, we can also choose which pair of zeros we combine with which pair of poles. With infinite accuracy (no quantization) this does not make a difference.






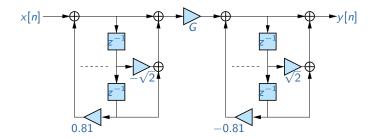Example (cont'd)

$$H_1(z) = \frac{(1 - e^{j\pi/4}z^{-1})(1 - e^{-j\pi/4}z^{-1})}{(1 - 0.9z^{-1})(1 + 0.9z^{-1})} = \frac{1 - \sqrt{2}z^{-1} + z^{-2}}{1 - 0.81z^{-2}}$$

$$H_2(z) = \frac{(1 - e^{j3\pi/4}z^{-1})(1 - e^{-3j\pi/4}z^{-1})}{(1 - 0.9jz^{-1})(1 + 0.9jz^{-1})} = \frac{1 + \sqrt{2}z^{-1} + z^{-2}}{1 + 0.81z^{-2}}$$





19 realizations


Transposition

Proposition: Given a realization (graph/network with nodes and edges). Make the following changes:

- **1** Reverse the direction of every edge (adders \leftrightarrow nodes)
- 2 Reverse input and output


The transfer function is not changed (cf. Tellegen's theorem).

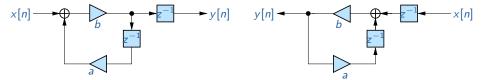Example:
$$H(z) = \frac{bz^{-1}}{1 - abz^{-1}}$$





Application to direct form no. 2

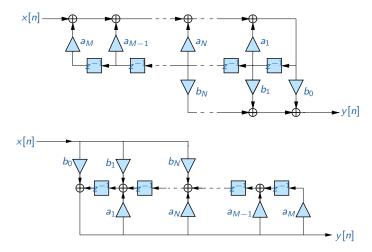

Advantage: a much shorter critical path (all adders can operate in parallel).

TUDelft

19 realizations