


COMBINATIONAL LOGIC

Combinational Logic - Outline

- Conventional Static CMOS basic principles
- Complementary static CMOS
 - Complex Logic Gates
 - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic
- Dynamic CMOS gates → only illustration

Complementary Static CMOS Basic Principles

Combinational vs. Sequential Logic

 

(a) Combinational

(b) Sequential



§ 6.2

Output = $f(\text{In})$

Output = $f(\text{In, History})$

Reminder

DeMorgan Transformations


$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a **switch** controlled by its gate signal

 
NMOS switch **closes** when switch control input is **high**




PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is **low**

$Y = X$ if ...

 


$Y = X$ if $\bar{A}$ and $\bar{B}$

 

$Y = X$ if $\bar{A}$ or $\bar{B}$

2-Input Nand

 

$Y = 1$ if $\bar{A}$ OR $\bar{B}$
 $Y = 1$ if $\overline{A \text{ AND } B}$

} DeMorgan


$Y = \overline{A \text{ AND } B}$

$Y = 0$ if $A \text{ AND } B$

B	A	Y
0	0	1
0	1	1
1	0	1
1	1	0

2-Input Nand

$$Y = \overline{A \text{ AND } B}$$

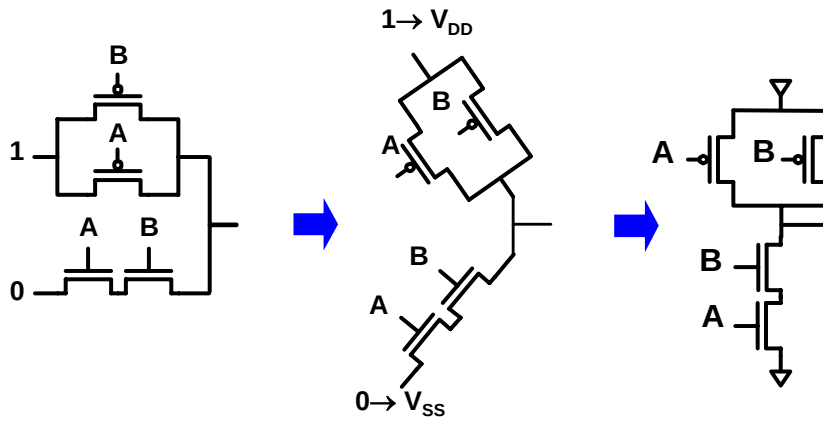


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

9

2-input Nand/Nor


 


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009


10

NMOS vs. PMOS, pull-down vs. pull-up

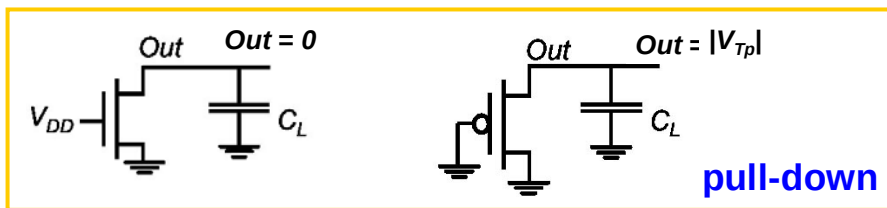 

- PMOS is better pull-up
- NMOS is better pull-down

Bad Idea

 

Exercise: Determine logic function

Determine V_{out}
for $V_{in} = V_{DD}$ and $V_{in} = V_{SS}$

Why is this a bad circuit?

CMOS Gate is Inverting

Assume full-swing inputs (high = V_{DD} , low = V_{SS})

- Highest output voltage of NMOS is

$$V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$$

- An 1 on NMOS gate can produce a strong 0 at the drain, but not a strong 1

- Lowest output voltage of PMOS is

$$V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$$

(with $V_{GS}, V_{Tp} < 0$ for PMOS)

- An 0 on PMOS gate can produce a strong 1 at the drain, but not a strong 0

- Need NMOS for pull-down, PMOS for pull-up

A 1 at input can pull-down, 0 at input can pull-up


Inverting behavior

For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates

Complementary static CMOS

- Complex Logic Gates
- VTC, Delay and Sizing


Complementary Static CMOS

 

- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**

Mutual Exclusive PDN and PUN

$$\text{Out} = (AB + C)'$$

 

			P D N	P U N	Out
C	B	A			
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

PDN Off
PUN On

PUN Off
PDN On

For all **Complementary Static CMOS Gates**, either the PUN or the PDN is conducting, but never both.

Complementary Static CMOS (2)

- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN
series $\Leftrightarrow$ parallel
nmos $\Leftrightarrow$ pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need 2N transistors for N-input gate

Implementation of Combinational Logic

- How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?


■ Example: $Y = \overline{(A + BC)}D$

- Remember: only inverting gates available



Implementation of Combinational Logic

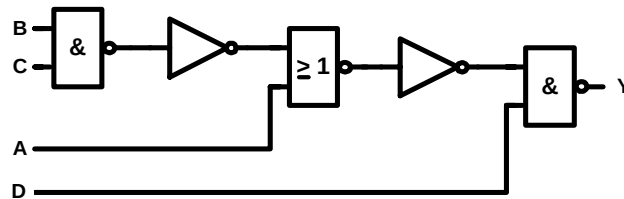- Example: $Y = \overline{(A + BC)D}$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path $\Rightarrow$ DELAY




transistors logic depth

- Q: Can this be improved?

Improved Gate Level Implementation

 
- Using DeMorgan $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



- Q: Can this be further improved?

Complex CMOS Logic Gates

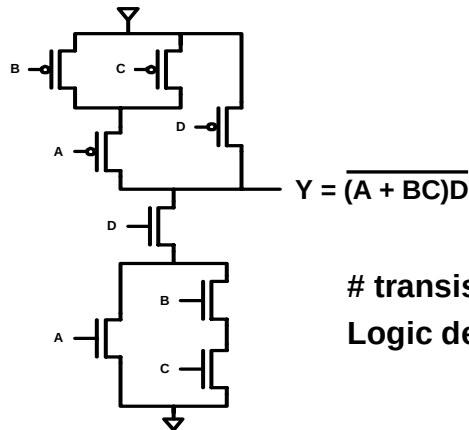- Restriction to basic NAND, NOR etc. **not necessary**
- Easy to synthesize **complex gates**



transistors: 8
Logic depth: 1


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

21

How to Synthesize Complex Gates

$$Y = (A + BC)D$$

 

- Using tree representation of Boolean function
- **Operator** with branches for **operands**
- As a **series-parallel** network

	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009


22

Complex Gate Synthesis Example

$$\bar{Y} = (A + (BC))D$$

 

	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

 

Recipe



- Write $Y = f(\text{inputs})$
- Decompose f in tree form
- Realize tree branches according to table at bottom-left
- Use inverted inputs if necessary

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

23

And-Or-Invert Gate

 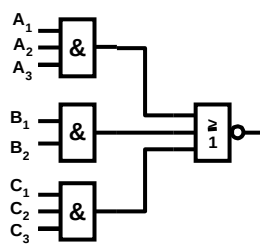

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

24

And-Or-Invert Example


■ From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$

$\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

 


$\bar{A}, \bar{B}$ to be created with extra inverters (or by restructuring previous circuits)

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009


25

And-Or-Invert Improvement

 

$$Y = \overline{\bar{A}BC + A\bar{B}C}$$

12 transistors

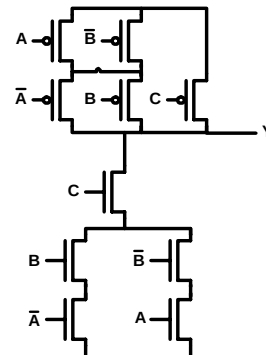

$$Y = \overline{(\bar{A}B + A\bar{B})C}$$

10 transistors


2-level logic minimization: boolean algebra technique

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

26

CMOS Complex Gate Sizing

 

- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability (timing) depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

27

CMOS Complex Gate Sizing


- Assume all transistors will have minimum length L
- Determine W_n for PDN transistor of inverter that would give the desired 'drive strength'
- For each transistor in PDN of complex gate do the following:
 - Determine the length l of the longest PDN chain in which it participates
 - Set $W = l W_n$
- Repeat this procedure for PUN, using W_p for PUN transistor of inverter.

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

28


Gate Sizing

 

- W/L ratios
- what are the W/L of 2-input NAND for same drive strength?

0-th order calculation


Exercise

 

Exercise:

- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, **assume $P_{U/PD} = 3$**
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same $P_{U/PD}$)
- Compare sum of gate areas in (a) and (b). Note: area $\sim$ width

Avoid Large Fan-In

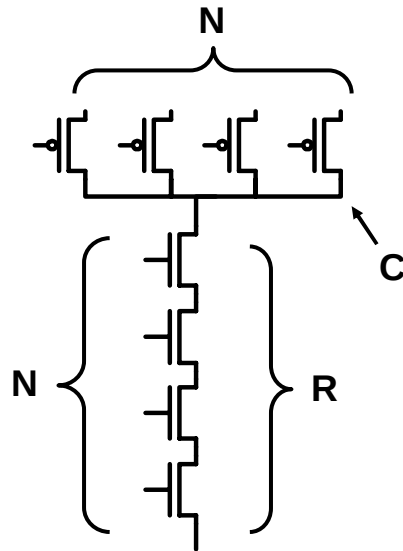

C linear in N


R linear in N

Delay $\propto$ RC **quadratic** in N

Empirical

Delay = $a_1 FI + a_2 FI^2 + a_3 FO$


Data-Dependent Timing

 

$$t_{PHL} = 0.69R_N C_L$$

$$t_{PLH} = 0.69R_P C_L$$

 You should be able to identify the transistor paths that charge or discharge C_L , and calculate resulting RC delay model, including effects of wires and fan-out



$$t_{PHL} = 0.69(R_N \times 2)C_L$$

$$t_{PLH} = 0.69R_P C_L$$



$$t_{PLH} = 0.69(R_P/2)C_L$$

Series connection

One input goes low

Two inputs go low, **parallel** connection

Data-dependent VTC: 2nd order effects

  



- Charge at 'int'
- Body effect in M_2
- Short-circuit currents

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

33

Data-dependent Timing

  

Input Data Pattern	Delay (pS)
$A = B = 0 \rightarrow 1$	69
$A = 1, B = 0 \rightarrow 1$	62
$A = 0 \rightarrow 1, B = 1$	50
$A = B = 1 \rightarrow 0$	35
$A = 1, B = 1 \rightarrow 0$	76
$A = 1 \rightarrow 0, B = 1$	57

$A=1, B=\downarrow$: need to charge *int*
 $A=\downarrow, B=1$: *int* does not need to be charged
 $A=\downarrow, B=\downarrow$: twice the pull-up strength

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

34



Remember: Inverter Delay


$$t_p = \frac{R_{ref}}{S} \left(C_{ref} S + f \frac{C_{ref} S}{\gamma} \right) = t_{p0} \left(1 + \frac{f}{\gamma} \right) \quad \text{with } t_{p0} = R_{ref} C_{ref}$$

$$d = 1 + f/\gamma$$

R_{ref}	Equivalent output resistance of min size inverter
C_{ref}	Drain (and Miller) cap of min size inverter
S	Size of inverter (relative to min inverter)
f	electrical effort – ratio between C_{load} and C_{in} (number of identical copies as load)
γ	ratio of drain cap to gate cap
t_{p0}	intrinsic delay - delay of unloaded inverter $t_{p0} \approx 20$ ps for a 250 nm process, $t_{p0} \approx 5$ ps for a 45 nm process
d	normalized delay = t_p/t_{p0}

$$d_{inv} = 1 + f/\gamma$$

  

 

Logical Effort Methodology

Inverter delay: $d_{inv} = 1 + f/\gamma$

Gate delay: $d_{gate} = p + gf/\gamma$


Logical Effort Methodology Definitions:

- p** parasitic delay
 - ratio of intrinsic delay compared to inverter
 - ratio of output cap for same drive strength
- g** logical effort
 - how much more load the gate creates
 - ratio of input cap for same drive strength
- h** gate effort, $h = gf$

[Logical Effort – Designing Fast CMOS Circuits, Sutherland, Sproul, Harris]

Beware: most texts, incl. Sutherland, interchange f and h

Intrinsic, Parasitic Delay

 


p parasitic delay - ratio of intrinsic delay compared to inverter

p is ratio of output capacitances if gate is sized for identical drive strength

p_{nand} is $(2+2+2)/(2+1) = 2$

$$d_{gate} = p + gf/\gamma$$

Logical Effort

 


g logical effort – ratio of input cap (per pin) if gate is sized for identical drive strength

g_{nand} is $(2+2)/(2+1) = 4/3$


$$d_{gate} = p + gf/\gamma$$

Logical Effort

 

p ratio of intrinsic delay compared to inverter
 g logical effort – ratio of inp. cap for same strength
 p, g independent of sizing, only topology of gate

Delay vs Fan-Out

 

Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + g_i \cdot f_i)$$

Normalized w.r.t. unit delay,
assume $\gamma = 1$

Stage effort: $h_i = g_i f_i$

Path electrical effort: $F = f_1 f_2 \dots f_N = C_{out}/C_{in}$

Path logical effort: $G = g_1 g_2 \dots g_N$

Path effort: $H = GF$

Path delay $D = \sum d_i = \sum p_i + \sum h_i$

Optimum Effort per Stage

When each stage bears the same effort:

$$h^N = H$$

$$h = \sqrt[N]{H}$$

Stage efforts: $g_1 f_1 = g_2 f_2 = \dots = g_N f_N = h$

Effective fanout of each stage: $f_i = h/g_i$


larger fanout for simpler stages

Minimum path delay

$$\hat{D} = \sum (g_i f_i + p_i) = NH^{1/N} + P$$

Example: Optimize Path

a, b, c: gate sizes t.b.d.

 

Effective fanout, $F = 5$

$$G = \prod g_i = 25/9$$

$$H = GF = 125/9 = 13.9$$

$$h = H^{1/4} = 1.93$$

$$g_1 f_1 = h \Rightarrow 1 \cdot a = h \Rightarrow a = 1.93$$

$$g_2 f_2 = h \Rightarrow (5/3 b)/1.93 = h \Rightarrow b = 2.23$$


$$g_3 f_3 = h \Rightarrow (5/3 c)/2.23 = h \Rightarrow c = 2.59$$

$$(g_3 f_3 = h \Rightarrow 5/c = h \Rightarrow c = 2.59)$$


Ratioed logic

Pass transistor logic

Pseudo NMOS Ratioed Logic

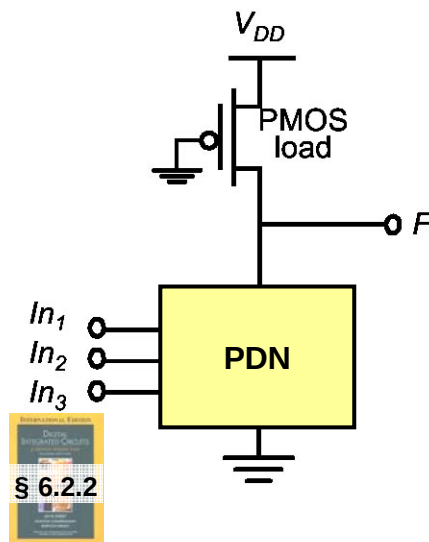

 - ☺ Reduced area
- ☺ Reduced capacitances
- ☹ Increased V_{OL}
- ☹ Reduced noise margins
- ☹ Static dissipation



TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational

3/15/2009

47

Ratioed Logic V_{OL} Computation

$$I_{Dn} \text{ (linear)} = I_{Dp} \text{ (saturation)}$$

Exercise: verify these assumptions/steps

$$k_n \left((V_{DD} - V_{Tn}) V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left((-V_{DD} - V_{Tp}) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn}) V_{OL} \approx k_p (-V_{DD} - V_{Tp}) V_{DSAT}$$

Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} V_{DSAT} \approx \frac{\mu_p W_p}{\mu_n W_n} V_{DSAT}$$

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 08 Combinational


3/15/2009

48

Pass-transistor and Pass-gate circuits

Pass Transistor Logic

 - Save area, capacitances
- Need complementary inputs (extra inverters)



But remember:

NMOS vs. PMOS, pull-down vs. pull-up

pull-down

pull-up

pull-down


pull-up

- PMOS is better pull-up
- NMOS is better pull-down



Pass Transistor Logic

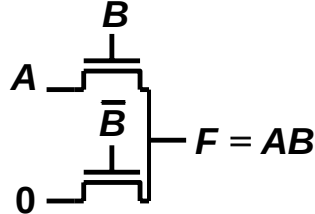
- Save **area, capacitances**
- Need complementary inputs (might mean extra inverters)
- Reduced V_{OH} , **noise margins**
- $V_{OH} = V_{DD} - (V_{Tno} + \gamma((\sqrt{2\phi_f} + V_{OH}) - \sqrt{2\phi_f}))$
- **Static dissipation** in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by **complementary pass gates** (NMOS + PMOS parallel)



 Exercise: Why is there static dissipation in next conventional gate?

Pass Gates

- Remedy: use an N-MOS and a P-MOS in parallel




- Pass gates **eliminate** some of the **disadvantages** of simple pass-transistors
- But also some of the **advantages**
- Design remains a **trade-off!**

Pass-gate a.k.a. Transmission-gate


 
Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?



Pass Transistor Logic

  - Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$ (S' is easier notation for $S\text{-bar} = S\text{-inverse} = \overline{S}$)
- $Y = ((AS)' (BS)')'$ allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8) transistors (see also Katz, section 4.2)



Summary

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
 - **Complex Logic Gates**
 - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**