 


## **MODULE 9**

### **Chapter 7**




## **SEQUENTIAL ELEMENTS**

## Sequential Elements - Outline

- **Background**
  - Timing, terminology, classification
- **Static Flipflops**
  - Latches
  - Registers
- **Dynamic Flipflops**
  - Latches
  - Registers
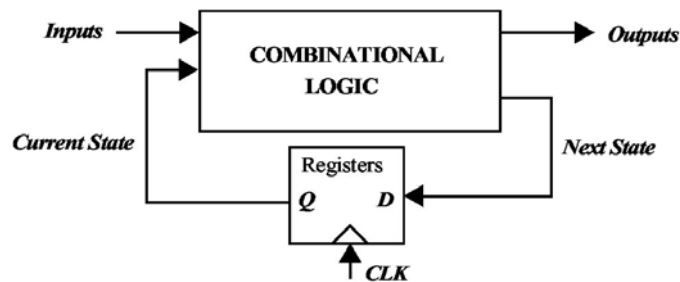
## FSM with Positive Edge Triggered Registers



- Flip-flops provide **memory/state**
- VLSI uses predominantly **D-type flip-flops**


## Memory elements

- Store a **temporary value**, remember a **state**
- Typically controlled by **clock**.
- May have load signal, etc.
- In CMOS, memory is created by:
  - **capacitance** (dynamic);
  - **feedback** (static).
- Also see [http://en.wikipedia.org/wiki/Flip-flop\\_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))

## Variations in memory elements

- Form of required clock signal.
- How behavior of data input around clock affects the stored value.
- When the stored value is presented to the output.
- Whether there is ever a combinational path from input to output.

## Timing Metrics Reminder

 

$t_{c-q}$  : delay from clock (edge) to Q

$t_{su}$  : setup time

$t_{hold}$  : hold time

$t_{plogic}$  : worst case propagation delay of logic

$t_{cd}$  : best case propagation delay  
(contamination delay)

$T$  : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

## Latches vs. Registers

### Latch

**Level-sensitive**

**Transparent** when clock is active

Clock active high: **positive** latch

Clock active low: **negative** latch

**Faster, smaller**

### Register

**Edge-triggered**

Input and output **isolated**

Sampling on 0 → 1 clock: **positive edge triggered**

Sampling on 1 → 0 clock: **negative edge triggered**

**Safer**

## Static vs. Dynamic Memory Elements

### Static

Operate through **positive feedback**

**Preserve state** as long as power is on

Can work when clock is **off**

**More robust**

### Dynamic

**Store charge** on (parasitic) capacitor

Charge **leaks** away (in milliseconds)

Clock must be kept **running** (for periodic refresh)


**Faster, smaller**

## Static Flipflops

### ■ Latches


### ■ Registers

## Positive Feedback: Bi-Stability

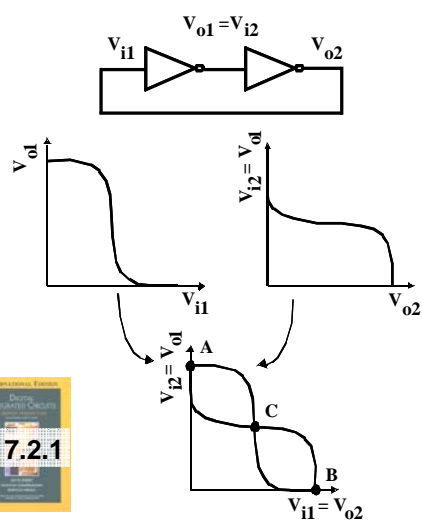

- Loop-gain in A,B  $\ll 1$
- A,B: **stable** points
- Loop-gain in C  $\gg 1$
- C: **meta-stable** point

## Meta-Stability

 



- Gain should be **larger than 1** in the transition region
- **Smaller than 1** in stable region

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009



11

## SR-Latch

  

| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | $\bar{Q}$ |
| 1 | 0 | 1 | 0         |
| 0 | 1 | 0 | 1         |
| 1 | 1 | 0 | 0         |

← forbidden

  

| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 1 | 1 | Q | $\bar{Q}$ |
| 0 | 1 | 1 | 0         |
| 1 | 0 | 0 | 1         |
| 0 | 0 | 1 | 1         |

← forbidden



§ 7.2.5



■ Construction of **D-latch**


■ D-latch **most common in VLSI**

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009


12

## Clocked SR-Latch

 

- Naïve implementation
- 16 transistors
- D latch requires 9xN, 9xP
- Master-slave D-register needs 18xN, 18xP
- Larger area, cost, power

## CMOS Clocked SR-Latch

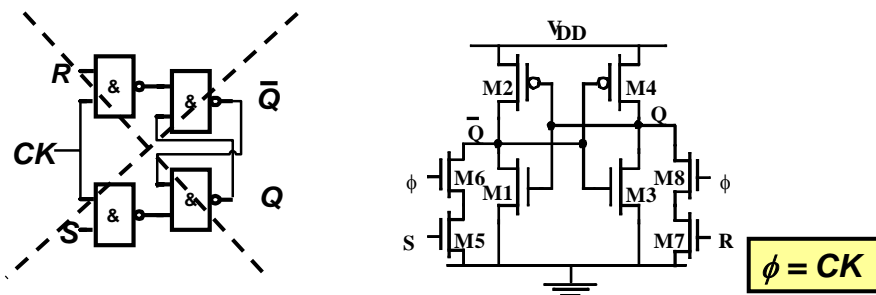


- Save 6 (incl. 4 large) PMOS transistors and 2 NMOS
- D-latch requires 7 x N, 3 x P (instead of 9xN, 9xP)

**Q:** Is this a **ratioed** design or not?  
Does it consume static power?


 
## Sizing for 'Set' Action

- $M_3$ - $M_4$  form conventional inverter
- Model  $M_5$ - $M_6$  as one equivalent (double length) transistor  $M_{56}$
- Assume  $Q = 0 \rightarrow M_1$  is off,  $M_2$  is on
- $M_2$ - $M_{56}$  operate like ratioed pseudo NMOS inverter
- Latch switches when  $M_{56}$  pulls input of  $M_3$ - $M_4$  below their switching threshold (assume  $V_{DD}/2$ )
- Positive feedback amplifies switching
- $M_2$  and  $M_{56}$  both in velocity saturation around  $V_Q = V_{DD}/2$





$$k'_n \left( \frac{W}{L} \right)_{5-6} \left( (V_{DD} - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k'_p \left( \frac{W}{L} \right)_2 \left( (-V_{DD} - V_{Tp}) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009

15

## Sizing for 'Set' Action

  



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009

16



## SR Latch Timing

  


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009

17

## Multiplexer-Based Latches

 

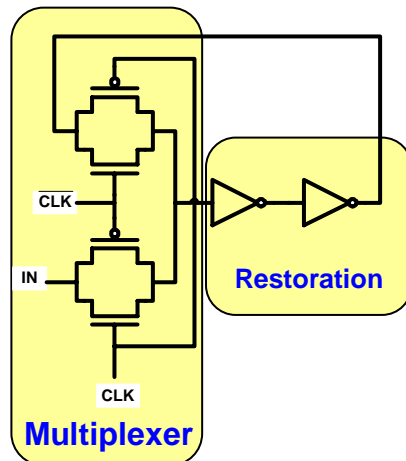
### Recirculating latch



§ 7.2.2

Mux-based latches much more common in modern dig. IC's




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009


18

## Recirculating latch

 

- **Quasi-static**, static on one phase
- Feedback **restores** value
- Requires 4 x N, 4 x P, minimum size  
(compare 7 x N, 3 x P, non-minimum size)
- $\phi_1$  and  $\phi_2$  inverse but should be non-overlapping
- Can suffer from **charge sharing** (when  $\phi$  not non-overlapping)
  - Output connected directly to input
  - $C_{in}$  and  $C_{load}$  form communicating vessels


## Insensitive for Charge Sharing

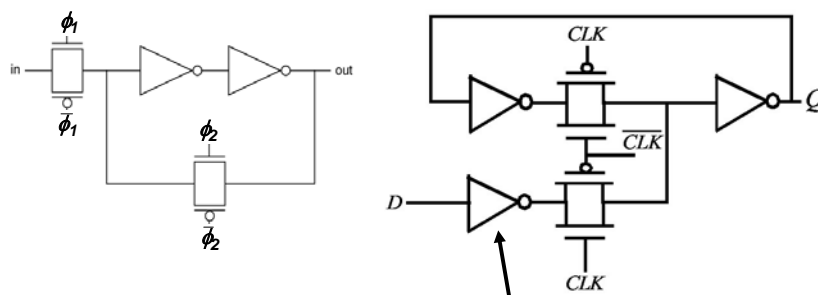

- **Non ratioed**
- **High load to CLK**



Uni-directionality of this inverter prevents coupling between Q and D

## Recirculating NMOS Latch.

 

- Degraded 1 at X
- Lower noise margin, higher delay, power
  
## Latch Designs can Suffer from Race Problems




Signal can **race around** during  $\phi = 1$


 
## Registers

- Not transparent—use multiple storage elements to isolate output from input.
- Master-slave, edge triggered principle




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009

23

## Master-slave operation

 

$\phi = 0$ :

- master latch is disabled;
- slave latch is enabled,
- but master latch output is stable,
- so output does not change.

$\phi = 1$ :


- master latch is enabled,
- loading value from input;
- slave latch is disabled,
- maintaining old output value.

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009


24
 
## Transistor Level Master Slave Positive Edge Triggered Register




- Robust Design
- Can eliminate  $I_1$  and  $I_4$ , however, they make design more robust (avoid charge sharing, robust input)
- High Clock Load (8 x)

## Set-up Time Simulation

 

**Slightly smaller delay  
between D and CLK**

## Ratioed Reduced Clock Load Register

 

- $I_2$  and  $I_4$  are small, even long
- Lower clock load
- Increased design complexity
- Reduced robustness (reverse conduction)

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 09 Sequential

3/15/2009

27

CMOS Flip-Flop Construction - Microsoft Internet Explorer

File Edit View Favorites Tools Help

Back Search Favorites Go Links

Address [http://www.play-hookey.com/digital/cmos\\_d\\_flip-flop.html](http://www.play-hookey.com/digital/cmos_d_flip-flop.html)

## CMOS Flip-Flop Construction

CMOS technology allows a very different approach to flip-flop design and construction. Instead of using logic gates to connect the clock signal to the master and slave sections of the flip-flop, a CMOS flip-flop uses *transmission gates* to control the data connections. (See the [CMOS gate electronics page](#) for a closer look at the transmission gate itself.)

The result is that a controllable flip-flop can be built with only inverters and transmission gates — a very small and simple structure for an IC.

The basic CMOS D flip-flop is shown below.


[www.play-hookey.com](http://www.play-hookey.com)

clickable



Internet
 
## Dynamic latch

Stores charge on inverter gate capacitance:



## Dynamic Edge Triggered Register

  

Is this a + or - edge triggered reg?

|                    |                              |                                      |
|--------------------|------------------------------|--------------------------------------|
| $t_{su}$           | $t_{T1}$                     |                                      |
| $t_{hold}$         | approximately zero           |                                      |
| $t_{cq}$           | $t_{I1} + t_{T2} + t_{I3}$   |                                      |
| $t_{overlap\ 0-0}$ | $< t_{T1} + t_{I1} + t_{T2}$ | Prevent race through $T_1, I_1, T_2$ |
| $t_{hold}$         | $> t_{overlap\ 1-1}$         | Enforce hold-time constraint         |

## Summary

- **Background**

- Timing, terminology, classification

- **Static Flipflops**

- Latches
  - Registers

- **Dynamic Flipflops**

- Latches
  - Registers