 


MODULE 7

TIMING DESIGN



TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 1

Outline

- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
- The Clock Skew Problem
- Controlling Clock Skew
- Case Study

Get basic appreciation of some
system level design issues

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 2

Design of LARGE Integrated Circuits


- **Correct signal**
 - Logic value
 - Right level (restoring logic, ...)
- **At right place**
 - Interconnect (R, C, L)
 - Busses
 - Off-chip drivers, and receivers
- **At right time**
 - How to cope with (uncertain) delay

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 3

Case Study: IBM Power6 CPU

 

- introduced 21 may 2007
- 64 bit, dual core
- 790 million transistors
- 4.7 (5⁺) GHz
- 65nm SOI, 10 Cu levels interconnect
- 2 Cores
- 8 MB on-chip level2 cache
- processor bandwidth: 300GB/sec
- 1953 signal I/O, 5449 power I/O


<http://www-03.ibm.com/press/us/en/pressrelease/21580.wss>

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 4


IBM 65nm SOI Technology

 

Uncertain Delay

- Data-dependent Delay
- Short and long combinational paths
- Device parameters variations (§3.4)
 - Batch to batch V_t threshold voltage
 - Wafer to wafer k' transconductance
 - Die to die W, L dimensions
- Supply Variations
 - IR drop, dI/dt drop, ringing,
- Interconnect Delay
 - Don't know length of line during logic design
 - Delay at begin of line smaller than at end
 - Interconnect parameter variability

Delay Along a Wire (Module 3)

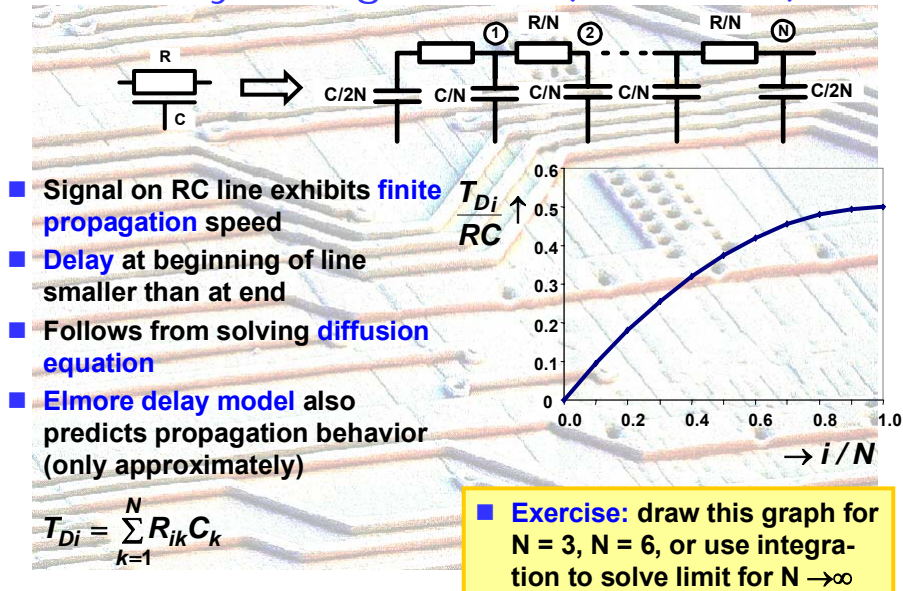


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 7

Delay of Clock Wire

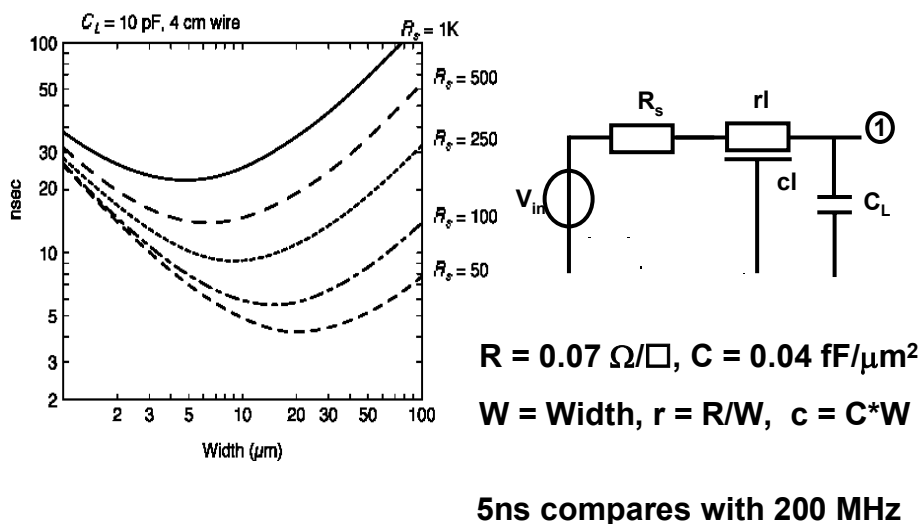

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing


3/23/2009

7 timing 8

Canonical Clock Tree Network

R_1 Clock Driver Output Resistance
 R_2 - R_4 Clock Line Segment Resistance
 C_2 - C_4 Clock Line Segment Capacitance
 CL_1 - CL_4 Clock Load Capacitance (from flip-flops)

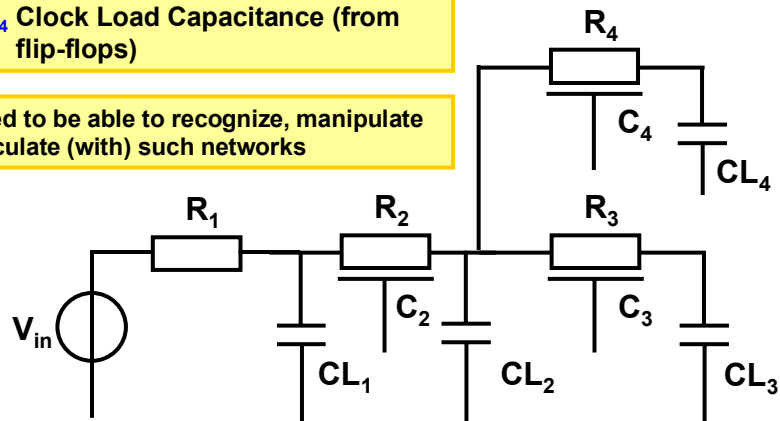You need to be able to recognize, manipulate and calculate (with) such networks



TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 9

Impact of Uncertain Delay

- **Combinational circuits** will eventually **settle** at correct output values when inputs are stable
- **Sequential circuits**
 - Have **state**
 - Must guarantee **storing of correct signals at correct time**
 - Require **ordered computations**

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 10

Sequential Circuits

- Sequential circuits require **ordered computation**
- Several ways for **imposing ordering**
 - ✓ ■ **Synchronous** (clock)
 - ✗ ■ **Asynchronous** (unstructured)
 - ✗ ■ **Self-timed** (negotiation)



- Clock works like an **orchestra conductor**



Synchronous Design

- **Global Clock Signal**
- Synchronicity may be **defeated** by
 - **Delay uncertainty** in clock signal
 - Relative timing errors: **clock skew**
 - **Slow** logic paths
 - **Fast** logic paths

Timing Metrics Reminder

  

t_{c-q} : delay from clock (edge) to Q

t_{su} : setup time

t_{hold} : hold time

t_{plogic} : worst case propagation delay of logic


t_{cd} : best case propagation delay (contamination delay)

T : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Sequential Circuit Timing.

 


$$T_{clk} > t_{c-q} + t_{plogic} + t_{su}$$

$$t_{plogic} = t_{p,add} + t_{p,abs} + t_{p,log}$$

How to reduce T_{clk} ?

Pipelined Laundry System

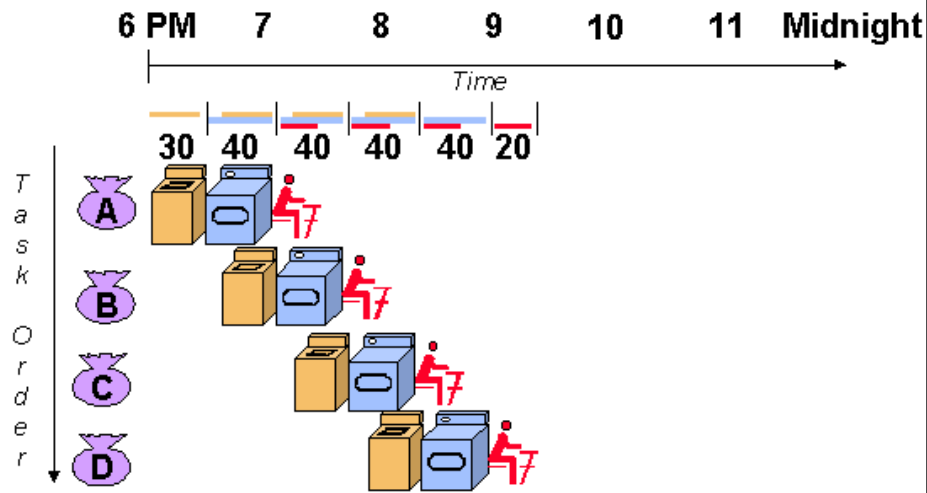

Also: <http://en.wikipedia.org/wiki/Pipelining>


From <http://cse.stanford.edu/class/sophomore-college/projects-00/risc/pipelining/index.html>
which credited <http://www.ece.arizona.edu/~ece462/Lec03-pipe/>

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 15

Pipelining

 

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

$$T_{clk} > t_{c-q} + \max(t_{p,add}, t_{p,abs}, t_{p,log}) + t_{su}$$

§ 7.5

- Improve resource utilization
- Increase functional throughput

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 16

Pipelining Observations

- Very popular/effective measure to increase functional **throughput and resource utilization**
- At the cost of increased **latency**
- All high performance microprocessors excessively use pipelining in **instruction fetch-decode-execute sequence**
- Pipelining efficiency may fall dramatically because of **branches** in program flow
 - Requires emptying of pipeline and **restarting**
 - Partially remedied by **advanced branch prediction techniques**
- But all is dictated by **GHz marketing drive**
 - All a customer asks is: **“How many GHz?”**
 - Or says: **“Mine is ... GHz!”**

Bottom line: more flip-flops, greater timing design problems

The Clock Skew Problem


- In Single Phase Edge Triggered Clocking
- In Two Phase Master-Slave Clocking



(Also: Katz § 6.2.2)

The Clock Skew Problem

Clock Rates $\gg 1$ GHz in CMOS

 


- Clock Edge Timing Depends upon Position
 - Because clock network forms distributed RC line with lumped load capacitances at multiple sites (see earlier slide)
- (Relative) Clock Skew $\delta = t_{\phi}'' - t_{\phi}'$
- Clock skew can take significant portion of T_{clk}

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 19

Positive and Negative Skew

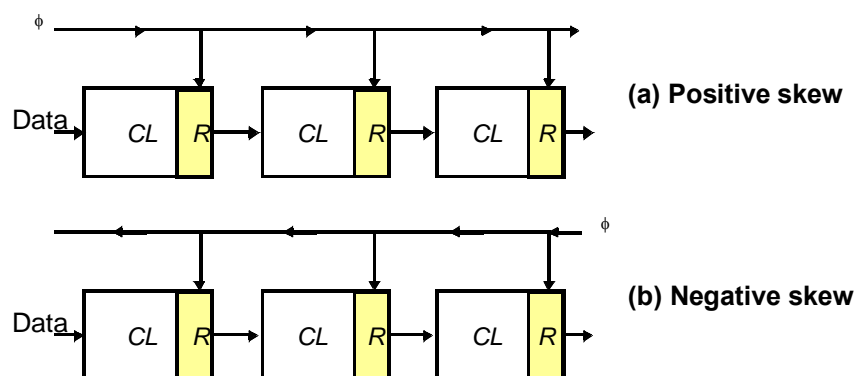


TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 20

Edge-Triggered Slow Path Skew Constraint

 

Timing constraint


$$T + \delta \geq t_{\max} = t_{p,\text{logic}} + t_i + t_{c-q,\text{max}} + t_{\text{su}} \quad (t_i = \text{interconnect delay})$$

Internal delay of flip-flop

$$T \geq t_{\max} - \delta$$

- **Minimum Clock Period Determined by Maximum Delay between Latches minus skew**

Edge-Triggered Fast Path Skew Constraint

 

Timing constraint

$$\delta \leq t_{\min} = t_{cd,\text{logic}} + t_i + t_{c-q,\text{min}} - t_{\text{hold}}$$

In recv. latch

In sending latch

- **Maximum Clock Skew Determined by Minimum Delay between Latches**

Clock Constraints in Edge-Triggered Logic

$$T \geq t_{\max} - \delta$$

$$\delta \leq t_{\min}$$

- **Observe:**

- Minimum Clock Period Determined by Maximum Delay between Registers minus clock skew
- Maximum Clock Skew Determined by Minimum Delay between Registers

- **Conclude:**

- Positive skew must be bounded
- Negative skew reduces maximum performance

Controlling Clock Skew

Case Study



Countering Clock Skew Problems


- Routing the clock in **opposite direction** of data (negative skew)
 - Hampers performance
 - Dataflow not always uni-directional
 - Maybe at sub circuit (e.g. datapath) level
 - Other approaches needed at global chip-level
 - Useful skew (or beneficial skew) is serious concept
- Enlarging **non-overlap periods** of clock [only with two-phase clocking]
 - Hampers performance
 - Can theoretically always be made to work
 - Delay in clock network may require impractical/excessively large scheduled $T_{\phi 12}$ to guarantee minimum $T_{\phi 12}$ everywhere across chip
 - Is becoming less popular for large high performance chips

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 25

Dataflow not unidirectional

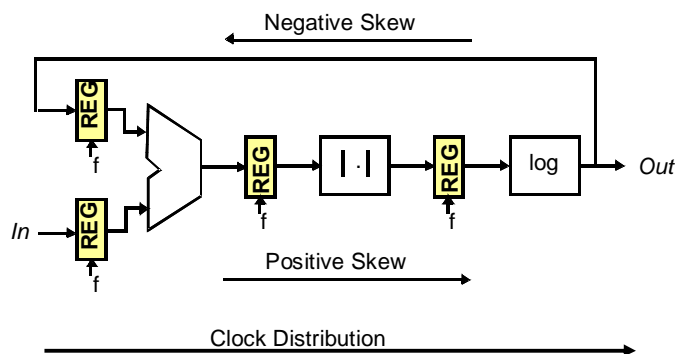

- Data and Clock Routing
- Cannot unambiguously route clock in opposite direction of data
- Need bounded skew

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing


3/23/2009

7 timing 26

Need bounded Skew

- Bounded skew most practical measure to guarantee functional correctness without reducing performance
- Clock Network Design
 - Interconnect material
 - Shape of clock-distribution network
 - Clock driver, buffers
 - Clock-line load
 - Clock signal rise and fall times
 - ...


H-tree Clock Network

 

- All blocks equidistant from clock source \Rightarrow **zero (relative) skew**
- **Sub blocks** should be small enough to ignore intra-block skew
- In practice perfect H-tree shape **not realizable**

Observe: Only Relative Skew Is Important

Clock Network with Distributed Buffering

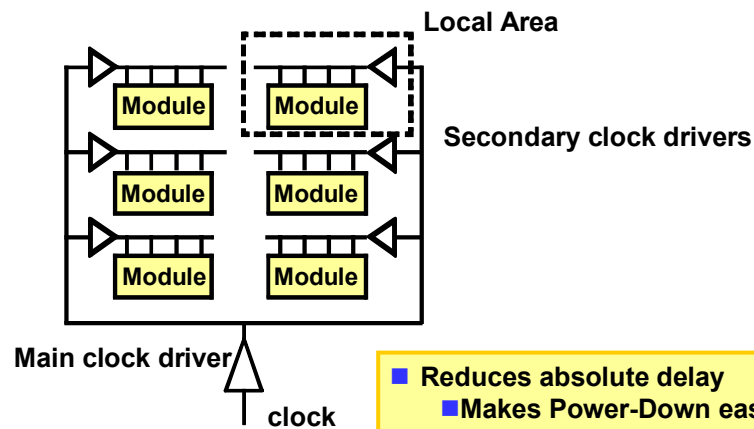



- Reduces absolute delay
 - Makes Power-Down easier
 - Easier of-chip communication
- Sensitive to variations in Buffer Delay

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 29

Power6 Clock Distribution

  

- Latency ~ cycle time


friedrich, isscc 2007

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 30

Power6 Clock Distribution

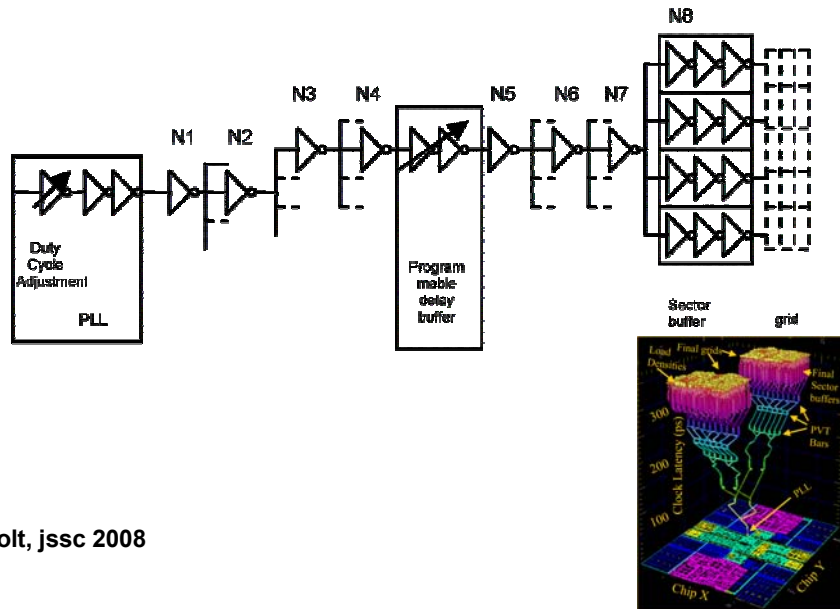


stolt, jssc 2008

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 31

IBM Power6 Physical Design Flow

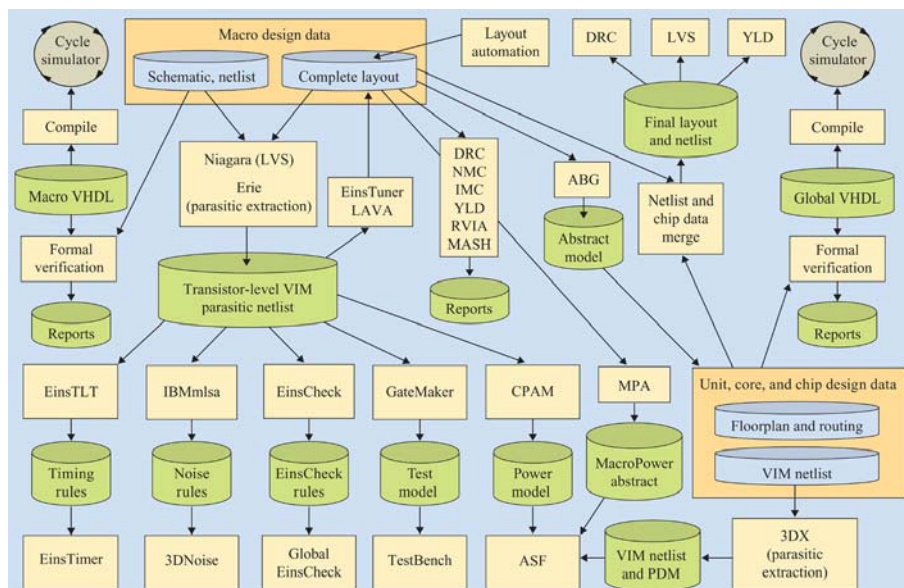

berridge, ibmjrd 2007

TUD/EE ET4293 Dig. VLSI 0809 - © NvdM - 09- timing

3/23/2009

7 timing 32

Timing Design

- Clocking Scheme is important design decision
- Influences
 - Power
 - Robustness
 - Ease of design, design time
 - Performance
 - Area, shape of floor plan
- Needs to be planned early in design phase
- But is becoming design bottle neck nevertheless
 - Clock frequencies increase
 - Die sizes increase
 - Clock skew significant fraction of T_{clk}
- Alternatives
 - Asynchronous or self-timed

Not in this course



Summary

- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
- The Clock Skew Problem
- Controlling Clock Skew
- Case Study

**Got basic appreciation of some
system level design issues?**