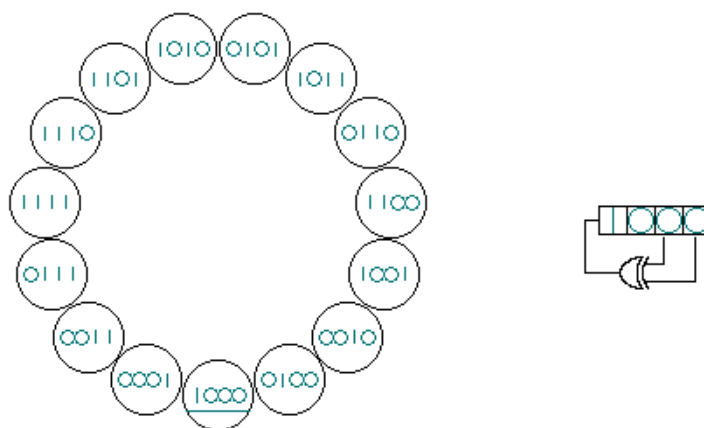


## Project


- **Pseudo Random Number Generator (PRNG)**
- A 'counter' producing an output sequence that **approximates** the properties of **random numbers**
- Pseudo random sequences have **many applications**
  - Spread spectrum communication
  - Whitening
  - Monte-Carlo simulation
  - Stream ciphers
  - Test pattern generation
  - ...

## 4-bit Fibonacci LFSR




[http://en.wikipedia.org/wiki/Linear\\_feedback\\_shift\\_register](http://en.wikipedia.org/wiki/Linear_feedback_shift_register)

## Fibonacci vs. Galois Style

 

 Can expect differences in speed/power tradeoff



## Project Requirements

- 8 bit PRNG
- Tap positions at 8, 6, 5, 4 for Fibonacci type
- Choose between Fibonacci or Galois (adapt 'taps' for Galois)
- Clock frequency to be specified (must use clock)
- Ideal non-overlapping 2-phase clock is made available
- 90nm UMC CMOS technology
- 10 fF load at each output
- Clock frequency 800 Mhz, 50ps slopes
- Circuit – Simulation – Spectre Simulation (No Layout)

## Design Goal and Deliverables

- **Design Goal: lowest power requirements**
  - All will use same test bench
  - VDD is variable (design specific)
  - Projected area of design (i.e. sum of transistor sizes) is not of concern
  
- **Deliverables (electronically):**
  - Design database (for checking performance)
  - Presentation
  - Design report

## Grading

- **Final grade 50/50% project/exam**

50%	Exam	Written exam (example will be made available)
30%	Design	Correctness, creativity, elegance, robustness A correct design gives at least a 6.
10%	Presentation	Relevance, information, (presentation skills)
10%	Report	Relevance, information, documentation ( <b>design decisions</b> ) (brief, factual, clarity and easy of reading (!), documentation, not essay or paper)

## Contest

### Bonus points for top-n


- 2 points for winner team
- 1.5 points for 2<sup>nd</sup> place, 1 for 3<sup>rd</sup>, 0.5 for 4<sup>th</sup>, 5<sup>th</sup> place
- Bonus to be added to overall mark

## Presentations

- Why is your design good
- What is special about it
- Present design decisions, trade-offs, ...
- Include important schematics, waveforms, ...
- Everything needed for demonstrating functionality and performance
- Try to avoid mostly-black screendumps for graphics, schematics
- References/citations (!)
  
- PPT presentation, ~ 10 minutes including Q&A
 
## Project Schedule

- **Due date: Thu Apr 16**  
(2<sup>nd</sup> week of next lecture period) Agree?
- **Presentations: 15:30 - finished**



## Feel free to



- **Use any circuit style (Chapter 6)**
  - complementary CMOS, ratioed logic, DCVSL, pass-transistor logic, CPL, dynamic logic, ...  
(No need to stick to style from book)
- **Any clocking scheme / Flip Flop type (Chapter 7)**
  - single phase, two phase, four phase, ...
  - Avoid Races
- **Consider any known (or unknown 😊) technique to improve power**
  - **ckt level**: body bias, sub-threshold logic, ... ,
  - **design**: automatic sizing, ...



## 2-phase Clock

- 2-phase clock is made available, can use 1 phase if you want
- More advanced clock has to be derived from it
- Only circuit design, no layout needed for clock generation
- Report (poster) should show schematic, design rationale, resulting waveforms
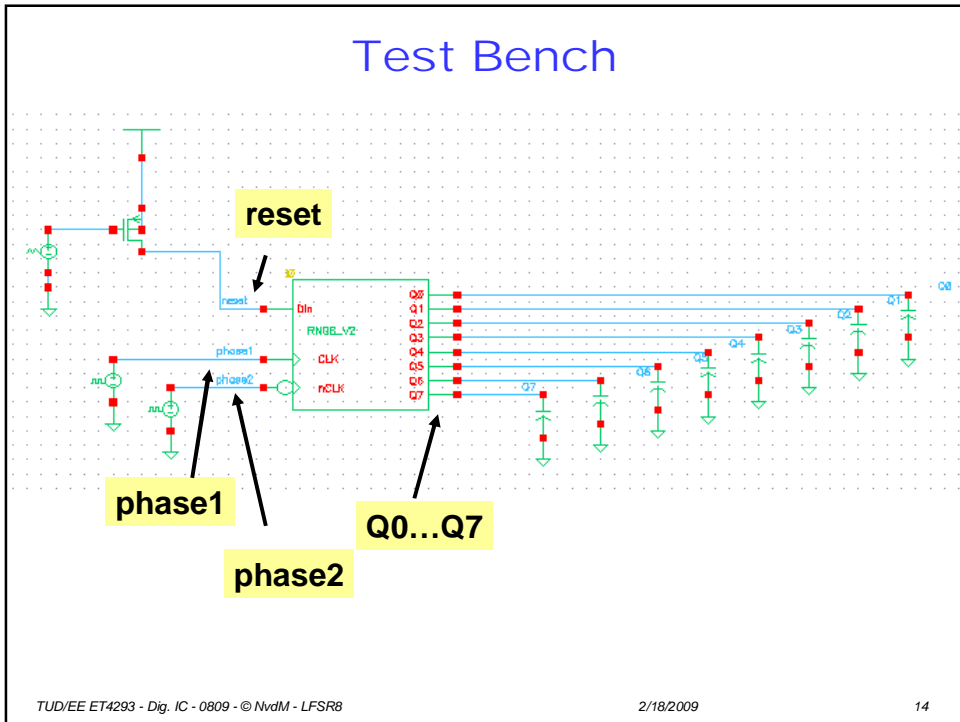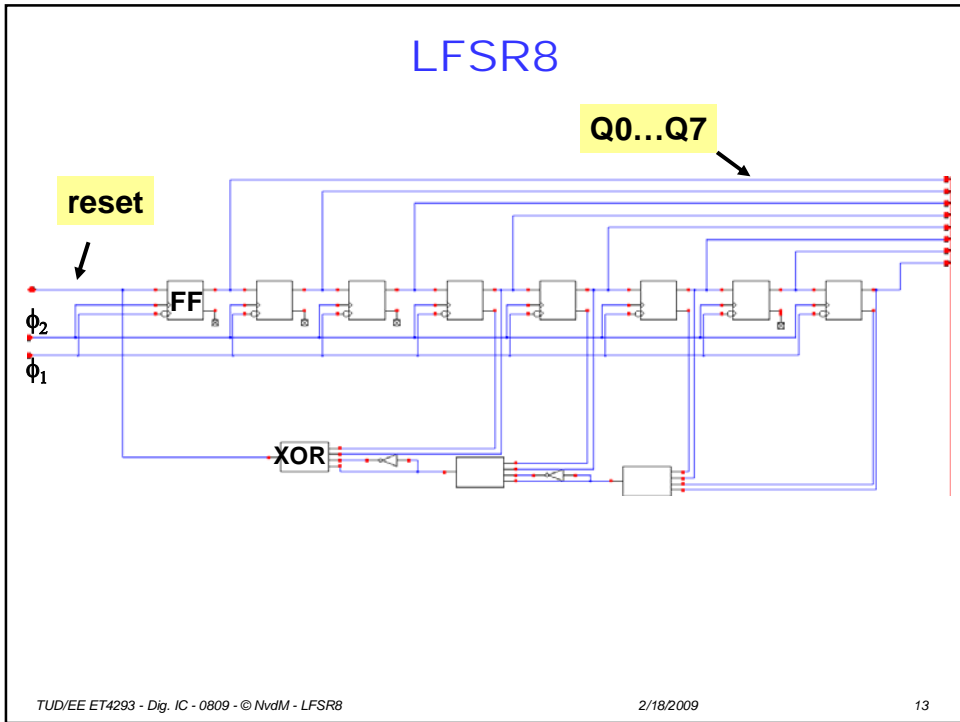
## Reference Schematic


- Reference netlist is made available
- This netlist is not tuned, transistors are minimum size, topology not necessarily optimal



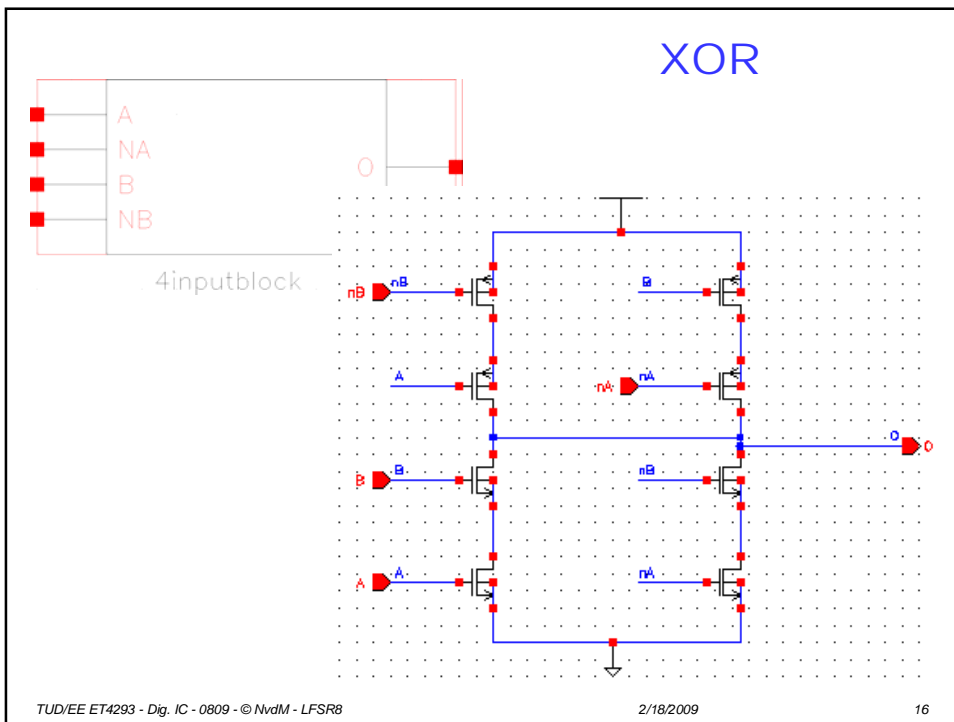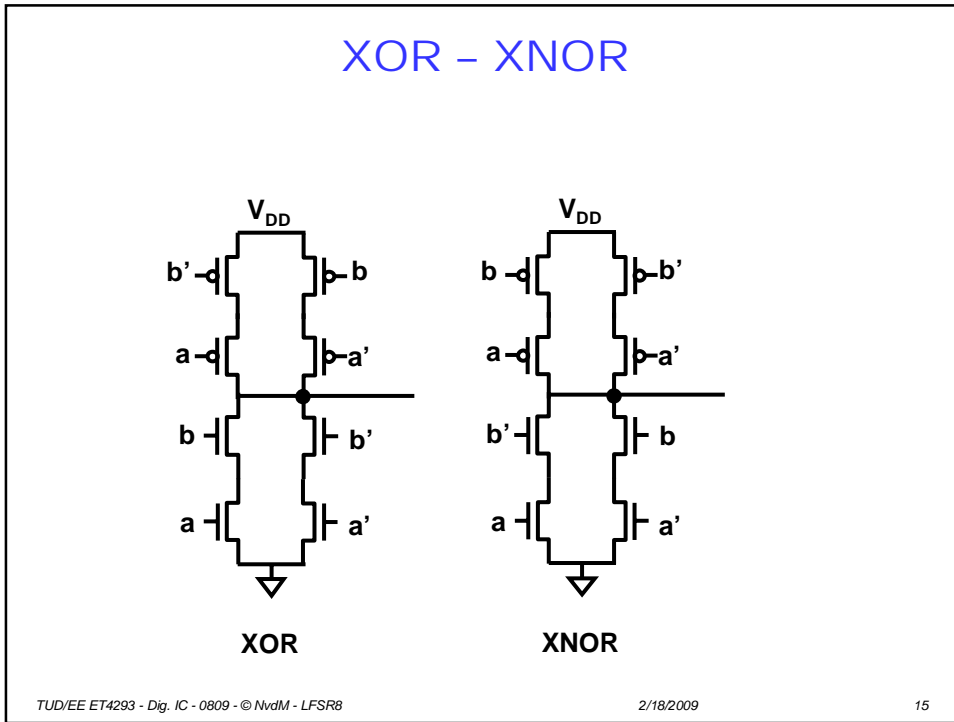




### XOR-2 alternatives

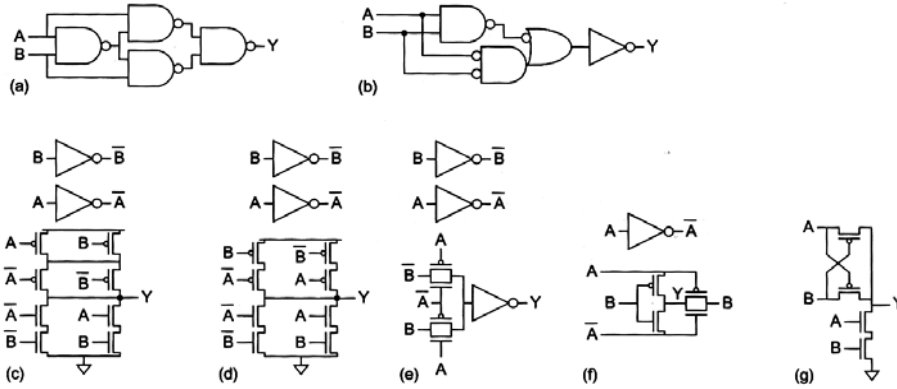

[Weste/Harris]



$AB=00 \rightarrow V_{out} = |V_{TP}|$


### XOR-4 alternatives

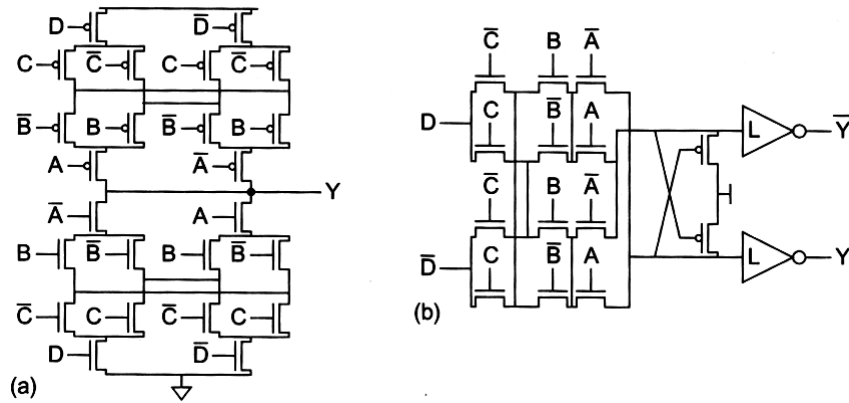

[Weste/Harris]

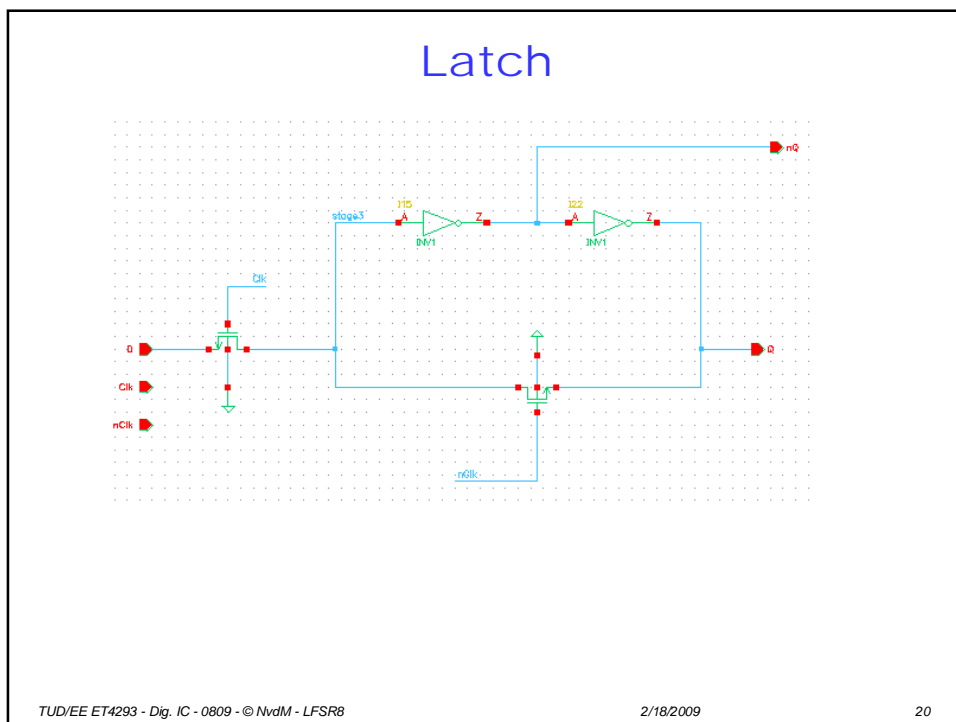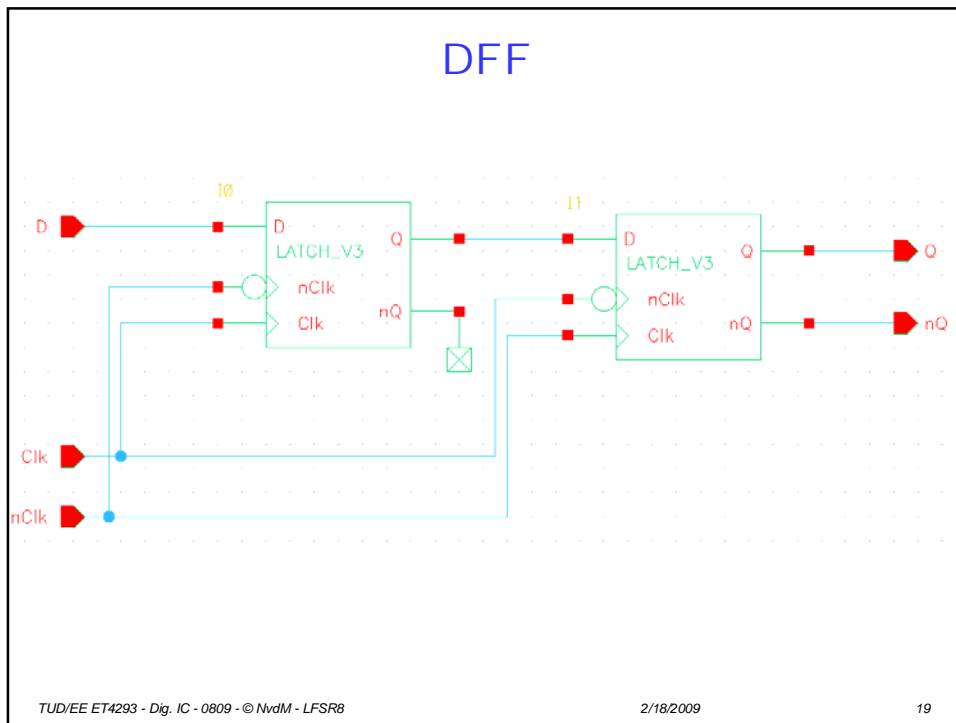- Can be more compact, not necessarily faster than xor2



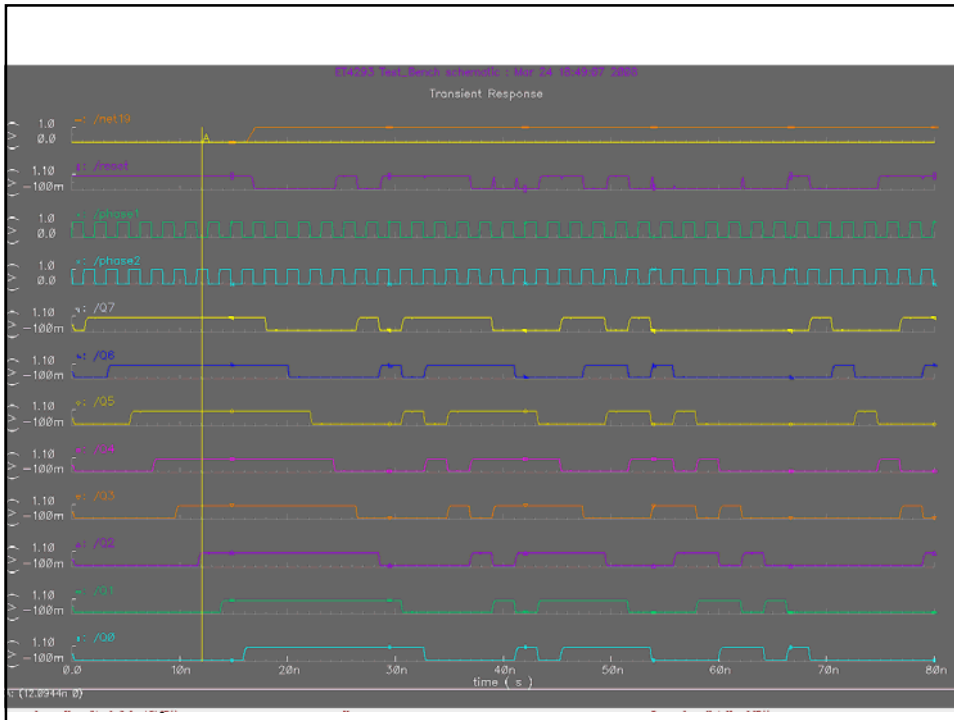

**?**

TUD/EE ET4293 - Dig. IC - 0809 - © NvdM - LFSR8 2/18/2009 22