

- a. Draw the schematic of the corresponding dual pull-up network.

Schematic of pull-up

- b. What is the logic function of the gate?

Function:

- c. A layout needs to comply with a set of design rules. Explain what kind of rules they are, and explain their purpose.

Explanation:

- d. Assume that the output will be loaded with $C = 50$ fF. Compute the worst-case propagation delay for a high-to-low transition, t_{pHL} . Use the transistor dimensions from the layout. You can use the equivalent on-resistance approximation with R_{eq} ; you don't need to apply the current formulas.

$t_{pHL} =$

Calculation:

- e. Which of the transistors M_1 en M_2 in the schematic can experience the body effect?

M_1

M_2

Explanation:

Name:	Student number:
-------	-----------------

f. Discuss the effect of the body effect on the performance of the circuit.

Discussion:


g. Certain areas in the layout correspond to the labeled nodes in the circuit (those identified by a circled number or by the symbols X, X', Y en Y'). The layout regions are identified by arrows and letters A through F. Multiple regions can correspond to the same node, not all nodes in the schematic are necessarily labeled in the layout.

Schematic	Layout
1	
2	
3	
4	

Schematic	Layout
X	
X'	
Y	
Y'	

 Question 2.

Consider the circuit on the right. Calculate I_D when $V_{out} = 0.25$ V. Give the corresponding equation for the region of operation (do not fill in numbers) and the answer. Assume the parameters from the inside-back cover of Rabaey. Hint: only write the equation and skip the actual calculation if you are on shortage of time.




$I_D =$

Equation:

Question 3.

Consider the circuit on the right. It can be used as a low-swing driver. Assume the input transition time is 0, the input swing is between 0 and VDD, and take

$$\phi_f = -0.3V.$$

 

a. Write the equations for V_{OH} and V_{OL} taking into account the body effect in both transistors. First write it using symbols, than fill in numbers. You don't need to solve the equations.

Equation with symbols: $V_{OH} =$
Equation with values: $V_{OH} =$
Equation with symbols $V_{OL} =$
Equation with values: $V_{OL} =$

b. Assume the output swing is between 0.8 V and 1.7 V. To estimate the t_{pHL} , you want to compute the current delivered by the PMOS. What is (are) the operating region(s) of the PMOS transistor? Clearly give the ranges of V_{out} for each operating region that you find.

Operating regions and voltage ranges:

c. Assume that the average pull-down current over the full output swing is 400 μA . Calculate t_{pHL} .


$t_{pHL} =$
Calculation:

Name:

Student number:

 Question 4.

Consider the circuit on the right. All NMOS transistors have the W/L ratio of 3. Use the R_{eq} data from the Rabaey tables. V_{DD} is 2.5 V.



a. What is the logic function of the output Y?

Y =

b. If the input is 10011, calculate the effective pull-down resistance. Only answer, no calculation.

R_{pd} =

c. Consider 2 scenarios. In scenario A, the input goes from 01000 to 11000. In scenario B, the input goes from 10000 to 11000. Which scenario is faster (which as the lowest T_{pHL})? Circle the right answer, and explain.

Scenario A is faster	Scenario B is faster	Both are equally fast	Cannot determine
Explain:			


Question 5.

a. The logical effort of an inverter is 1. Determine the logical effort of a NOR-2 gate which is used as an inverter (2 inputs wired together).

$g =$

Explanation/calculation:

Question 6.

 

a. Calculate the optimum sizing for the logic circuit shown above. C_i denotes the gate capacitance of gate i . The size of gate i will be denoted as S_i . The load capacitance C_L is 45 times the gate capacitance of the first inverter C_1 . Determine the sizes S_2 - S_4 of gates 2-4 respectively (in multiples of the size of gate 1) that minimize the path delay. Assume $\gamma = 1$.

$S_2 =$

$S_3 =$

$S_4 =$

Calculation:

Name:

Student number:

Question 7.

a. Consider a possible implementation for a 2-phase non-overlapping clock generator as shown on the right. Draw the waveforms for CLK_1 and CLK_2 below, given the waveform of CLK_0 . The clock period is 20τ , as shown on the horizontal axis of the waveform. The propagation delays of the inverter, buffer and NAND gates are τ , τ , and 2τ respectively, as indicated in the figure. Assume all rise and fall times are 0 (infinite slopes).

