

### Dynamic Power Consumption

Power = Energy/transition • Transition rate

$$= C_L V_{DD}^2 \cdot f_{0 \rightarrow 1}$$

$$= C_L V_{DD}^2 \cdot f \cdot P_{0 \rightarrow 1}$$

$$= C_{switched} V_{DD}^2 \cdot f$$

- Transistor Sizing

- Physical capacitance
- Input and output rise/fall times
- Short-circuit power
- Threshold and temperature
- Leakage power
- Switching activity

- Power dissipation is data dependent – depends on the switching probability
- Switched capacitance  $C_{switched} = P_{0 \rightarrow 1} C_L = \alpha C_L$  ( $\alpha$  is called the **switching activity**)

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 1

### Signal Probabilities in Simple Gates

Let  $P_x(s)$ ,  $x \in \{0,1\}$ , be the probability of signal  $s$  being  $x$   
**Obviously**,  $P_0(s) = 1 - P_1(s)$

**Observe:**

- Output of NOR is low iff all inputs are high
- Output of NAND is high iff all inputs are low

**Conclude:**

- $P_0(\text{NOR}) = \prod P_1(\text{input } i)$
- $P_1(\text{NAND}) = \prod P_0(\text{input } i)$

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 2

### Signal Probabilities Example

Example: propagate signal probabilities to outputs  
 Assume  $P_1$  of primary inputs given and **independent**

$P_1 = 0.9 \times 0.5 \times 0.1 = 0.045$

$P_0 = 0.045 \times 0.99 \times 0.25 = 0.011$   
 $P_1 = 1 - P_0 = 0.989$

$P_0 = 0.1 \times 0.1 = 0.01$   
 $P_1 = 1 - P_0 = 0.99$

$P_1 = 0.5 \times 0.5 = 0.25$

This fails upon reconvergent fanout, correlation of inputs

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 3

### Signal Probabilities in AOI gates

Consider probabilities of blocks being on or off, rather than logic levels  
 Output is 1 if the pull-down network is off and vice versa

**Observe:**

- A parallel block (NOR) is off if all constituting blocks are off
- A series block (NAND) is on if all constituting blocks are on

$P_{off}(\text{NOR}) = \prod P_{off}(\text{block } i)$   
 $P_{off} = P_0(a) \times P_0(b)$

$P_{on}(\text{NAND}) = \prod P_{on}(\text{block } i)$   
 $P_{on} = P_1(c) \times P_1(d)$

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 4

### Signal Probabilities in AOI gates (2)

$P_{off}(\text{NOR}) = \prod P_{off}(\text{block } i)$   
 $P_{off} = P_{off}(\text{block } 1) \times P_{off}(\text{block } 2)$   
 $= P_0(a) \times P_0(b) \times (1 - P_1(c) \times P_1(d))$

$P_{on}(\text{NAND}) = \prod P_{on}(\text{block } i)$   
 $P_{on} = (1 - P_0(a) \times P_0(b)) \times P_1(c) \times P_1(d)$

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 5

### Signal Probabilities in AOI gates Example

(See Q6 of Exam April 2011)

$Y = \overline{(b+c) \times a} + d$

**Solution**

$P_{off}((b+c) \times a + d) = 0.0824$

$P_{off}((b+c) \times a) = 0.412$

$P_{off}(b+c) = 0.16$

$P_{off} = 0.4$  (for b),  $P_{off} = 0.4$  (for c)

$P_0 = 0.2$  (for d)

$P_0 = 0.3$  (for a)

$P_{off}(\text{pulldown}) = 0.0824 \Rightarrow P_0(Y) = 0.9176$

TU/EE ET4293 digic - 1112 - © NvdM - 04 Combinational - supplement 12/04/12 6

### From Signal Probability to Transition Probability

Example: Static 2-input NAND gate

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Assume **signal probabilities**

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then **transition probability**

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 1/4 \times 3/4 = 3/16$$


If inputs switch every cycle

$$\alpha_{NAND} = 3/16 \quad \alpha_{NAND} = p_A p_B (1 - p_A p_B)$$

NOR gate yields similar result
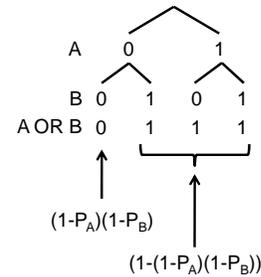
### Transition Probabilities

Activity for static CMOS gates:  $\alpha = p_0 p_1$



### Transition Probabilities for Basic Gates

As a function of the input probabilities


	$p_{0 \rightarrow 1}$
AND	$(1 - p_A p_B) p_A p_B$
OR	$(1 - p_A)(1 - p_B)(1 - (1 - p_A)(1 - p_B))$
XOR	$(1 - (p_A + p_B - 2p_A p_B))(p_A + p_B - 2p_A p_B)$

Activity for static CMOS gates:  $\alpha = p_0 p_1$

Because of symmetry: AND  $\leftrightarrow$  NAND, OR  $\leftrightarrow$  NOR
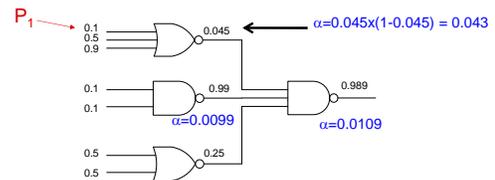
### Activity Factors

Transition probabilities from signal probabilities




However, calculation becomes far more involved upon:

Reconvergent fanout

Feedback and temporal/spatial correlations
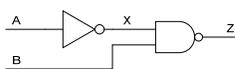
### Reconvergent Fanout (Spatial Correlation)


Inputs to gate can be interdependent (correlated)



no reconvergence

$$P_Z = 1 - (1 - P_A)P_B$$

$P_Z$ : probability that Z=1

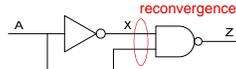

reconvergent

$$P_Z = 1 - (1 - P_A)P_A?$$

NO!

$$P_Z = 1$$

Must use conditional probabilities


$$P_Z = 1 - P_A \cdot P(X|A) = 1$$

probability that X=1 given that A=1

Becomes complex and intractable real fast
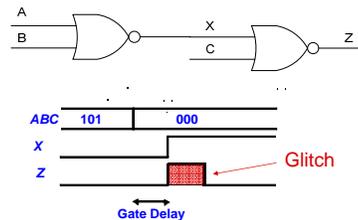
### Glitching in Static CMOS

Analysis so far did not include timing effects



The result is correct, but extra power is dissipated

Also known as dynamic hazards:

"A single input change causing multiple changes in the output"

