

Lab/Exercises Instructions

Assignment 1: Spectre

Use Spectre for Rabaey Exercises 3.4 and 3.5

- Spectre information/how to on course web site
- There are other ways to run Spectre, do as you see fit ...
- Better to use Spectre than other simulator (Spice, ADS, ...) which you may feel more familiar with – you need to learn Spectre anyway
- Hand-in 1 A4 with 4 annotated graphs on Thu 21/2 before class
- Write you names (as a team) on it

- **Due date: Thu Feb 21**
- Will not be graded, but will be checked. Need to pass
- We will provide feedback if necessary

Assignment 2: Virtuoso

Virtuoso Layout Design and Schematic Driven Layout

- Draw a PMOS transistor using Virtuoso
- Make sure it is DRC correct using Calibre
- See layout design rules (ppt/pdf on web)
- Design an inverter using Schematic Composer and Spectre Simulation
- Design Layout using Virtuoso Analog Design Environment (Schematic Driven Layout)

- Hand-out with extensive instructions is on course website

- **Due date: Mon Feb 25**
- Not to be graded, but will be checked. Need to pass
- We will provide feedback if necessary

Assignments need to be Checked

- You need to complete the assignments
- No grading – just pass/fail
- a serious attempt counts as pass, not needed to have everything exactly correct and optimal (but it can give you satisfaction)
- A non-serious attempt requires improvement
- We will try to give feedback, so that you know what is OK and what needs improvement
- Hand in to TA's when you are done 😊
- Ask TA's when you are stuck 😞

TA Help

- **Lucho Gutierrez (TA),
Yuxin Yan (TA),
Venkat Krishnaswami (PhD)
Availability: see BB contact information**
- **Might also come to lab in rush hours**
- **BB Forum** – me and TA's will answer questions

Logistics

- Prepare yourself, form **pairs**
- **Register pairs on BB -> groups -> sign up form**
- Become familiar with linux, cadence
- **Can only use computers in MSc lab Room LH 0.530**
(ground floor of EWI low building, the long corridor)
- **Instructions are posted on web, being augmented through the course**
- **Login using netid**
- **Door lock: see BB**
- **Use time slot registration sheets**
- **Odd/Even groups have priority on alternating days**

- **Next: example of Spectre way of working for exercise Rabaey 3.11**

Rabaey Exercise 3.11

11. [M, SPICE, 3.3.2] Problem 11 uses the MOS circuit of Figure 0.7.
- Plot V_{out} vs. V_{in} with V_{in} varying from 0 to 2.5 volts (use steps of 0.5V). $V_{DD} = 2.5$ V.
 - Repeat *a* using SPICE.
 - Repeat *a* and *b* using a MOS transistor with $(W/L) = 4/1$. Is the discrepancy between manual and computer analysis larger or smaller. Explain why.


 


Figure 0.7 MOS circuit.

Simulation Example

- Make sketch
- Assign node names
- Write file
- Add control statements

 

Exercise 3.11

```
simulator lang=spectre
include "g25_scs.lib"
vdd (vdd 0) vsource dc=2.5
vin (in 0) vsource dc=2.5
r1 (vdd out_long) resistor r=8K
r2 (vdd out_short) resistor r=8k
m1 (out_long in 0 0) nmos l=0.5u w=2u      <- model doesn't allow l=1
m2 (out_short in 0 0) nmos l=0.25u w=1u
Inputsweep dc param=dc dev=vin start=0 stop=2.5 step=0.1
save vin out_long out_short
```

250nm Spectre BSIM3 MOS Models

```
simulator lang=spectre
model nmos bsim3v3
+version=3.1
+type=n
+tnom      = 25          xl      = 3e-8
+xw        = 0          tox      = 5.8e-9
+xj        = 1e-07      nch     = 2.354946e+17  lln    = 1
+vth0      = 0.4321336  lvth1  = 2.081814e-08  wvth0  = -5.470342e-11
+pvth0     = -6.721795e-16  k1     = 0.3281252    lk1     = 9.238362e-08
... 60 lines deleted ...
+tlevev    = 1          tlevec  = 1          js     = 1e-06
+jsw       = 5e-11
```

- Similar for **pmos** device

Spectre Terminal Interface

```
nick@charon:/users/nick/spice/3_11_scs
[nick@charon:~/spice/3_11_scs]
[nick@charon:~/spice/3_11_scs]
[nick@charon:~/spice/3_11_scs] spectre 3_11.scs
spectre (ver. 5.10.41_USR2.052705 -- 27 May 2005).
Includes RSA BSAFE(R) Cryptographic or Security Protocol Software from
  RSA Security, Inc.


Simulating `3_11.scs' on charon at 10:02:46 PM, Sun Feb 10, 2008.

Circuit inventory:
  nodes 4
  equations 12
  iprobe 1
  bsim3v3 2
  resistor 2
  vsource 2


*****
DC Analysis `Inputsweep': vin:dc = (0 V -> 2.5 V)
*****
Important parameter values:
  reltol = 1e-03
  abstol(I) = 1 pA
  abstol(V) = 1 uV
  temp = 27 C
  tnom = 27 C
  tempeffects = all
  gmin = 1 pS
  maxrsd = 0 Ohm
  mos_method = s
  mos_vres = 50 mV
.....9.....8.....7.....6.....5.....4.....3.....2.....1.....0
Total time required for dc analysis `Inputsweep' was 160 ms.

Aggregate audit (10:02:47 PM, Sun Feb 10, 2008):
Time used: CPU = 127 ms, elapsed = 1 s, util. = 12.7%.
Virtual memory used = 1.55 Mbytes.
spectre completes with 0 errors, 0 warnings, and 0 notices.
[nick@charon:~/spice/3_11_scs] wavescan -datadir 3_11.raw █
```

WaveScan Results Browser

 

WaveScan Graph Window

 

Exercise 3.4+3.5

4. [E, SPICE, 3.3.2] Using SPICE plot the I - V characteristics for the following devices.

 


Figure 0.3 NMOS and PMOS devices.

- NMOS $W = 1.2\mu\text{m}$, $L = 0.25\mu\text{m}$
 - NMOS $W = 4.8\mu\text{m}$, $L = 0.5\mu\text{m}$
 - PMOS $W = 1.2\mu\text{m}$, $L = 0.25\mu\text{m}$
 - PMOS $W = 4.8\mu\text{m}$, $L = 0.5\mu\text{m}$
5. [E, SPICE, 3.3.2] Indicate on the plots from problem 4.
- the regions of operation.
 - the effects of channel length modulation.
 - Which of the devices are in velocity saturation? Explain how this can be observed on the I - V plots.

Tips for Ex 3.4, 3.5

- Make 4 circuits, 1 for each of the cases 4a-4b
- Each circuit will have 6 transistors
 - All drains are connected, drain voltage to be swept from 0 to 2.5 V
 - All gates unconnected, different gate voltages: 0, 0.5, 1.0, 1.5, 2.0, 2.5 V
- **Alternatively**, use **parameter sweeping** instead of different layouts
- Plot each circuit in a separate graph, combine them on 1 page (word or latex)
 - Wavescan can **export png files**, looks better compared to screen dumps