

CMOS INVERTER

Course Material for Inverter

Chapter 5, 2nd ed.


P = primair, I = Illustratie, O = overslaan

P	5.1	Introduction	180
P	5.2	The Static CMOS inverter - intuitive	181 – 184
P	1.3.2	Functionality and Robustness	18 – 27
P	5.3	Evaluating the Robustness ...	184 – 191
I	5.3.3	Robustness Revisited	191 – 193
P	1.3.3	Performance	27 – 30
I	5.4	Performance of the CMOS inverter	193 – 213
P	1.3.4	Power and Energy Consumption	30 – 31
I	5.5	Power, Energy, and Energy-Delay	213 – 223
O	5.5.2	Static Consumption	223 – 225
O	5.5.3	Putting it All Together	225 – 227
O	5.5.4	Analyzing Power Consumption using SPICE	227 – 229.
O	5.6	Perspective: Technology scaling...	229 – 231
P	5.7	Summary	232 – 233


The CMOS Inverter - Outline

- **First Glance**
- **Digital Gate Characterization**
- **Static Behavior (Robustness)**
 - **VTC**
 - **Switching Threshold**
 - **Noise Margins**
- **Dynamic Behavior (Performance)**
 - **Capacitances**
 - **Delay**
- **Power**
 - **Dynamic Power, Static Power, Metrics**


The CMOS Inverter: A First Glance

 

CMOS Inverters (1)

 

CMOS Inverter Operation Principle

 


$$V_{OH} = V_{DD} \quad V_{OL} = 0$$




Digital Gate Fundamental Parameters

- **Functionality**
- **Reliability, Robustness**
- **Area**
- **Performance**
 - **Speed (delay)**
 - **Power Consumption**
 - **Energy**

The Ideal Inverter

 


Static CMOS Properties

 

Basic inverter belongs to class of **static circuits**: output always connected to either V_{DD} or V_{SS} . **Not ideal but:**

 - Rail to rail voltage swing
- Ratio less design
- Low output impedance
- Extremely high input impedance
- No static power dissipation
- Good noise properties/margins




Exercise: prioritize the list above

Voltage Transfer Characteristic (VTC)



Load Line (Ckt Theory)

 

Exercise:

The **blue** load line A corresponds to $R =$

The **orange** load line B corresponds to $R =$

With load line A and $V_{GS} = 1V$, $V_{out} =$

Draw a graph $V_{out}(V_{in})$ for load line A and B

PMOS Load Lines



Goal: Combine I_{Dn} and I_{Dp} in one graph

Kirchoff:

$$V_{in} = V_{DD} + V_{GSp}$$

$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DSp}$$

  


Example: $V_{DD}=5V$

$$V_{in} = V_{DD} + V_{GSp}$$



$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DSp}$$

CMOS Inverter Load Characteristics

 


CMOS Inverter VTC

  

NMOS Operating Conditions

 Need to know for proper dimensioning, analysis of noise margin, etc.



NMOS


1 $V_{in} = V_{GS} < V_{Tn} \Rightarrow$ **off**

2 $V_{out} > V_{in} - V_{Tn}$
 $V_{DS} > V_{GS} - V_{Tn}$
 $V_{GD} < V_{Tn} \Rightarrow$ **saturation**

3 $V_{out} < V_{in} - V_{Tn} \Rightarrow$ **resistive**

PMOS Operating Conditions

 Need to know for proper dimensioning, analysis of noise margin, etc.



PMOS


4 $V_{in} > V_{DD} + V_{Tp} \Rightarrow$ **off**

5 $V_{out} < V_{in} - V_{Tp} \Rightarrow$ **saturation**

6 $V_{out} > V_{in} - V_{Tp} \Rightarrow$ **resistive**


Exercise: check results for PMOS

Operating Conditions

 

**NMOS 1 off
2 saturation
3 resistive**

**PMOS 4 off
5 saturation
6 resistive**


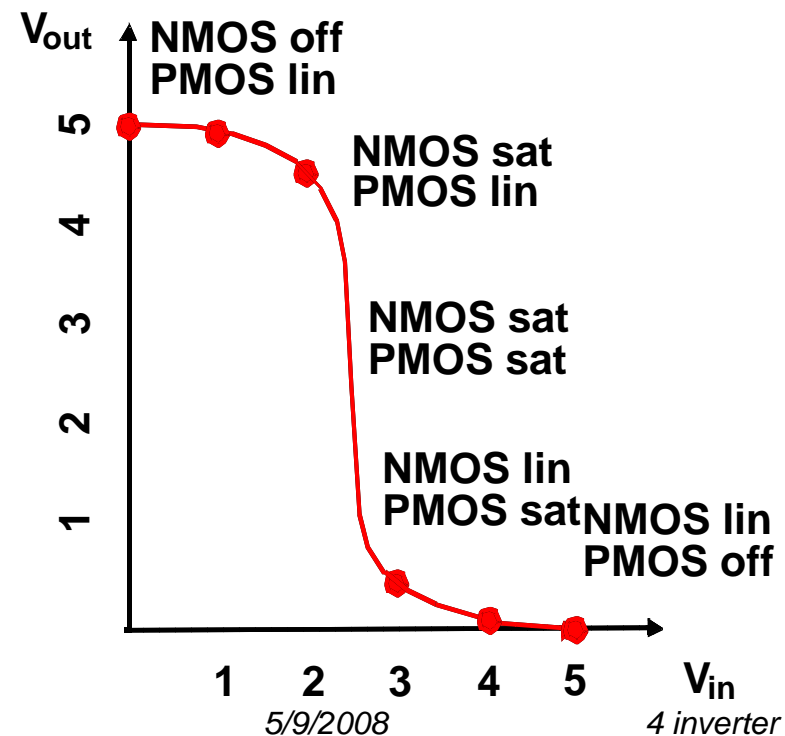


Inverter Static Behavior


- Regeneration
- Noise margins
- Delay metrics




The Realistic Inverter

  

The Regenerative Property

 


A chain of inverters

 


■ **Regenerative Property:** ability to regenerate (repair) a weak signal in a chain of gates


The regenerative property

 


The Regenerative Property (2)

 

(a) A chain of inverters.

 


(b) Regenerative gate

 

(c) Non-regenerative gate

The regenerative Property (3)

 


Exercise: what is the output voltage of a chain of 4 inverters with a piece-wise linear VTC passing through (0, 10), (4,8), (6,2) and (10,0) [Volt], as the result of an input voltage of 5.5 [Volt].

 Exercise: discuss the behavior for an input of 5 [Volt]


Inverter Switching Threshold

- Not the device threshold $V_m = f(R_{onn}, R_{onp})$
- Point of $V_{in} = V_{out}$




- Try to set W_n, L_n, W_p, L_p so that VTC is symmetric as this will improve noise margins

optimize NMOS-PMOS ratio

 

Simulated Gate Switching Threshold

 

Electrical Design Rule

$$W_p \approx 2.5 W_n$$

- Assumes $L_p = L_n$
- Should be applied consistently

■ Symmetrical VTC $\Rightarrow V_m \approx \frac{1}{2} V_{DD} \Rightarrow W_p/W_n \approx$


■ In practice: choose somewhat smaller value of W_p/W_n

■ Why?

Inverter Switching Threshold

Analytical Derivation

 - V_M is V_{in} such that $V_{in} = V_{out}$
- $V_{DS} = V_{GS} \Leftrightarrow V_{GD} = 0 \Rightarrow$ saturation
 - Assume $V_{DSAT} < V_M - V_T$
(velocity saturation)
 - Ignore channel length modulation
- V_M follows from
 - $I_{DSATn}(V_M) = -I_{DSATp}(V_M)$



Inverter Switching Threshold

Analytical Derivation (ctd)

$$I_{DSATn}(V_M) = -I_{DSATp}(V_M)$$

$$I_D = kV_{DSAT}(V_{GS} - V_T - V_{DSAT}/2)$$

$$\Leftrightarrow k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2) = -k_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)$$


$$\Leftrightarrow \frac{k_p}{k_n} = \frac{-V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \quad k = \frac{W}{L} k'$$

$$\Rightarrow \frac{(W/L)_p}{(W/L)_n} = \left| \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \right|$$

- See Example 5.1:
- $(W/L)_p = 3.5 (W/L)_n$ for typical conditions and $V_M = \frac{1}{2} V_{DD}$
- Usually: $L_n = L_p$

Gate Switching Threshold w/o Velocity Saturation

 
- Long channel approximation
- Applicable with low V_{DD}




Exercise (Problem 5.1):
derive V_M for long-
channel approximation
as shown below

$$V_M = \frac{r(V_{DD} - V_{Tp} + V_{Tn})}{1+r} \text{ with } r = \sqrt{\frac{-k_p}{k_n}}$$


Noise in Digital Integrated Circuits

 

(a) Inductive coupling

 


(b) Capacitive coupling

 

(c) Power and ground noise



- Study behavior of static CMOS Gates with **noisy signals**

Noise Margins

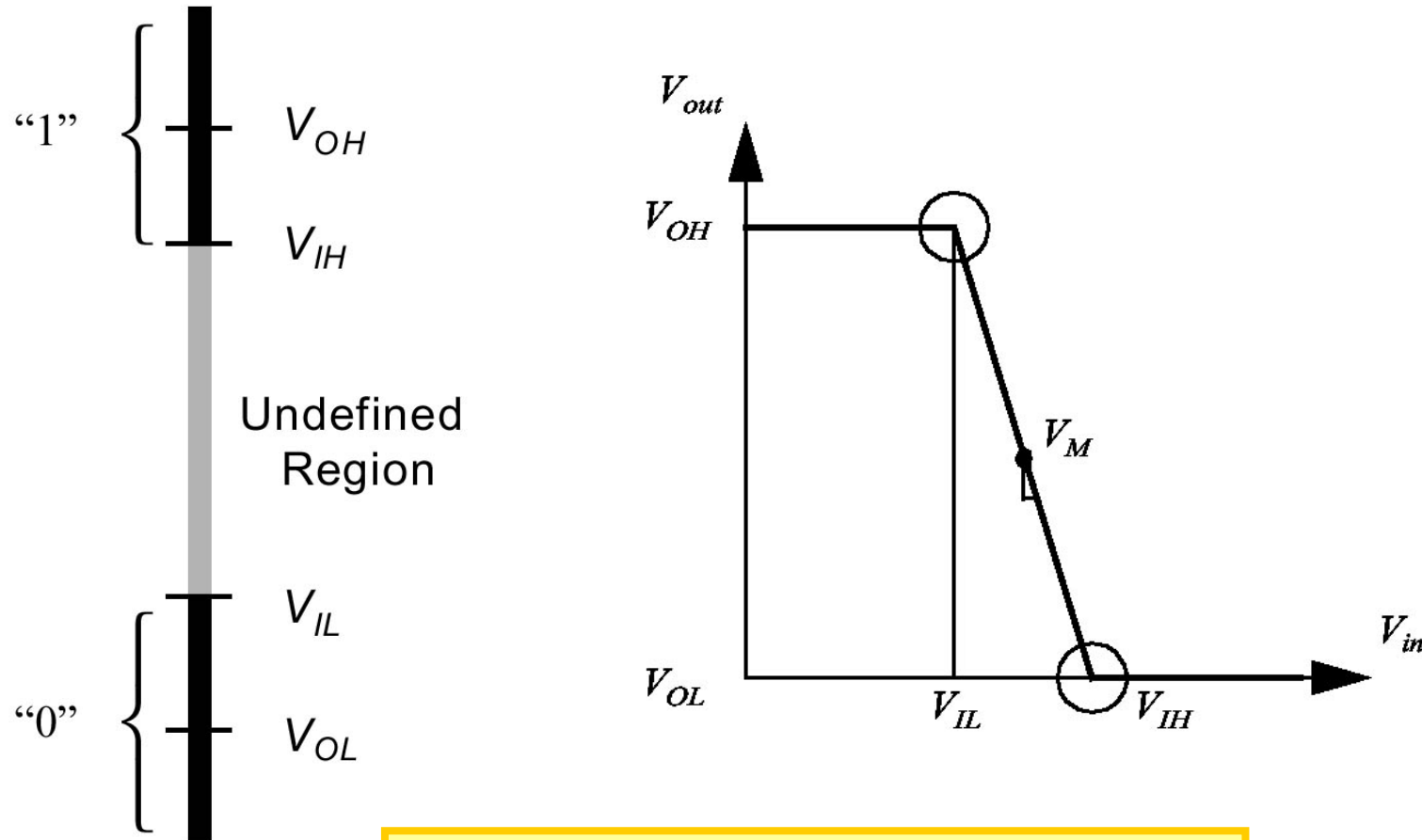

- V_{OL} = Output Low Voltage
- V_{IL} = Input Low Voltage
- $V_{OH}, V_{IH} = \dots$


Noise Margins

  

■ $NM_H = V_{OH} - V_{IH} = \text{High Noise Margin}$


■ $NM_L = V_{IL} - V_{OL} = \text{Low Noise Margin}$

Noise Margin for Realistic Gates

 

Exercise: explain significance of slope = -1 for noise margin

Noise Margin Calculation

 

Piece-wise linear approximation of VTC

g = gain factor (slope of VTC)

We know how to compute V_M
Next: how to compute g

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g}$$

$$V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL}$$



Noise Margin Calculation (2)

- Approximate g as the slope in V_{out} vs. V_{in} at $V_{in} = V_M$

$$k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn} / 2)(1 + \lambda_n V_{out}) +$$

$$k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp} / 2)(1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$

$$g = \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} \approx \frac{1+r}{(V_M - V_T - V_{DSATp} / 2)(\lambda_n - \lambda_p)} \quad r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

- Mostly determined by technology
- See example 5.2

- **Exercise:** verify calculation
- **Exercise:** explain why we add channel length modulation to the I_D expressions (we did not do this to determine V_M)


Dynamic Behavior (Performance)

- Capacitances
- Delay

- But: we take much simpler model for capacitances compared to book.
- See the syllabus.
- § 5.4.1 of book is only illustration.




CMOS Inverters

 

- What causes the delay?
- What is R_{on} ?
- Where are the capacitances?
- Which capacitances determine T_p ?

Delay Definitions

 


$$t_p = \frac{1}{2}(t_{pHL} + t_{pLH})$$



§ 1.3.3






t_p : property of gate
 t_r, t_f : property of signal

CMOS Inverter Rise/Fall Delay

 






- **Goal: determine t_f , t_r and t_p**
- **First: compute relevant capacitances**
- **Second: determine equivalent R_{on}**
- **Third: compute RC delay (τ) and scale result**
- **Assume: ideal source, step input**

Modeling

     

From module 1- devices

Modeling (2)

     


$$R = R_{on1}$$

$$C = C_{D1} + C_{D2} + C_{G3} + C_{G4}$$



$$V_S = 0$$

Modeling (3)

 

- Delay can be modeled using RC circuit
 - First order simplified model
- R is (linearized) on-resistance of active transistor
- C is sum of (linearized) C 's that are switched
 - Typically, C_G of driven gate, C_D of driving gate
 - Plus relevant interconnect C
 - Might need to include interconnect R in model
- V_s is final voltage of delay node (initial voltage determined by previous state)

RC Delay Review (1)

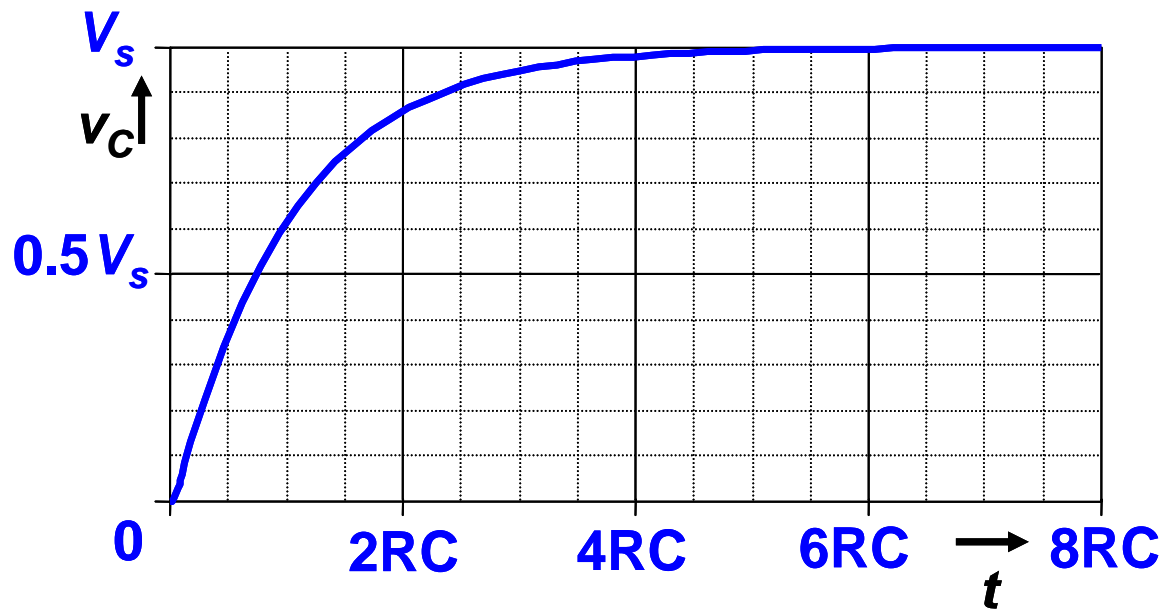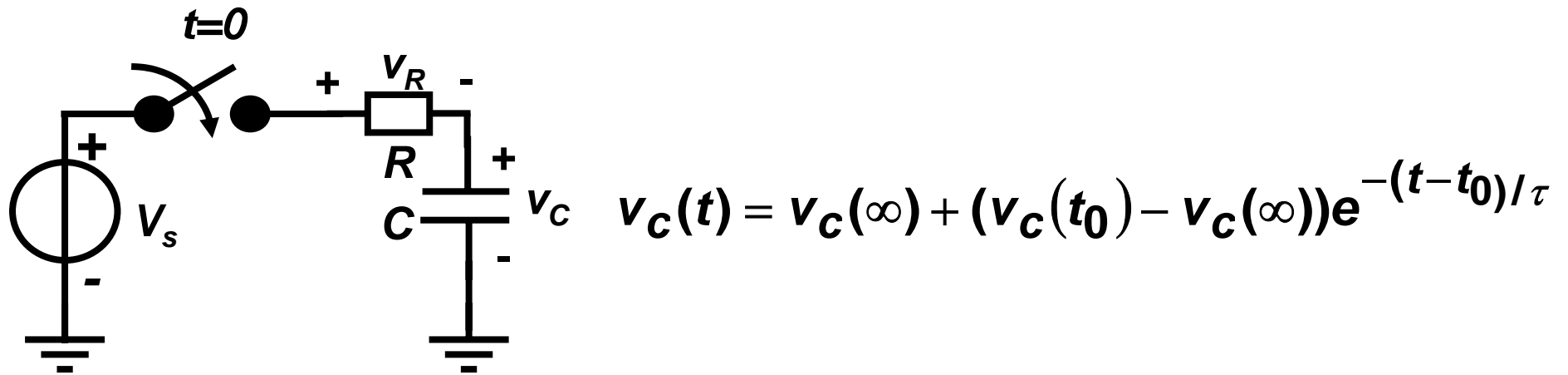

$$RC \frac{dv_C}{dt} = V_s - v_C$$

$$v_C = V_s \left(1 - e^{-\frac{t}{RC}} \right)$$


RC Delay Review (2)

- Response can be **normalized** with respect to $\tau=RC$ and $V_s = v_c(t = \infty)$

$$v_c = V_s(1 - e^{-\frac{t}{RC}})$$

$$\frac{v_c}{V_s} = (1 - e^{-t/\tau})$$


Example: $(1 - e^{-2}) = 0.86$

 

Each τ -step gives **63%** of remaining swing

swing	time
0–50%	0.69τ
0–63%	1.0τ
10%–90%	2.2τ
0–90%	2.3τ

Inverter Propagation Delay Summary

 


$$t_{pHL} = 0.69R_{eqn}C_L$$

$$t_{pLH} = 0.69R_{eqp}C_L$$

$$t_p = \frac{1}{2}(t_{pHL} + t_{pLH}) \quad \text{Propagation time}$$


Propagation Delay w. Wire Resistance

 


$$t_{PHL} = 0.69R_{eqn}(C_{out} + 0.5C_W) \\ + 0.69(R_{eqn} + R_W)(0.5C_W + C_{in})$$

■ See module 3, interconnect

Equivalent R_{on} (R_{eq})

 

(a) Schematic

 


(b) trajectory traversed on ID-VDS curve.

$$R_{eq} = \frac{1}{2} \left[\frac{V_{DD}}{I_{DSAT} (1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} (1 + \lambda V_{DD}/2)} \right]$$

$$\approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

See 3-devices, example 3.8

Impact of Rise Time on Delay

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

**Empirical from
the first edition of
book**

Delay as a function of V_{DD}


 
 


Fig.5.17

CMOS Inverter Propagation Delay

Alternative current-based estimate for T_p , assuming velocity saturation
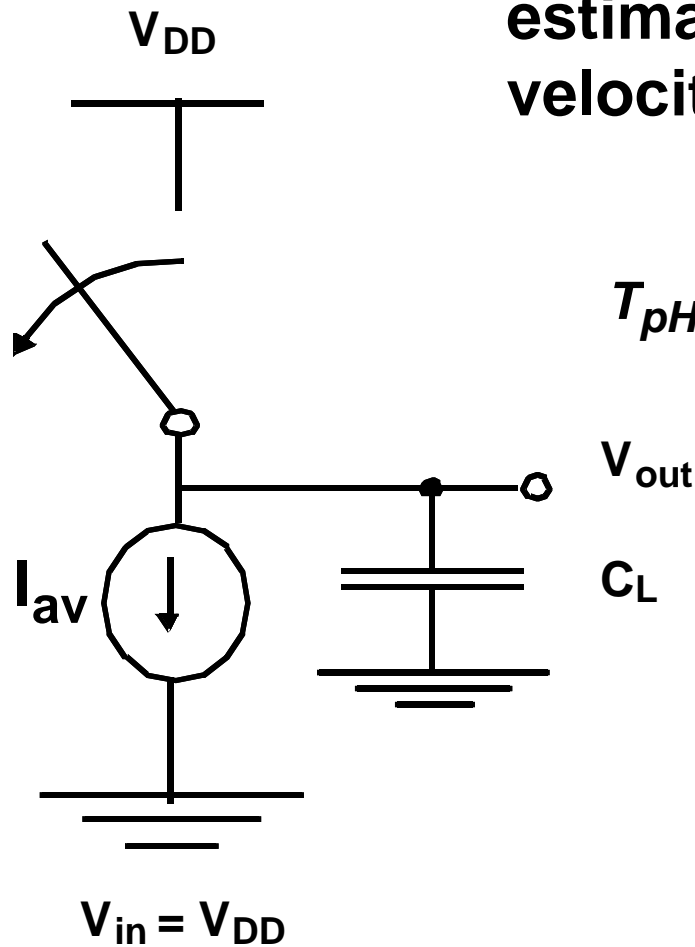
$$T_{pHL} = \frac{C_L \frac{V_{swing}}{2}}{I_{av}} \approx \frac{C_L V_{DD}}{2I_{DSAT}(1 + \frac{3}{4}\lambda V_{DD})}$$





Exercise (Problem 5.4): Derive the expression above

Ring Oscillator

Frequently used to obtain T_p by measurement (or simulation)

  N : number of inverters
 T_p : propagation delay
 T : period of oscillation





§ 1.3.3

$$T = 2 \times T_p \times N \Leftrightarrow T_p = T/2N$$

Exercise: explain the factor 2 in the expression above

Fan-in and Fan-out

 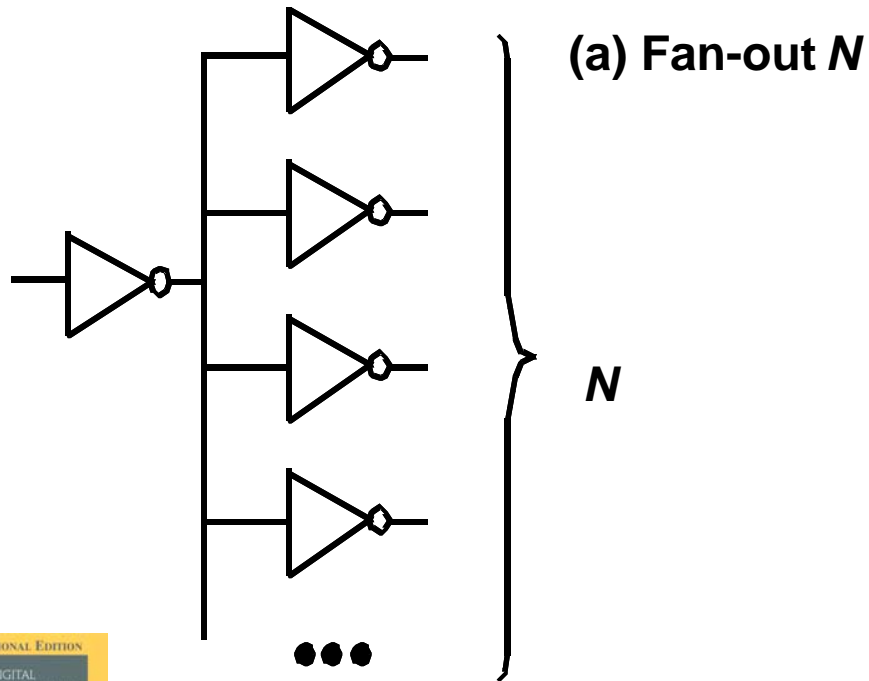

Power (§ 5.5)

- Dynamic Power
- Static Power
- Metrics

CMOS Power Dissipation

- Power dissipation is a **very important** circuit characteristic
- CMOS has relatively low static dissipation
- Power dissipation was the reason that CMOS technology won over bipolar and NMOS technology for digital IC's
- (Extremely) high clock frequencies increase dynamic dissipation
- Low V_T increase leakage
- Advanced IC design is a continuous struggle to contain the power requirements!



Power Density



Estimate

- Furnace: 2000 Watt, $r=10\text{cm}$ → $P \approx 6\text{Watt/cm}^2$
- Processor chip: 100 Watt, 3cm^2 → $P \approx 33\text{Watt/cm}^2$

Power-aware design, design for low power, is blossoming subfield of VLSI Design

Where Does Power Go in CMOS

- **Dynamic Power Consumption**
 - Charging and discharging capacitors
- **Short Circuit Currents**
 - Short circuit path between supply rails during switching
- **Leakage**
 - Leaking diodes and transistors
 - May be important for battery-operated equipment

Dynamic Power


Dynamic Power

- E_i = energy of switching event i
 - (to first order) independent of switching speed
 - depends on process, layout
- Power = Energy/Time

$$P = \frac{1}{T} \sum_i E_i$$

- E_i = Power-Delay-Product P-D
 - important quality measure
- Energy-Delay-Product E-D
 - combines power*speed performance

Low-to-High Transition Energy

 


Equivalent circuit for **low-to-high** transition

E_C - Energy stored on C

$$\begin{aligned} E_C &= \int_0^{\infty} i v_0 dt & v_0 &= v_0(t) & i &= i(t) = C \frac{dv_0}{dt} \\ &= \int_0^{\infty} C v_0 \frac{dv_0}{dt} dt \\ &= \int_0^{V_{DD}} C v_0 dv_0 = \frac{1}{2} C v_0^2 \Big|_0^{V_{DD}} = \frac{1}{2} C V_{DD}^2 \end{aligned}$$

Low-to-High Transition Energy

 

$E_{V_{DD}}$ Energy delivered by supply


$$E_{V_{DD}} = \int_0^{\infty} i(t) V_{DD} dt = \int_0^{V_{DD}} C V_{DD} \frac{dv_0}{dt} dt = C V_{DD}^2$$

$$E_{V_{DD}} = C V_{DD}^2 \quad E_C = \frac{1}{2} C V_{DD}^2$$

Where is the rest?



Low-to-High Transition Energy

 


E_{diss} Energy dissipated in transistor

$$\begin{aligned} E_{diss} &= \int_0^{\infty} i(V_{DD} - v_0) dt \\ &= \int_0^{\infty} iV_{DD} dt - \int_0^{\infty} iv_0 dt \\ &= E_{V_{DD}} - E_C \end{aligned}$$



High-to-Low Transition Energy

 

Equivalent circuit

Exercise: Show that the energy that is dissipated in the transistor upon discharging C from V_{DD} to 0 equals $E_{\text{diss}} = \frac{1}{2}CV_{DD}^2$

CMOS Dynamic Power Dissipation

$$\mathbf{Energy = E_{charge} + E_{discharge}}$$

$$\mathbf{Power = \frac{Energy}{Time} = \frac{Energy}{transition} \times \frac{\#transitions}{time}}$$
$$\mathbf{= CV_{DD}^2 \times f}$$

- Independent of transistor on-resistances
- Can only reduce C , V_{DD} or f to reduce power
- In this formula, f accounts for switching activity (not necessarily a simple regular waveform)

Summary

- **First Glance**
- **Digital Gate Characterization (§ 1.3)**
- **Static Behavior (Robustness) (§ 5.3)**
 - **VTC**
 - **Switching Threshold**
 - **Noise Margins**
- **Dynamic Behavior (Performance) (§ 5.4)**
 - **Capacitances**
 - **Delay**
- **Power (§ 5.5)**
 - **Dynamic Power, Static Power, Metrics**