

# ***MODULE 5***

## ***COMBINATIONAL LOGIC***

# Course Material for Combinational

Extra: Slides about how to implement a static combinational gate with NMOS/PMOS transistors, given the Boolean function

P	6.1	Introduction	236
P	6.2	Static CMOS Design	236 – 237
P	6.2.1	Complementary CMOS	237 – 242
I		Propagation Delay of Complementary CMOS gates	242 – 249
I		Design Techniques for large fan-in	249 – 251
O		Optimizing performance in combinational networks	251 – 257
O		Power consumption in CMOS logic gates	257 – 263
P	6.2.2	Ratioed Logic	263 – 267
I		How to build even better loads	267 – 268
P	6.2.3	Pass-transistor basics	269 – 270
I		Example 6.10	271 – 272
O		Diversen	272 – 277
P		Solution 3: Transmission gate logic	277 – 280
I		Rest of § 6.2.3	280 – 284
I	6.3	Dynamic CMOS Design	
I	6.3.1	Dynamic Logic: Basic Principles	284 – 286
I	6.3.2	Speed and Power Dissipation of Dynamic Logic	287 – 290
I	6.3.3	Signal Integrity Issues in Dynamic Design	290 – 295
O	6.3.4	Cascading Dynamic Gates	295 – 303
O	6.4	Perspectives	303 – 306
P	6.5	Summary	306 – 307


# Combinational Logic - Outline

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
  - **Complex Logic Gates**
  - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**
- **Dynamic CMOS gates → only illustration**

# Complementary Static CMOS


## Basic Principles

# Combinational vs. Sequential Logic

 


(a) Combinational

$$\text{Output} = f(\text{In})$$

 

 (b) Sequential

$$\text{Output} = f(\text{In, History})$$



# Reminder

## DeMorgan Transformations



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

# NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a **switch** controlled by its gate signal

  
**NMOS** switch **closes** when switch control input is **high**




# PMOS Transistors in Series/Parallel Connection

**PMOS** switch closes when switch control input is **low**

$Y = X$  if ...

 


$Y = X$  if  $\bar{A}$  and  $\bar{B}$

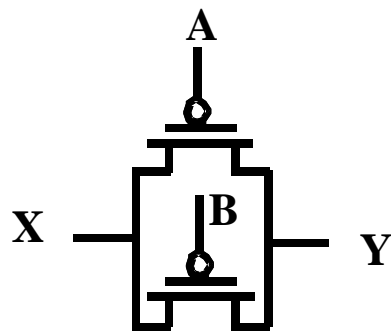

$Y = X$  if  $\bar{A}$  or  $\bar{B}$



# 2-Input Nand

 

$Y = 1$  if  $\bar{A}$  OR  $\bar{B}$

$Y = 1$  if  $\overline{A \text{ AND } B}$

$Y = \overline{A \text{ AND } B}$


$Y = 0$  if  $A \text{ AND } B$

DeMorgan



B	A	Y
0	0	1
0	1	1
1	0	1
1	1	0

# 2-Input Nand



$$Y = \overline{A \text{ AND } B}$$

 

# 2-input Nand/Nor

 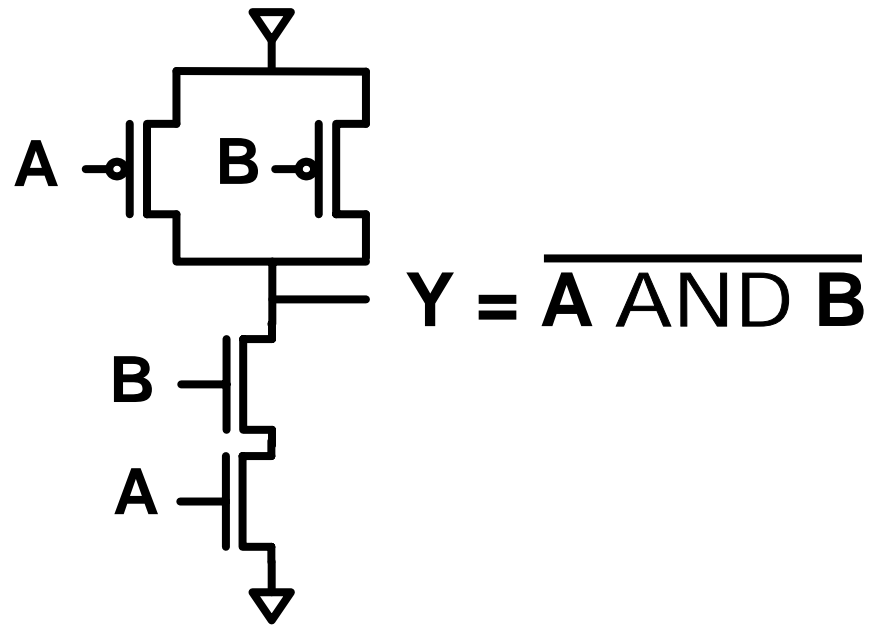


# NMOS vs. PMOS, pull-down vs. pull-up

 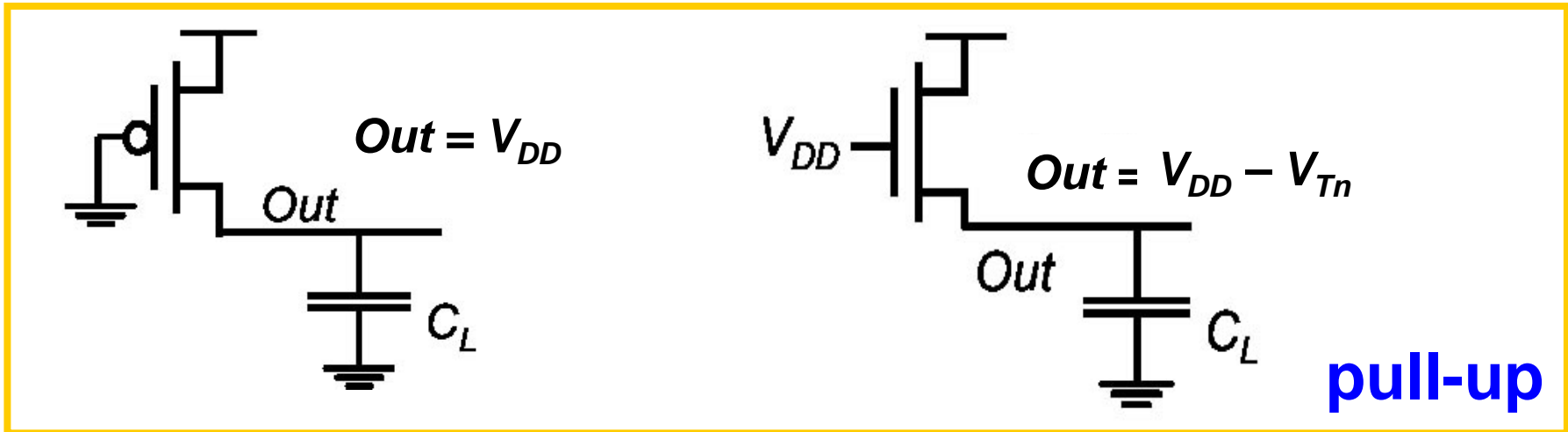

- PMOS is better pull-up
- NMOS is better pull-down

## Bad Idea

 

**Exercise:** Determine logic function

Determine  $V_{out}$   
for  $V_{in} = V_{DD}$  and  $V_{in} = V_{SS}$

**Why is this a bad circuit?**

# CMOS Gate is Inverting

Assume full-swing inputs (high =  $V_{DD}$ , low =  $V_{SS}$ )

- Highest output voltage of NMOS is

$$V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$$

- An 1 on **NMOS** gate can produce a **strong 0** at the drain, but not a strong 1

- Lowest output voltage of PMOS is

$$V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$$

(with  $V_{GS}, V_{Tp} < 0$  for PMOS)

- An 0 on **PMOS** gate can produce a **strong 1** at the drain, but not a strong 0

- **Need NMOS for pull-down, PMOS for pull-up**

A 1 at input can pull-down, 0 at input can pull-up

A 1 can produce a 0, a 0 can produce a 1


**Inverting behavior**

**For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates**

# Complementary static CMOS

- Complex Logic Gates
- VTC, Delay and Sizing

# Complementary Static CMOS

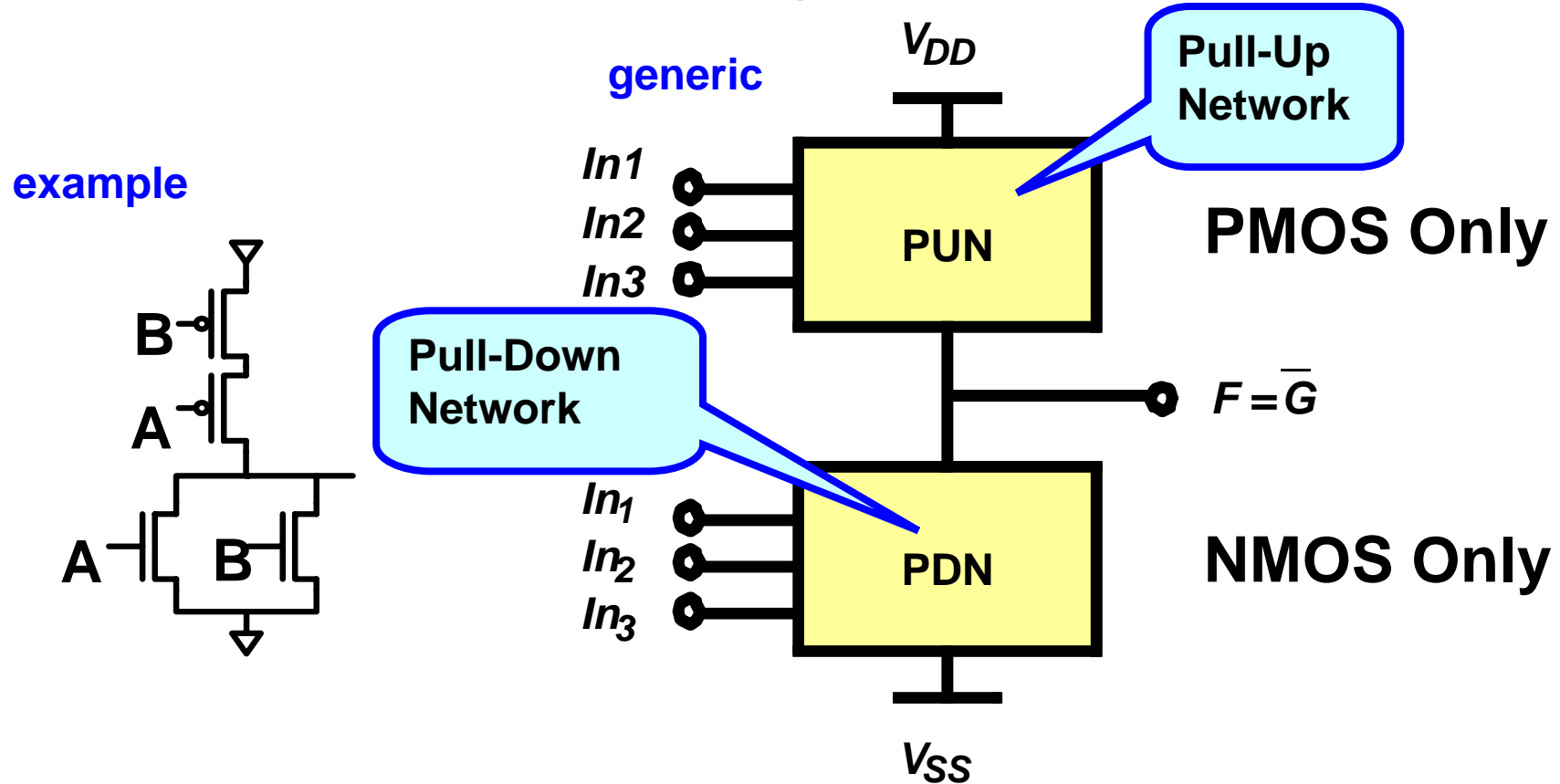


- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**



# Mutual Exclusive PDN and PUN

$$\text{Out} = (AB + C)'$$

 

C	B	A	P D N	P U N	Out
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

PDN Off

PUN On

PUN Off

PDN On

**For all Complementary Static CMOS Gates, either the PUN or the PDN is conducting, but never both.**

# Complementary Static CMOS (2)


- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN
  - series  $\Leftrightarrow$  parallel
  - nmos  $\Leftrightarrow$  pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need  $2N$  transistors for  $N$ -input gate

# Implementation of Combinational Logic

- How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?

 
- Example:  $Y = \overline{(A + BC)}D$

- Remember: only inverting gates available



# Implementation of Combinational Logic

 - Example:  $Y = \overline{(A + BC)D}$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path  $\Rightarrow$  DELAY





# transistors  logic depth

- Q: Can this be improved?
  
# Improved Gate Level Implementation


■ Using DeMorgan  $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



■ Q: Can this be further improved?

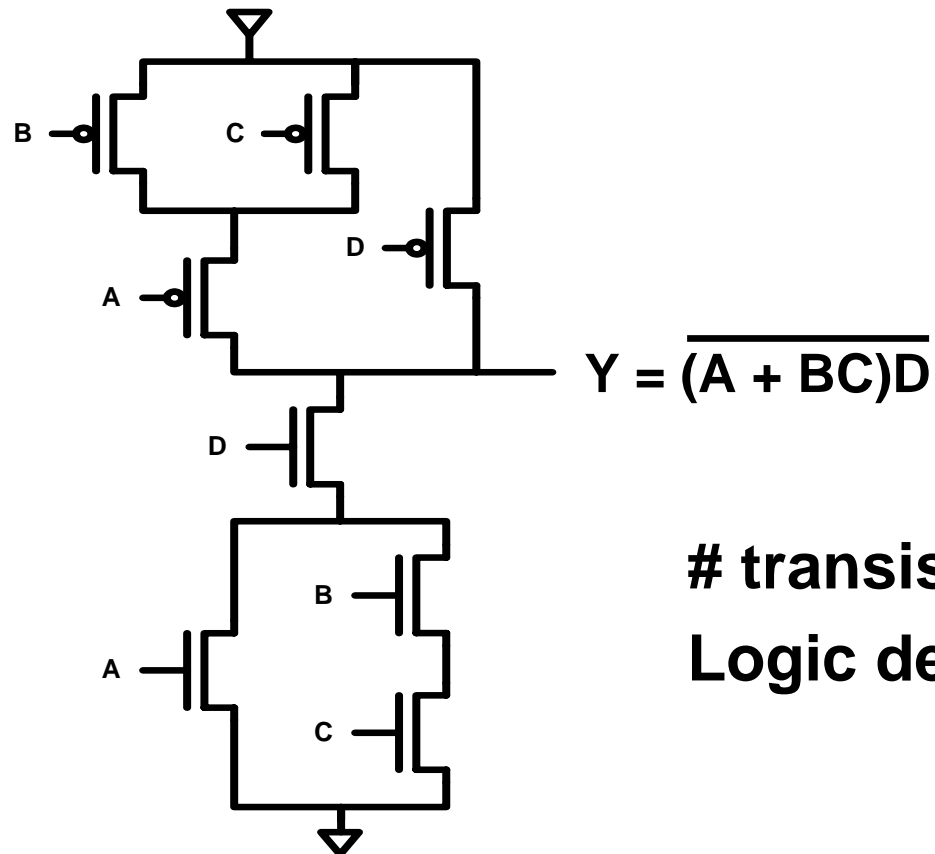
# Complex CMOS Logic Gates

- **Restriction to basic NAND, NOR etc. not necessary**
- **Easy to synthesize complex gates**



# How to Synthesize Complex Gates

$$Y = \overline{(A + BC)D}$$

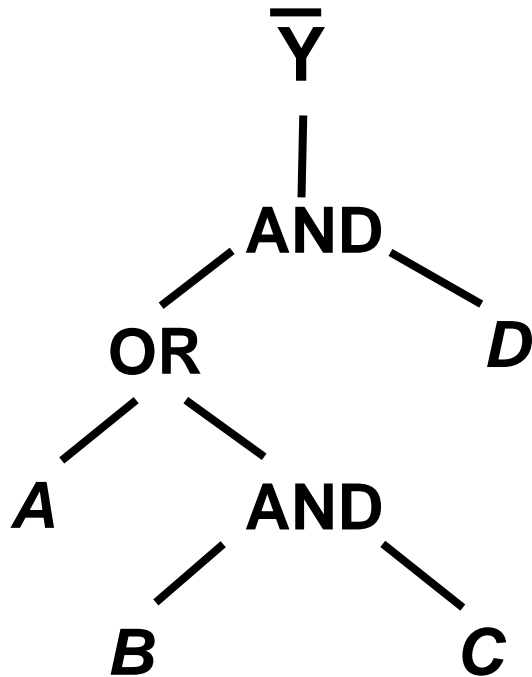


- Using tree representation of Boolean function
- *Operator* with branches for *operands*
- As a **series-parallel** network


	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

# Complex Gate Synthesis Example

$$\bar{Y} = (A + (BC))D$$

 

	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

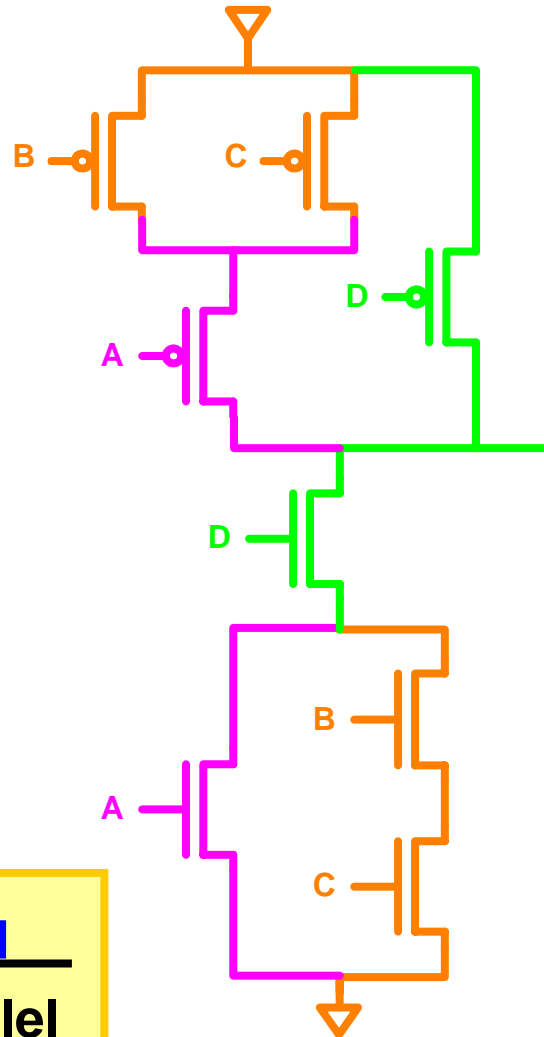


## Recipe

- Write  $\bar{Y} = f(\text{inputs})$
- Decompose  $f$  in tree form
- Realize tree branches according to table at bottom-left
- Use inverted inputs if necessary



# And-Or-Invert Gate

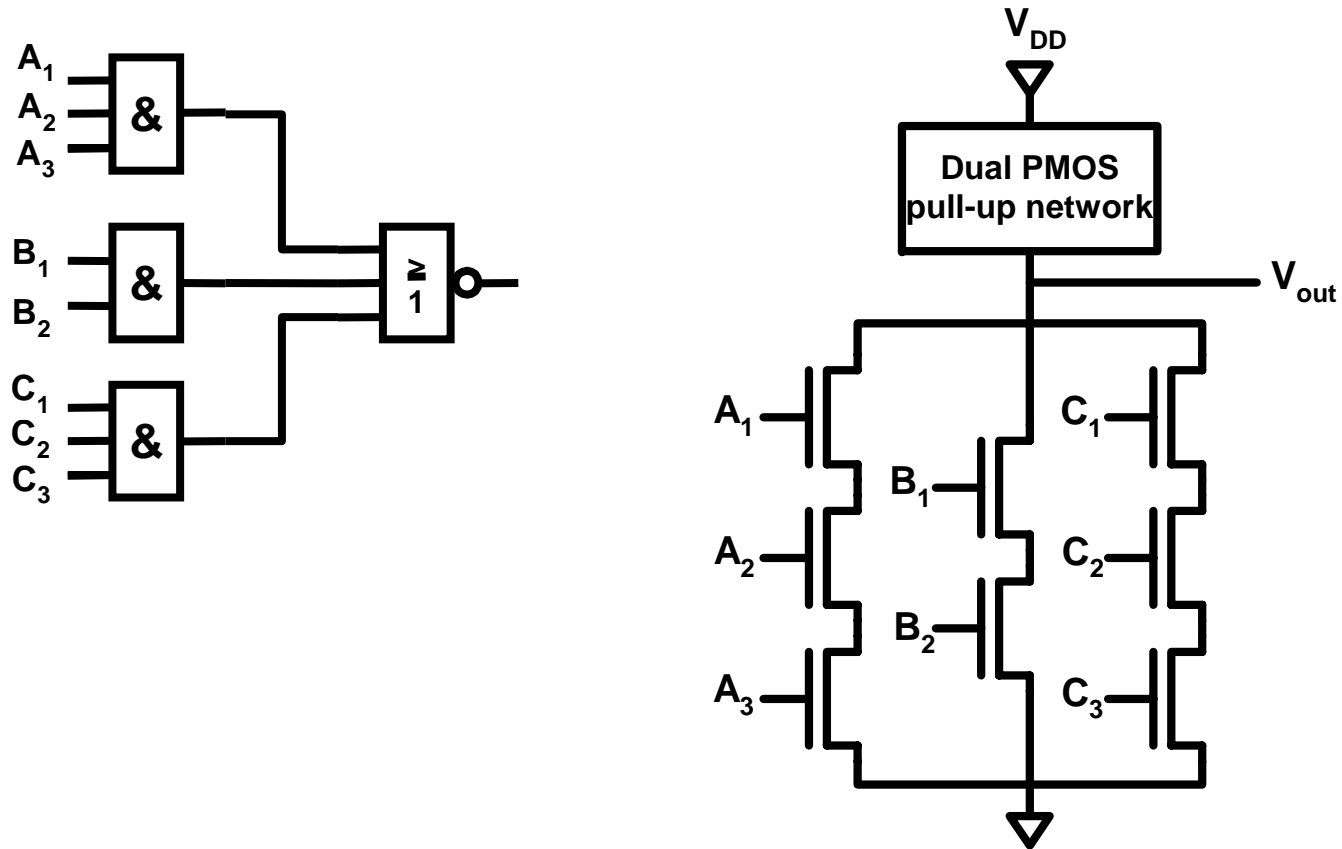

# And-Or-Invert Example


- From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$


$\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

 


$\bar{A}, \bar{B}$  to be created with extra inverters (or by restructuring previous circuits)

# And-Or-Invert Improvement

 

$$Y = \overline{\bar{A}BC + ABC}$$

12 transistors

 


$$Y = \overline{(\bar{A}B + \bar{A}\bar{B})C}$$

10 transistors

2-level logic minimization: see Katz (CS1), § 2.3

# CMOS Complex Gate Sizing


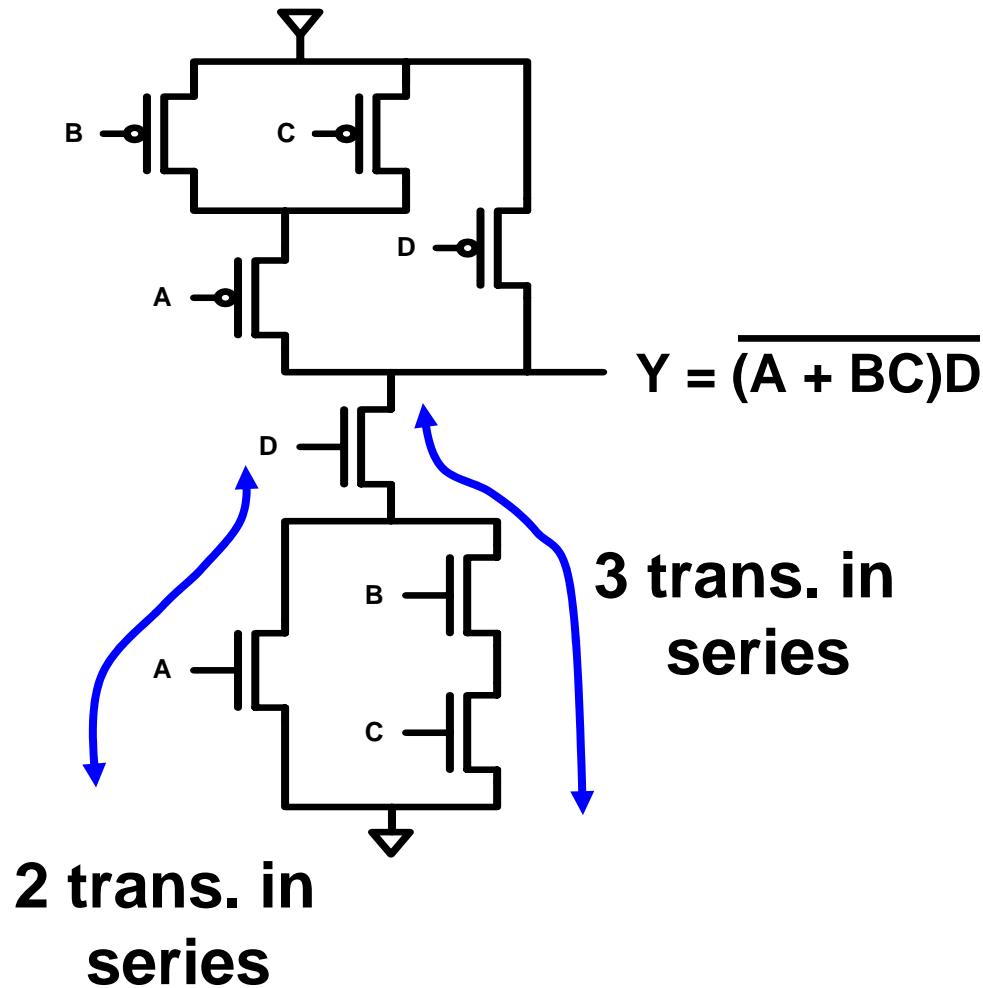


- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

# CMOS Complex Gate Sizing

- Assume all transistors will have minimum length  $L$
- Determine  $W_n$  for PDN transistor of inverter that would give the desired 'drive strength'
- For each transistor in PDN of complex gate do the following:
  - Determine the length  $l$  of the longest PDN chain in which it participates
  - Set  $W = l W_n$
- Repeat this procedure for PUN, using  $W_p$  for PUN transistor of inverter.



# Gate Sizing

  

- **W/L ratios**
- **what are the W/L of 2-input NAND for same drive strength?**

**0-th order calculation**


# Exercise

 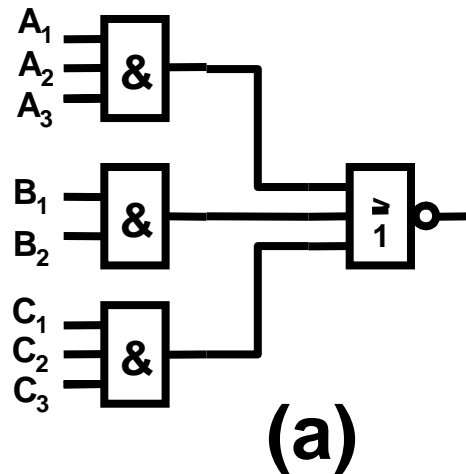

## Exercise:

- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, **assume  $PU/PD = 3$**
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same PU/PD)
- Compare sum of gate areas in (a) and (b). Note: area  $\sim$  width

# Avoid Large Fan-In

 

**C linear** in N

**R linear** in N


**Delay**  $\propto$  **RC quadratic** in N

**Empirical**

**Delay =  $a_1 FI + a_2 FI^2 + a_3 FO$**




# Data-Dependent Timing

 

$$t_{PHL} = 0.69R_N C_L$$

$$t_{PLH} = 0.69R_P C_L$$

 **You** should be able to identify the transistor paths that charge or discharge  $C_L$ , and calculate resulting RC delay model, including effects of wires and fan-out



$$t_{PHL} = 0.69(R_N \times 2)C_L$$

$$t_{PLH} = 0.69R_p C_L$$



$$t_{PLH} = 0.69(R_p/2)C_L$$

**Series** connection

**One input** goes low

**Two inputs** go low,  
**parallel** connection



# Data-dependent VTC: 2nd order effects

  

- Charge at 'int'
- Body effect in  $M_2$
- Short-circuit currents

- Don't need to be able to work with these effects
- But remember: there is more going on than shown by our simple, 1<sup>st</sup> order model

# Data-dependent Timing (2)

 
 


Input Data Pattern	Delay (pS)
$A = B = 0 \rightarrow 1$	69
$A = 1, B = 0 \rightarrow 1$	62
$A = 0 \rightarrow 1, B = 1$	50
$A = B = 1 \rightarrow 0$	35
$A = 1, B = 1 \rightarrow 0$	76
$A = 1 \rightarrow 0, B = 1$	57


**Ratioed logic**

**Pass transistor logic**

# Pseudo NMOS Ratioed Logic

  

 - ☺ Reduced area
- ☺ Reduced capacitances
- ☹ Increased  $V_{OL}$
- ☹ Reduced noise margins
- ☹ Static dissipation



# Ratioed Logic $V_{OL}$ Computation

$$I_{Dn} \text{ (linear)} = I_{Dp} \text{ (saturation)}$$

**Exercise:** verify these assumptions/steps

$$k_n \left( (V_{DD} - V_{Tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left( (-V_{DD} - V_{Tp})V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn})V_{OL} \approx k_p (-V_{DD} - V_{Tp})V_{DSAT}$$


Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} |V_{DSAT}| \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSAT}|$$

# Pass-transistor and Pass-gate circuits

 
# Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (extra inverters)



But remember:

NMOS vs. PMOS, pull-down vs. pull-up

 


- PMOS is better pull-up
- NMOS is better pull-down

TUD/EE ET1205 EC/GS 0506 - © NvdM

09-May-06


5 combinational 12

 


 
# Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (might mean extra inverters)
- Reduced  $V_{OH}$ , noise margins




- $V_{OH} = V_{DD} - \left( V_{Tno} + \gamma \left( \left( \sqrt{|2\phi_f|} + V_{OH} \right) - \sqrt{|2\phi_f|} \right) \right)$
- Static dissipation in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by complementary pass gates (NMOS + PMOS parallel)

**Exercise:** Why is there static dissipation in next conventional gate?
 
# Pass Gates

- Remedy: use an N-MOS and a P-MOS in parallel




- Pass gates **eliminate** some of the **disadvantages** of simple pass-transistors
- But also some of the **advantages**
- Design remains a **trade-off!**

Pass-gate a.k.a. Transmission-gate


 
# Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?


  
# Pass Transistor Logic

- Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$  ( $S'$  is easier notation for S-bar = S-inverse =  $\overline{S}$ )
- $Y = ((AS)' (BS)')'$  allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8) transistors (see also Katz, section 4.2)



# Summary

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
  - **Complex Logic Gates**
  - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**