

MODULE 5

COMBINATIONAL LOGIC

Course Material for Combinational

Extra: Slides about how to implement a static combinational gate with NMOS/PMOS transistors, given the Boolean function


P	6.1	Introduction	236
P	6.2	Static CMOS Design	236 – 237
P	6.2.1	Complementary CMOS	237 – 242
I		Propagation Delay of Complementary CMOS gates	242 – 249
I		Design Techniques for large fan-in	249 – 251
O		Optimizing performance in combinational networks	251 – 257
O		Power consumption in CMOS logic gates	257 – 263
P	6.2.2	Ratioed Logic	263 – 267
I		How to build even better loads	267 – 268
P	6.2.3	Pass-transistor basics	269 – 270
I		Example 6.10	271 – 272
O		Diversen	272 – 277
P		Solution 3: Transmission gate logic	277 – 280
I		Rest of § 6.2.3	280 – 284
I	6.3	Dynamic CMOS Design	
I	6.3.1	Dynamic Logic: Basic Principles	284 – 286
I	6.3.2	Speed and Power Dissipation of Dynamic Logic	287 – 290
I	6.3.3	Signal Integrity Issues in Dynamic Design	290 – 295
O	6.3.4	Cascading Dynamic Gates	295 – 303
O	6.4	Perspectives	303 – 306
P	6.5	Summary	306 – 307

Combinational Logic - Outline

- Conventional Static CMOS basic principles
- Complementary static CMOS
 - Complex Logic Gates
 - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic
- Dynamic CMOS gates → only illustration

Complementary Static CMOS Basic Principles

Combinational vs. Sequential Logic

 

(a) Combinational

(b) Sequential



§ 6.2

Output = f(In)

Output = f(In, History)

Reminder


DeMorgan Transformations

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NMOS Transistors in Series/Parallel Connection

 Transistors can be thought as a **switch** controlled by its gate signal
NMOS switch closes when switch control input is **high**




§ 6.2.1


PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is **low**

$Y = X$ if ...

 


2-Input Nand

 


2-Input Nand


$Y = \bar{A} \text{ AND } \bar{B}$

 

2-input Nand/Nor

 

NMOS vs. PMOS, pull-down vs. pull-up

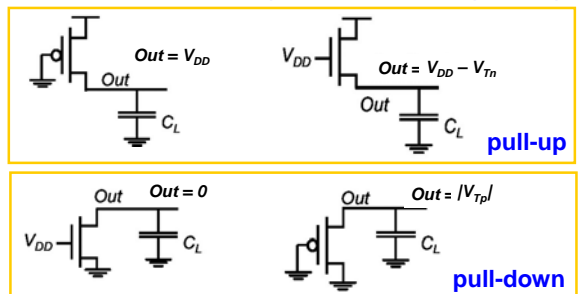

- PMOS is better pull-up
- NMOS is better pull-down

Bad Idea

Exercise: Determine logic function

Determine V_{out} for $V_{in} = V_{DD}$ and $V_{in} = V_{SS}$

Why is this a bad circuit?

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 13

CMOS Gate is Inverting

Assume full-swing inputs (high = V_{DD} , low = V_{SS})

- Highest output voltage of NMOS is $V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$
- An 1 on NMOS gate can produce a **strong 0** at the drain, but not a strong 1
- Lowest output voltage of PMOS is $V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$ (with $V_{GS}, V_{Tp} < 0$ for PMOS)
- An 0 on PMOS gate can produce a **strong 1** at the drain, but not a strong 0
- Need NMOS for pull-down, PMOS for pull-up
- A 1 at input can pull-down, 0 at input can pull-up
- A 1 can produce a 0, a 0 can produce a 1

Inverting behavior

For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 14

Complementary static CMOS

- Complex Logic Gates
- VTC, Delay and Sizing

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 15

Complementary Static CMOS

§ 6.2.1

- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 16

Mutual Exclusive PDN and PUN

Out = $(AB + C)'$

C	B	A	P D N	P U N	Out
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

PDN Off
PUN On

PUN Off
PDN On

For all Complementary Static CMOS Gates, either the PUN or the PDN is conducting, but never both.

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 17

Complementary Static CMOS (2)

- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN
- series \leftrightarrow parallel
- nmos \leftrightarrow pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need 2N transistors for N-input gate

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 18

Implementation of Combinational Logic

How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?

- Example: $Y = \overline{(A + BC)}D$
- Remember: only inverting gates available




TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 19

Implementation of Combinational Logic

 - Example: $Y = \overline{(A + BC)}D$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path → DELAY



transistors logic depth
 Q: Can this be improved?


TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 20

Improved Gate Level Implementation

 Using DeMorgan $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



- Q: Can this be further improved?


TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 21

Complex CMOS Logic Gates

 - Restriction to basic NAND, NOR etc. **not necessary**
- Easy to synthesize **complex gates**



transistors: 8
 Logic depth: 1

TUD/EE ET1205 D2 0708 - © NvdM


5/22/2008

5 combinational 22

How to Synthesize Complex Gates

$Y = \overline{(A + BC)}D$

 - Using tree representation of Boolean function
- Operator with branches for operands
- As a series-parallel network



	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series


TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 23

Complex Gate Synthesis Example

$\overline{Y} = (A + (BC))D$

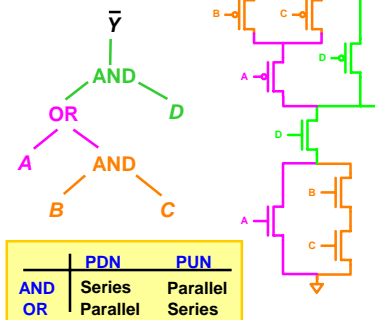

- Recipe
- Write $Y = f(\text{inputs})$
 - Decompose f in tree form
 - Realize tree branches according to table at bottom-left
 - Use inverted inputs if necessary

TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 24

And-Or-Invert Gate

Dual PMOS pull-up network

V_{out}

V_{DD}

5/22/2008 5 combinational 25

And-Or-Invert Example

■ From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$

$\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

■ \bar{A}, \bar{B} to be created with extra inverters (or by restructuring previous circuits)

5/22/2008 5 combinational 26

And-Or-Invert Improvement

$Y = \bar{A}BC + A\bar{B}C$
12 transistors

$Y = (\bar{A}B + A\bar{B})C$
10 transistors

2-level logic minimization: see Katz (CS1), § 2.3

5/22/2008 5 combinational 27

CMOS Complex Gate Sizing

$Y = (A + BC)D$

2 trans. in series

3 trans. in series

- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

5/22/2008 5 combinational 28

CMOS Complex Gate Sizing

- Assume all transistors will have minimum length L
- Determine W_p for PDN transistor of inverter that would give the desired 'drive strength'
- For each transistor in PDN of complex gate do the following:
 - Determine the length l of the longest PDN chain in which it participates
 - Set $W = l W_p$
- Repeat this procedure for PUN, using W_p for PUN transistor of inverter.

5/22/2008 5 combinational 29


Gate Sizing

- W/L ratios
- what are the W/L of 2-input NAND for same drive strength?

0-th order calculation

5/22/2008 5 combinational 30


Exercise

 

Exercise:

- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, assume PU/PD = 3
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same PU/PD)
- Compare sum of gate areas in (a) and (b). Note: area ~ width


Avoid Large Fan-In

 

C linear in N
R linear in N
Delay ∝ RC quadratic in N

Empirical
Delay = a₁FI + a₂FI² + a₃F³

Data-Dependent Timing


 


$t_{PHL} = 0.69R_N C_L$
 $t_{PLH} = 0.69R_P C_L$

You should be able to identify the transistor paths that charge or discharge C_L , and calculate resulting RC delay model, including effects of wires and fan-out

$t_{PHL} = 0.69(R_N \times 2)C_L$ **Series connection**
 $t_{PLH} = 0.69R_P C_L$ **One input goes low**
 $t_{PLH} = 0.69(R_P/2)C_L$ **Two inputs go low, parallel connection**



Data-dependent VTC: 2nd order effects

  

- Charge at 'int'
- Body effect in M_2
- Short-circuit currents

Don't need to be able to work with these effects
 But remember: there is more going on than shown by our simple, 1st order model

Data-dependent Timing (2)

  

Input Data Pattern	Delay (pS)
A = B = 0 → 1	69
A = 1, B = 0 → 1	62
A = 0 → 1, B = 1	50
A = B = 1 → 0	35
A = 1, B = 1 → 0	76
A = 1 → 0, B = 1	57

Ratioed logic
Pass transistor logic

Pseudo NMOS Ratioed Logic

- ☺ Reduced area
- ☺ Reduced capacitances
- ☹ Increased V_{OL}
- ☹ Reduced noise margins
- ☹ Static dissipation

§ 6.2.2

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 37

Ratioed Logic V_{OL} Computation

Exercise: verify these assumptions/steps

$I_{Dn} \text{ (linear)} = I_{Dp} \text{ (saturation)}$

$$k_n \left((V_{DD} - V_{Tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left((-V_{DD} - V_{Tp})V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn})V_{OL} \approx k_p (-V_{DD} - V_{Tp})V_{DSAT}$$

Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} |V_{DSAT}| \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSAT}|$$

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 38

Pass-transistor and Pass-gate circuits

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 39

Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (extra inverters)

But remember:

NMOS vs. PMOS, pull-down vs. pull-up

- PMOS is better pull-up
- NMOS is better pull-down

§ 6.2.3

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 40

Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (might mean extra inverters)
- Reduced V_{OH} , noise margins
- $V_{OH} = V_{DD} - (V_{Tno} + \gamma(\sqrt{2\phi_f} + V_{OH}) - \sqrt{2\phi_f})$
- Static dissipation in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by complementary pass gates (NMOS + PMOS parallel)

Exercise: Why is there static dissipation in next conventional gate?

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 41

Pass Gates

- Remedy: use an N-MOS and a P-MOS in parallel


- Pass gates eliminate some of the disadvantages of simple pass-transistors
- But also some of the advantages
- Design remains a trade-off!

Pass-gate a.k.a. Transmission-gate

TUD/EE ET1205 D2 0708 - © NvdM 5/22/2008 5 combinational 42

 Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?





TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 43

Pass Transistor Logic

  - Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$ (S' is easier notation for $S\text{-bar} = S\text{-inverse} = \overline{S}$)
- $Y = ((AS)' (BS)')'$ allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8) transistors (see also Katz, section 4.2)



TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 44

Summary

- Conventional Static CMOS basic principles
- Complementary static CMOS
 - Complex Logic Gates
 - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic

TUD/EE ET1205 D2 0708 - © NvdM

5/22/2008

5 combinational 45