

## MODULE 8

### MODULARITY

## Course Material for Modularity

### Chapter 11

P = primair, I = Illustratie, O = overslaan

P 11.1	Introduction	560
P 11.2	Datapaths in Digital Processor Architectures	560-561
P 11.3	The Adder	561
P 11.3.1	The Binary Adder: Definitions	561-564
P 11.3.2	The Full Adder: Circuit Design Consideration	564-578
I 11.3.2	Manchester Carry Chain Adder	568-570
O 11.3.3	The Binary Adder: Logic Design Considerations	571-586
P 11.4	The Multiplier	586
P 11.4.1	The Multiplier: Definitions	586-587
P 11.4.2	Partial-Product Generation	587-589
P 11.4.3	Partial-Product Accumulation	589-592
O	The Tree Multiplier	592-593
I 11.4.4	Final Addition	593-594
P 11.5	The Shifter	595
P 11.5.1	Barrel Shifter	595-596
P 11.5.2	Logarithmic Shifter	596
O 11.6	Other Arithmetic Operators	596-600
O 11.7	Power and speed trade-offs	600-618
P 11.8	Perspective: Design as a Trade-off	618-619
P 11.9	Summary	619-620

## Outline

- Background on Modular Design
  - Hierarchy, reuse, regularity
  - Architecture, bit-slicing
- Adder Design
- Multiplier Design
- Shifter Design
- Layout Strategies (regularity)
- Design as a Trade-Off

contains a lot of reminders

Get further appreciation of some system level design issues


## Adder Design

- Adders are fundamental building blocks
  - Digital filtering (DSP): MP3 en/decoder, GSM, GPS, ...
  - Data processing
  - Multiplication
  - Address arithmetic
  - ...
- Good performance is key
- Many architectures
  - ✓ ■ Static adder
  - ✗ ■ Dynamic adder (Manchester Carry Chain)
  - ✗ ■ Pipelined Adder
  - ✗ ■ Carry-Bypass, Carry Lookahead, Carry Select
  - ✗ ■ ...
- Design trade-offs, optimization
  - ✓ ■ Architecture level
  - ✓ ■ Logic level
  - ✓ ■ Circuit level
  - ✓ ■ Layout level

Also see Digital Systems – Katz § 5.5

Most effective  
↑  
↓  
Least effective


## Full-Adder

 

A	B	$C_i$	S	$C_o$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Add three one-bit numbers  
Equivalently: count # 1's in A, B,  $C_i$   
Output as 2-bit number  $\langle C_o S \rangle$

## The Ripple-Carry Adder

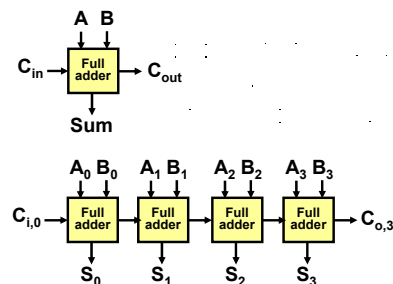

### The Binary Adder

$\bar{C}$	$C$
$\bar{A}\bar{B}$	1
$\bar{A}B$	1
$A\bar{B}$	1
$A\bar{B}$	1

$\bar{C}$	$C$
$\bar{A}\bar{B}$	
$\bar{A}B$	1
$A\bar{B}$	1
$A\bar{B}$	1

(a) SUM      (b) CARRY

$S = A \oplus B \oplus C_i$   
 $= \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$

$C_o = AB + BC_i + AC_i$   
 $= AB + BC_i + AC_i$

AND-OR expressions for sum and carry

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 7

### Naïve Complementary CMOS Implementation

- Use DeMorgan to convert AND-OR expressions for SUM and CARRY to NAND-NAND
- $PQ + RS = \overline{\overline{PQ} \overline{RS}}$  (example)

**Transistor Count**

- 3 × INVERT
- 3 × NAND-2
- 5 × NAND-3
- 1 × NAND-4

Q: What is advantage of NAND-NAND over NOR-NOR? Consider drive strength vs. area

SUM =  $A'B'C_i + A'BC_i + AB'C_i + ABC_i$

C<sub>o</sub>

Can do better using more clever boolean factoring, but...

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 8

### Full-Adder Boolean Factoring

$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$   
 $= ABC_i + \bar{C}_0(A + B + C_i)$

$C_o = AB + BC_i + AC_i$   
 $= AB + (A + B)C_i$

A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 9

### Improved Complementary Static Full Adder

**28 Transistors**

Carry logic  
 $C_o = AB + (A + B)C_i$

Sum logic  
 $S = ABC_i + \bar{C}_0(A + B + C_i)$

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 10

### Ripple-Carry Adder Delay

- Worst case delay through full carry path (ripple carry)
- Linear with the number of bits (N)
- $T_{adder} = (N-1) T_{carry} + \text{Max}(T_{carry}, T_{sum})$
- $T_{adder} = O(N)$  "T<sub>adder</sub> is of Order N" means linear with N
- Goal: Make the fastest possible carry path circuit

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 11


### Adder Evaluation

**Carry Chain:**

- Long PMOS chains
- High C at X
- 2 (inverting) stages

TU/EE ET1205 D2 0708 - © NvdM      5/28/2008      8 modularity 12


### Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_0(A, B, C_i) = C_0(\bar{A}, \bar{B}, \bar{C}_i)$$
 
### Minimize Critical Path by Reducing Inverting Stages



- Can eliminate inverter in carry from each FA
- Need 2 different types of cells, but both with inverting carry – will require only one stage per bit

### Eliminate Inverter In Carry

 

### Multiplier Design

- Multipliers are fundamental building blocks too
  - Digital filtering (DSP): MP3 en/decoder, GSM, GPS, ...
  - Data processing
  - Address arithmetic
  - ...
- Good performance is key, often they are the performance bottleneck
- Multipliers are complex arrays of adders
- Many architectures
  - Basic Array Multiplier
  - Bit-serial
  - Booth-encoding multiplier
  - Baugh-Wooley multiplier
  - Wallace tree multiplier
  - ...
- Design trade-offs, optimization
  - Architecture level, Logic level, Circuit level, Layout level

### The Binary Multiplication

$$X = \sum_{i=0}^{M-1} X_i 2^i \quad Y = \sum_{j=0}^{N-1} Y_j 2^j$$


$$Z = X \times Y = \sum_{k=0}^{M+N-1} Z_k 2^k$$

$$= \left( \sum_{i=0}^{M-1} X_i 2^i \right) \left( \sum_{j=0}^{N-1} Y_j 2^j \right)$$

$$= \sum_{i=0}^{M-1} \left( \sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right)$$

ADD AND SHIFT



Example: 42 x 11 = 462

 


Conclusion: similar to decimal multiplication

$$X_{10} \times Y_{10} = \sum_{i=0}^{M-1} \left( \sum_{j=0}^{N-1} X_i Y_j 10^{i+j} \right)$$

### The Array Multiplier

 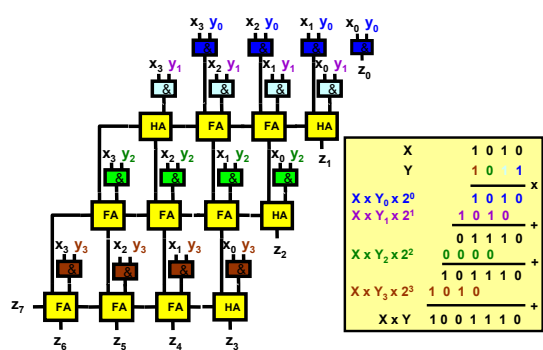
 
### The MxN Array Multiplier — Critical Path



- $t_{mult} \approx [(M - 1) + (N - 2)]t_{carry} + (N - 1)t_{sum} + t_{and}$
- Requires comparable carry and sum delays


### Adder Cells in Array Multiplier

#### Identical Delays for Carry and Sum

A	B	C <sub>i</sub>	S	C <sub>o</sub>	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate


$P = A \oplus B$   
 If  $P = 1$  then  $S = \bar{C}_i$ ,  $C_o = C_i$   
 If  $P = 0$  then  $S = C_i$ ,  $C_o = A$

### Carry-Save Multiplier

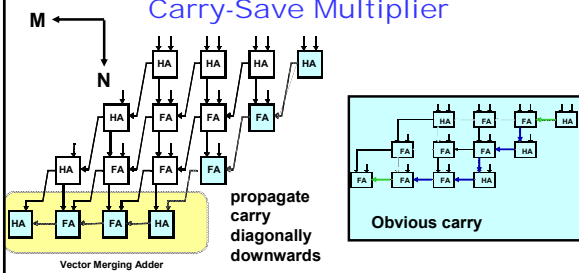

- $t_{mult} \approx (N - 1)t_{carry} + t_{and} + t_{merge}$  (assuming  $t_{add} \approx t_{carry}$ )
- Use **fastest possible adder** for final vector merging
- Will be larger, use more power, etc, **but need only one row!**

### Multiplier Floorplan

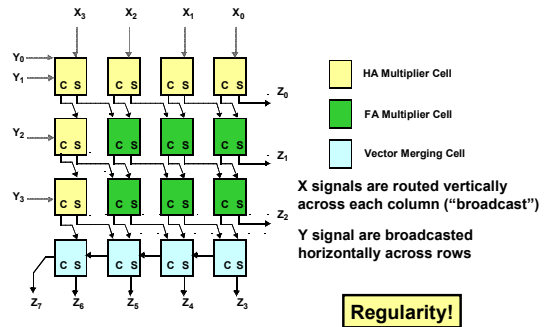

### Multippliers — Summary.

- Optimization Goals Different Vs Binary Adder
  - Once Again: Identify Critical Path
  - Other possible techniques
    - Logarithmic versus Linear (Wallace Tree Mult)
    - Data encoding (Booth)
    - Pipelining
- GLIMPSE AT SYSTEM LEVEL OPTIMIZATION**

### Shifter Design

- Shifters are fundamental building blocks too
  - Floating point units
  - Scalars
  - Multiplication by constant numbers (add and shift)
  - ...
- Constant shifting is only interconnect
- Programmable shifting requires active circuitry
- Usually dominated by interconnect
- Architectures
  - ✓ ■ Barrel Shifter
  - ✓ ■ Logarithmic Shifter
  - ...
- Design trade-offs, optimization
  - Architecture level, Logic level, Circuit level, Layout level
  - Simpler compared to Adder, Multiplier, hence less rewarding
- Good example of pay-off of structural design

### The Binary Shifter

Right nop Left

$A_i$   $B_i$

$A_{i-1}$   $B_{i-1}$

Bit slice i-1

- Multibit shifters by cascading
- M stages for M-bit shift
- Complex and slow for larger M
- More structured approach needed

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 25

### The Barrel Shifter

$A_3$   $B_3$

$A_2$   $B_2$

$A_1$   $B_1$

$A_0$   $B_0$

Sh0 Sh1 Sh2 Sh3

- Need M stages for M-bit shift
- Signal passes only one pass-transistor => delay?
- Area Dominated by Wiring, not (always) by # transistors

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 26

### 4x4 Barrel Shifter

$A_3$   $B_3$

$A_2$   $B_2$

$A_1$   $B_1$

$A_0$   $B_0$

Sh0 Sh1 Sh2 Sh3

Buffer

- Section i shifts  $2^{(i-1)}$  bits
- Need only  $\log_2 M$  stages for M-bit shift

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 27

### Logarithmic Shifter

Sh1 Sh1  $2^{Sh1}$  Sh2 Sh2  $2^{Sh2}$  Sh4 Sh4  $2^{Sh4}$

$A_3$   $B_3$

$A_2$   $B_2$

$A_1$   $B_1$

$A_0$   $B_0$

- Section i shifts  $2^{(i-1)}$  bits
- Need only  $\log_2 M$  stages for M-bit shift

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 28

### 0-7 bit Logarithmic Shifter

$A_3$  Out3

$A_2$  Out2

$A_1$  Out1

$A_0$  Out0

Shift 1 Buffers Shift 2 Buffers Shift 4 Buffers

Basic cell Inverters with level restorer (see R2, Figure 6.35)

Exercise: decipher layout of basic cell and draw transistor circuit

- M is maximum bit displacement,  $K = \log_2 M$
- For large M, width is dominated by vertical metal wires
- Disregard buffer size, only count vertical wires
- Barrel shifter needs 1 control and 1 data wire per stage
- # Wires:  $2M$
- Log shifter needs 2 control +  $2^{i-1}$  data wires for stage i
- # Wires:  $2K + (1+2+4+\dots+2^{K-1}) = 2K + 2^K - 1 = 2 \log_2 M + M - 1$
- Log shifter will have smaller area for larger M!

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 29


### Size Comparison

width

- M is maximum bit displacement,  $K = \log_2 M$
- For large M, width is dominated by vertical metal wires
- Disregard buffer size, only count vertical wires
- Barrel shifter needs 1 control and 1 data wire per stage
- # Wires:  $2M$
- Log shifter needs 2 control +  $2^{i-1}$  data wires for stage i
- # Wires:  $2K + (1+2+4+\dots+2^{K-1}) = 2K + 2^K - 1 = 2 \log_2 M + M - 1$
- Log shifter will have smaller area for larger M!

TU/EE ET1205 D2 0708 - © NvdM 5/28/2008 8 modularity 30

## Speed Comparison

 


### Exercise

- Discuss the relative speeds of both shifters, as a function of  $M$  (see discussion in book). Consider:
  - Number of sections
  - Input capacitance at the buffers (including diffusion areas of the driving pass-transistors)
  - Number of buffers (necessity of buffers)
  - The number of pass-transistors the signal has to pass
  - ...


## Layout Strategies (regularity)

## Bit-Sliced Design

 


- Tile identical processing elements
- Rows for each bit
- Columns for each function
- Control from top (often with *control-slice*)
- (Example orientation)

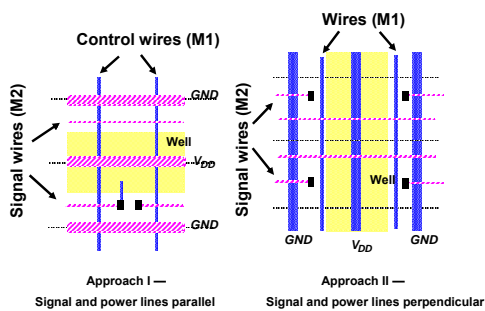
## Layout Strategies for Bit-Sliced Datapaths




## Layout of Bit-sliced Datapaths

 

## Layout of Bit-sliced Datapaths (2)

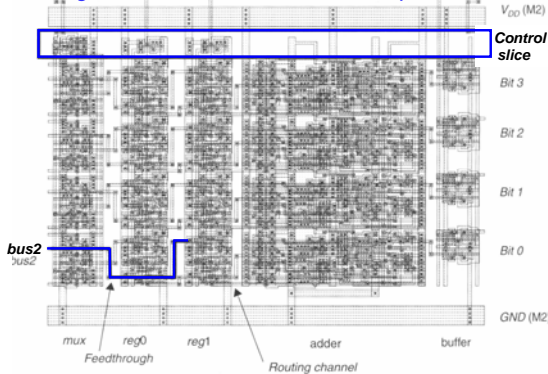

## Layout of Bit-sliced Datapaths (3)

 

Unoptimized  
Area: 4.2mm<sup>2</sup>

With feedthroughs  
Area: 3.2mm<sup>2</sup>

+ Equalized cell height  
Area: 2.2mm<sup>2</sup>


- Good layout really counts!
- Feedthroughs less (but still) useful with multiple metal layers

TU/EE ET1205 D2 0708 - © NvdM

5/28/2008

8 modularity 37

## Design as a Trade-Off

 

TU/EE ET1205 D2 0708 - © NvdM

5/28/2008

8 modularity 38

## VLSI Design

- Select **right structure**
- Determine and optimize **critical timing path** for speed
- Optimize rest for **area** (cost) and/or **power** and/or **design time**
- Consider **layout** aspects

**Regularity and modularity** are a VLSI designer's best friends

TU/EE ET1205 D2 0708 - © NvdM

5/28/2008

8 modularity 39

## Summary

- Background on Modular Design
  - Hierarchy, reuse, regularity
  - Architecture, bit-slicing
- Adder Design
- Multiplier Design
- Shifter Design
- Layout Strategies (regularity)
- Design as a Trade-Off

Got further appreciation of some **system level design issues?**

TU/EE ET1205 D2 0708 - © NvdM

5/28/2008

8 modularity 40

## The End



TU/EE ET1205 D2 0708 - © NvdM

5/28/2008

8 modularity 41