 


# Interconnect



# Course Material for Interconnect


## Chapter 4, 2nd ed.

**P = primair, I = Illustratie, O = overslaan**

<b>P</b>	<b>4.1</b>	<b>Introduction</b>	<b>136</b>
<b>P</b>	<b>4.2</b>	<b>A First Glance</b>	<b>136 – 138</b>
<b>P</b>	<b>4.3</b>	<b>Interconnect Parameters</b>	<b>138 – e.v.</b>
<b>O</b>		<b>So far we have .... (onder example 4.2)</b>	<b>147 – 148</b>
<b>O</b>	<b>4.3.3</b>	<b>Inductance</b>	<b>148 – 150</b>
<b>P</b>	<b>4.4</b>	<b>Electrical Wire Models</b>	<b>150 – 156</b>
<b>I</b>	<b>4.4.4</b>	<b>Distributed rc line – <i>hiervoor is vervangende stof</i></b>	<b>156 – 159 (1)</b>
<b>O</b>	<b>4.4.5</b>	<b>The transmission line</b>	<b>159 – e.v.</b>
<b>O</b>	<b>4.5</b>	<b>Spice wire models</b>	<b>170 – 171</b>
<b>I</b>	<b>4.5.3</b>	<b>Perspective: a look into the future</b>	<b>171 – 174</b>


**Replacement voor Distributed RC line: Elmore Delay**

# Interconnect

 

- Wires are **not ideal** interconnections
- They may have non-negligible **capacitance, resistance, inductance**
- These are called **wire parasitics**
- Can **dominate** performance of chip
- Must be accounted for during **design**
- Using **approximate models**
- Detailed **post-layout verification** also necessary

# Wires

 


← IBM CMOS 7S  
copper process,  
0.16  $\mu\text{m}$

# Interconnect Hierarchy




 **Cross-section of IBM 0.13  $\mu$  process**



**Example Interconnect Hierarchy for typical 0.25  $\mu$  process (Layer Stack)**

# 45 nm Interconnect Technology

 

**8 interconnect layers in 45 nm technology**

**[Ingerly – iitc – 2008]**

# Outline





- **Capacitance**
  - Area/perimeter model, coupling**
- **Resistance**
  - Sheet resistance**
- **Interconnect delay**
  - Delay metrics, rc delay, Elmore delay**

# Capacitance

- Area/perimeter model, coupling




# Wake Up! Models ahead!

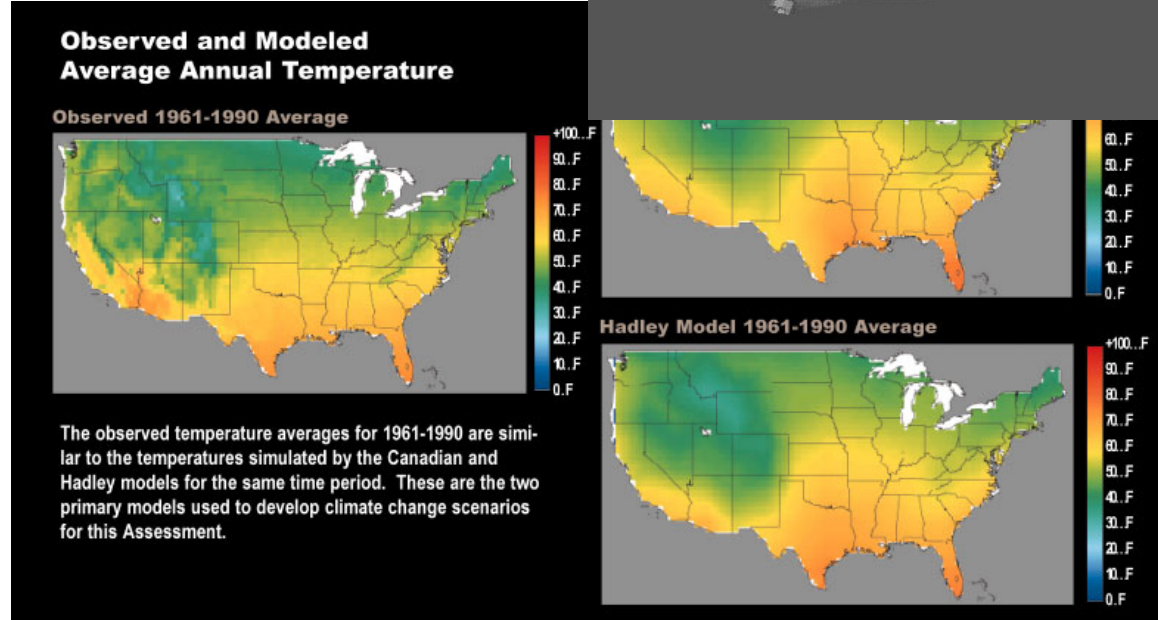   

6 entries found for **model**.  
To select an entry, click on it.

model[1,noun]  
model[2,verb]  
model[3,adjective]  
animal model  
role model  
Watson-Crick model

Go

Main Entry: **<sup>1</sup>mod·el** 

Pronunciation: 'mä-d<sup>ə</sup>l

Function: *noun*

Etymology: Middle French *modelle*, from Old Italian *modello*, from (assumed) Vulgar Latin *modellus*, from Latin *modulus* small measure, from *modus*

**1** *obsolete* : a set of plans for a building

**2** *dialect British* : COPY, IMAGE

**3** : structural design <a home on the *model* of an old farmhouse>

**4** : a usually miniature representation of something; *also* : a pattern of something to be made

**5** : an example for imitation or emulation

**6** : a person or thing that serves as a pattern for an artist; *especially* : one who poses for an artist

**7** : ARCHETYPE

**8** : an organism whose appearance a mimic imitates

**9** : one who is employed to display clothes or other merchandise : MANNEQUIN

(as an atom) that cannot be directly observed

**12** : a system of postulates, data, and inferences presented as a mathematical description of an entity or state of affairs

**13** : VERSION


**15** : VERSION

# Modeling


- An **abstraction** of (the properties) of something to help **understanding** and **predicting** its behavior
- **Domain Specific**: weather, climate, economy, stock market, ...
- Different models for something to **answer different questions**
- **Black-Box** modeling vs. **Physically Based**

After Einstein:

 
**<a model> should be as simple as possible, but not simpler**



# Wire Capacitance – Parallel Plate

 
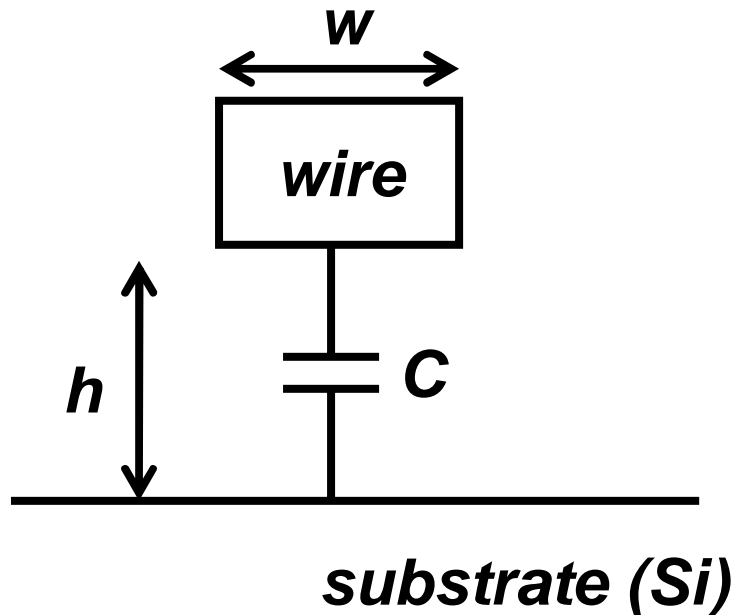
$$C = \frac{\epsilon_0 \epsilon_r W l}{d}$$




$$\frac{C}{l} = \epsilon_0 \epsilon_r \frac{w}{h}$$

$$\epsilon_0 = 8.85 \text{ pF/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

# Wire Capacitance – Fringing Fields

 


$$C_{\text{wire}} = C_{\text{fringe}} + C_{\text{pp}} = \frac{2\pi\epsilon d_i}{\log(t_{di}/H)} + \frac{W\epsilon d_i}{t_{di}}$$

- Works reasonably well in practice
- Not directly applicable for interconnects with varying widths
 
# Wire Capacitance – Area/Perimeter Model

- $C_a$  was calculated with modified wire width
- Formula inapplicable for irregular interconnects (non-constant width)



- More practical approximation

$$C = A \times C_a + P \times C_p$$

$A$  = Area

$C_a$  = Area capacitance

$P$  = Perimeter

$C_p$  = Perimeter capacitance

*units*

$m^2$

$F / m^2$

$m$

$F / m$


*alternative*

$\mu m^2$

$aF / \mu m^2$


$\mu m$

$aF / \mu m$

 

$$C = \square \times C_a + \square \times C_p$$

# Area / Perimeter Capacitance Model

 



$$C = \square \times C_a + \square \times C_p$$

■ **Question:** How to derive  $C_a, C_p$  ?

**How accurate is this model?**

# Derivation of $C_a, C_p$

$C \uparrow$   
[aF/ $\mu\text{m}$ ]

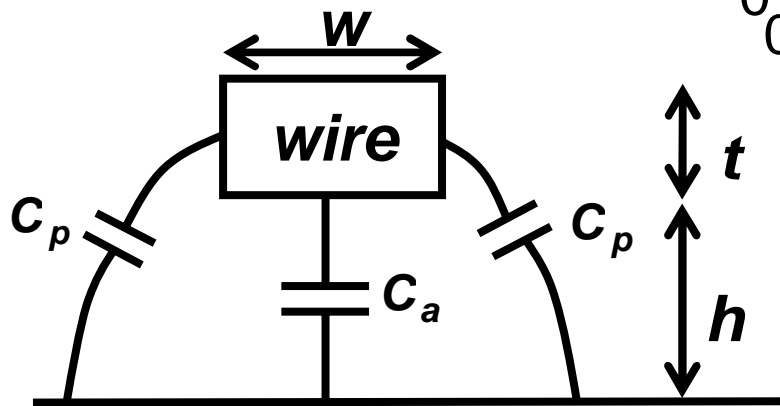
 




## Derivation of $C_a, C_p$

- **2D (cross-section) numerical computation (or measurement)**
- **$C_l$  : total wire capacitance per unit length**
- **$C_a = \epsilon_0 \epsilon_r / h$**
- **$C_p = 1/2 (C_l - C_a \times w)$**
- **$C_p$  depends on  $t, h \rightarrow$  determined by technology, layer**
- **$C_p$  would depend slightly on  $w$  (see previous graph), this dependence is often ignored in practice**


# Area / Perimeter Capacitance

  

- $C_p$  dominates for many wires
- $C_p$  may not be neglected
- A constant value for  $C_p$  is usually a good approximation
- $C_p$  is sometimes called  $C_f$  (fringe capacitance)


 
# Interconnect Capacitance Design data

- See Table 4.2 (or inside backside cover)
- Example: M1 over Field vs. M1 over Active (hypothetical)





M1 over Active	M1 over Field	Unit
$C_a = 41$	$C_a = 30$	$aF/\mu m^2$
$C_p = 47$	$C_p = 40$	$aF/\mu m$

# Coupling Capacitances

  

## Coupling Capacitances (2).

  


- $C_T = C_{1g} + C_{12} = C_{2g} + C_{12}$  fairly constant
- Use that as first order model
- Interconnect capacitance design data (e.g. Table 4.3)

# Resistance

- Sheet resistance

# Wire Resistance

 

- Proportional to  $l$
- Inversely proportional to  $w$  and  $t$  (cross-sectional area)
- Proportional to  $\rho$ : specific resistance, material property [ $\Omega\text{m}$ ]
- $R = \rho l / wt$
- Aluminum:  $\rho = 2.7 \times 10^{-8} \Omega\text{m}$   
Copper:  $\rho = 1.7 \times 10^{-8} \Omega\text{m}$


# Sheet Resistance

- $R = \rho l / wt$
- $t, \rho$  constant for layer, technology
- $R = R_s l / w$
- $R_s$  : sheet resistance [ $\Omega / \square$ ]  
resistance of a square piece of interconnect  
other symbol:  $R_s$
- Interconnect resistance design data e.g. Table 4.5 (or inside back-cover)



 
# Interconnect Resistance

- Assume  $R_{\square} = 40 \Omega$
- Estimate the resistance between A and B in the wire below.


 
$$R_{AB} \approx 6 \times 40 = 240 \Omega$$



$$R_{CD} \approx 11 \times 40 = 440 \Omega$$

**Engineering** is about making controlled approximations to something that is too complicated to compute exactly, while ensuring that the approximate answer still leads to a working (functional, safe, ...) system

# Exercise.


An interconnect line is made from a material that has a resistivity of  $\rho = 4 \mu\Omega\text{-cm}$ . The interconnect is  $1200 \text{ \AA}$  thick, where 1 Angstrom ( $\text{\AA}$ ) is  $10^{-10} \text{ m}$ . The line has a width of  $0.6 \mu\text{m}$ .

- a) Calculate the sheet resistance  $R_{\square}$  of the line.
- b) Find the line resistance for a line that is  $125 \mu\text{m}$  long.

## Interconnect delay


- Delay metrics, rc delay, Elmore delay

# Delay

 

- Model driver as linearized Thevenin source  $V$ ,  $R_s$ , assume step input
- Model load as  $C_L$
- Wire is an RC network (two-port)

# Wire Capacitance

 


Assume wire  
behaves purely  
capacitive

$$(C_w + C_L) \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_s} = 0$$

$$V_{out} = V_{in} - \tau \frac{dV_{out}}{dt} \quad \tau = R_s (C_w + C_L)$$

$$V_{out} = (1 - e^{-t/\tau}) V_{in}$$

# Wire Resistance

 


Now, assume wire capacitance *and* resistance

- $\tau = (R_s + R_w)(C_w + C_L)$


- Is this a good model?

- R and C are **distributed** along the wire


# Uniform RC Line

 


**Symbol**

 

**[Always] use first order model**

 


# RC Delay (Uniform RC Line)

 

**Basic  $\pi$ -model  
of wire**



# Equivalent Time Constant

 


- Multiple time-constants
- Need for one “equivalent” number
- Offered by *Elmore Delay*  $T_D$

$$T_D = R_s C_w/2 + (R_s + R_w)(C_w/2 + C_L)$$


- Effective “one number” model for delay

How to  
compute  
Elmore  
Delay?


# Equivalent Time Constant

 
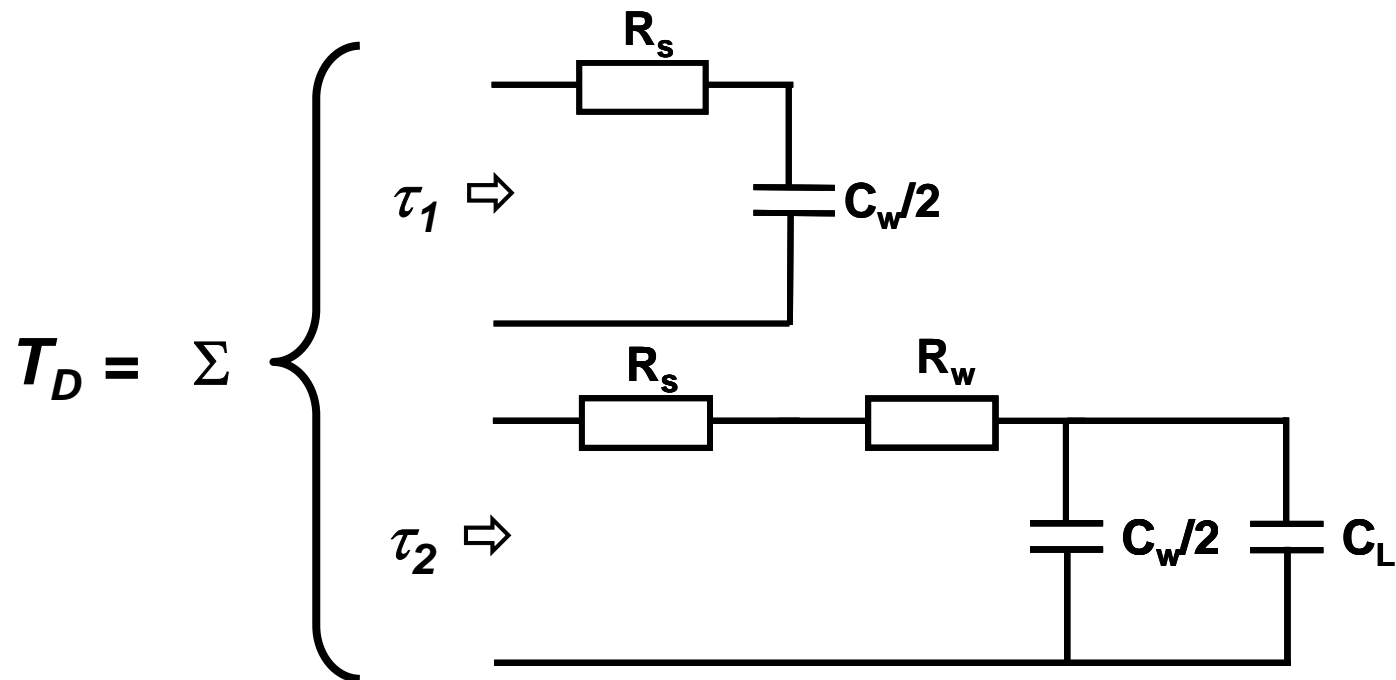
$$T_D = R_S C_W / 2 + (R_S + R_W)(C_W / 2 + C_L)$$



# Shared Path Resistance

 


■ Define:  $R_{ii}$  = Resistance from node i to input

■ Example:  $R_{11} = R_1$      $R_{22} = R_1 + R_2$      $R_{33} = R_1 + R_2 + R_3$

■ Define:  $R_{ik}$  = Shared path resistance to input for node i and k

■  $R_{12} = R_1$      $R_{13} = R_1$      $R_{23} =$

# Elmore Delay for RC ladders

 

■ Define:  $T_{Di} = \sum_{k=1}^N R_{ik} C_k$

## Elmore Delay


We will use  $0.69 \times T_{di}$  as approximation of wire delay ( $t_{50\%}$ )

■  $T_{D1} = R_{11}C_1 + R_{12}C_2 + R_{13}C_3 =$   
 $= R_1C_1 + R_1C_2 + R_1C_3$


$T_{D3} = R_{31}C_1 + R_{32}C_2 + R_{33}C_3 =$   
 $= R_1C_1 + (R_1 + R_2)C_2 + (R_1 + R_2 + R_3)C_3$

■  $T_{D2} =$


# Elmore Delay for Distributed RC Lines

 

**Symbol**

 


**Symmetric  
 $\pi$ -model**

 

- **Theorem:** For Elmore Delay calculations, each uniform distributed RC section is equivalent to a symmetric  $\pi$ -model

# Canonical Driver-Line-Load

 

$$\begin{aligned} \blacksquare T_{D_1} &= R_s \frac{cl}{2} + (R_s + rl) \left( C_L + \frac{cl}{2} \right) \\ &= R_s (cl + C_L) + rl C_L + \frac{1}{2} rcl^2 \end{aligned}$$


**■ Delay quadratic in line length**

# Shared Path Resistance for Tree Structures

In order to compute Elmore Delay at node 3:

 Exercise (for node 4):


Compute  $R_{41}$ ,  $R_{42}$ ,  $R_{43}$ ,  $R_{44}$



$R_{31}?$	$R_1$
$R_{32}?$	$R_1 + R_2$
$R_{33}?$	$R_1 + R_2 + R_3$
$R_{34}?$	$R_1 + R_2$


Off-path resistances don't count

# Elmore Delay for Tree Structures.

 

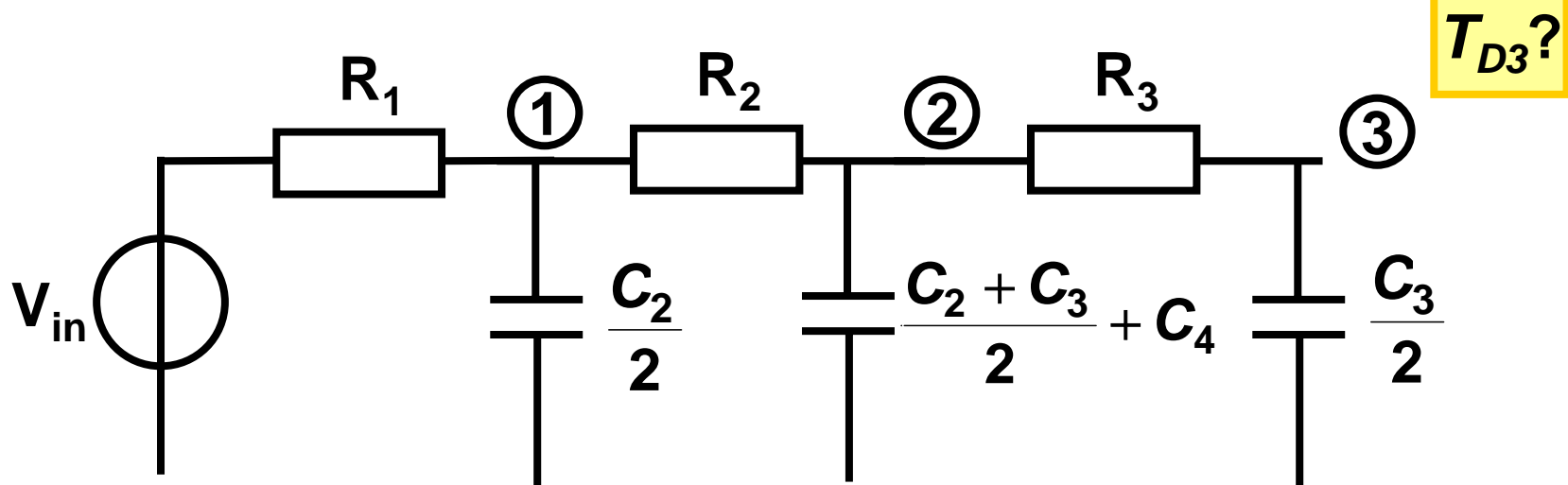**Exercise:** Compute  $T_{D1}$ ,  $T_{D2}$ ,  $T_{D3}$ ,  $T_{D4}$

- Replace RC lines by  $\pi$ -sections
- Given observation node  $i$ , then only resistances along the path from input to node  $i$  can possibly count
- Make others zero
- Compute as if RC ladder





# Summary

- **Capacitance**  
Area/perimeter model, coupling
- **Resistance**  
Sheet resistance
- **Interconnect delay**  
Delay metrics, rc delay, Elmore delay