

MODULE 5

COMBINATIONAL LOGIC

Course Material for Combinational

Extra: Slides about how to implement a static combinational gate with NMOS/PMOS transistors, given the Boolean function

P	6.1	Introduction	236
P	6.2	Static CMOS Design	236 – 237
P	6.2.1	Complementary CMOS	237 – 242
I		Propagation Delay of Complementary CMOS gates	242 – 249
I		Design Techniques for large fan-in	249 – 251
O		Optimizing performance in combinational networks	251 – 257
O		Power consumption in CMOS logic gates	257 – 263
P	6.2.2	Ratioed Logic	263 – 267
I		How to build even better loads	267 – 268
P	6.2.3	Pass-transistor basics	269 – 270
I		Example 6.10	271 – 272
O		Diversen	272 – 277
P		Solution 3: Transmission gate logic	277 – 280
I		Rest of § 6.2.3	280 – 284
I	6.3	Dynamic CMOS Design	
I	6.3.1	Dynamic Logic: Basic Principles	284 – 286
I	6.3.2	Speed and Power Dissipation of Dynamic Logic	287 – 290
I	6.3.3	Signal Integrity Issues in Dynamic Design	290 – 295
O	6.3.4	Cascading Dynamic Gates	295 – 303
O	6.4	Perspectives	303 – 306
P	6.5	Summary	306 – 307


Combinational Logic - Outline

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
 - **Complex Logic Gates**
 - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**
- **Dynamic CMOS gates → only illustration**

Complementary Static CMOS


Basic Principles

Combinational vs. Sequential Logic

 

(a) Combinational

$$\text{Output} = f(\text{In})$$

 

(b) Sequential

$$\text{Output} = f(\text{In}, \text{History})$$



Reminder

DeMorgan Transformations



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a **switch** controlled by its gate signal

  
NMOS switch **closes** when switch control input is **high**




PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is **low**

$Y = X$ if ...

 


$Y = X$ if \bar{A} and \bar{B}

 

$Y = X$ if \bar{A} or \bar{B}

2-Input Nand

 

$Y = 1$ if \bar{A} OR \bar{B}

$Y = 1$ if $\overline{A \text{ AND } B}$

$Y = \overline{A \text{ AND } B}$


$Y = 0$ if $A \text{ AND } B$

DeMorgan



B	A	Y
0	0	1
0	1	1
1	0	1
1	1	0

2-Input Nand



$$Y = \overline{A \text{ AND } B}$$

 

2-input Nand/Nor

  


NMOS vs. PMOS, pull-down vs. pull-up

 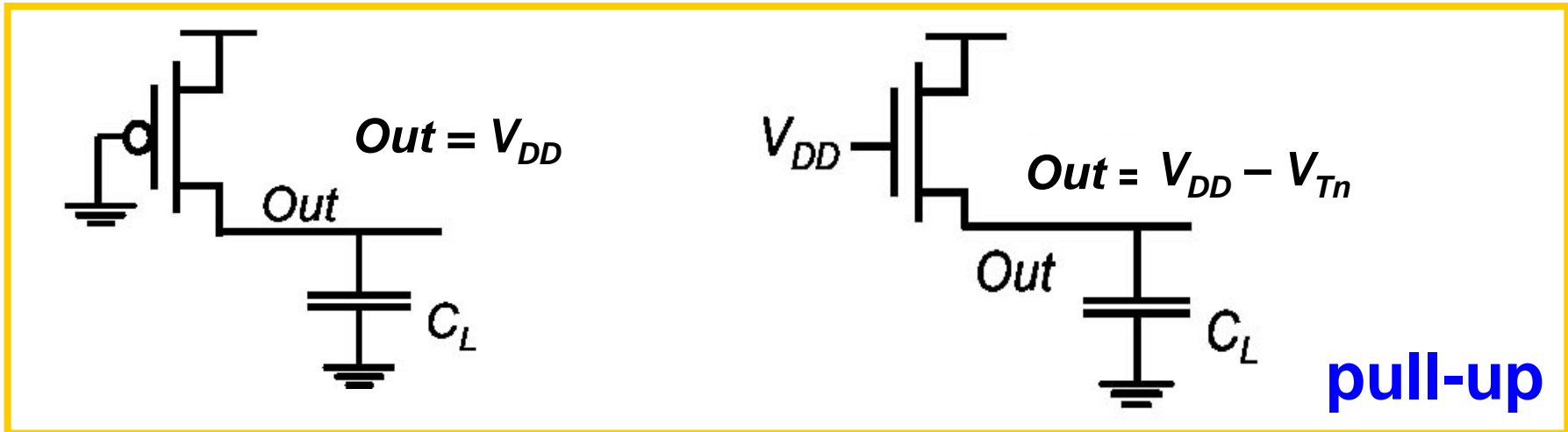

- PMOS is better pull-up
- NMOS is better pull-down

Bad Idea

 

Exercise: Determine logic function

Determine V_{out}
for $V_{in} = V_{DD}$ and $V_{in} = V_{SS}$

Why is this a bad circuit?

CMOS Gate is Inverting.

Assume full-swing inputs (high = V_{DD} , low = V_{SS})

- Highest output voltage of NMOS is

$$V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$$

- An 1 on **NMOS** gate can produce a **strong 0** at the drain, but not a strong 1

- Lowest output voltage of PMOS is

$$V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$$

(with $V_{GS}, V_{Tp} < 0$ for PMOS)

- An 0 on **PMOS** gate can produce a **strong 1** at the drain, but not a strong 0

- **Need NMOS for pull-down, PMOS for pull-up**

A 1 at input can pull-down, 0 at input can pull-up

A 1 can produce a 0, a 0 can produce a 1


Inverting behavior

For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates

Complementary static CMOS

- **Complex Logic Gates**
- **VTC, Delay and Sizing**


Complementary Static CMOS

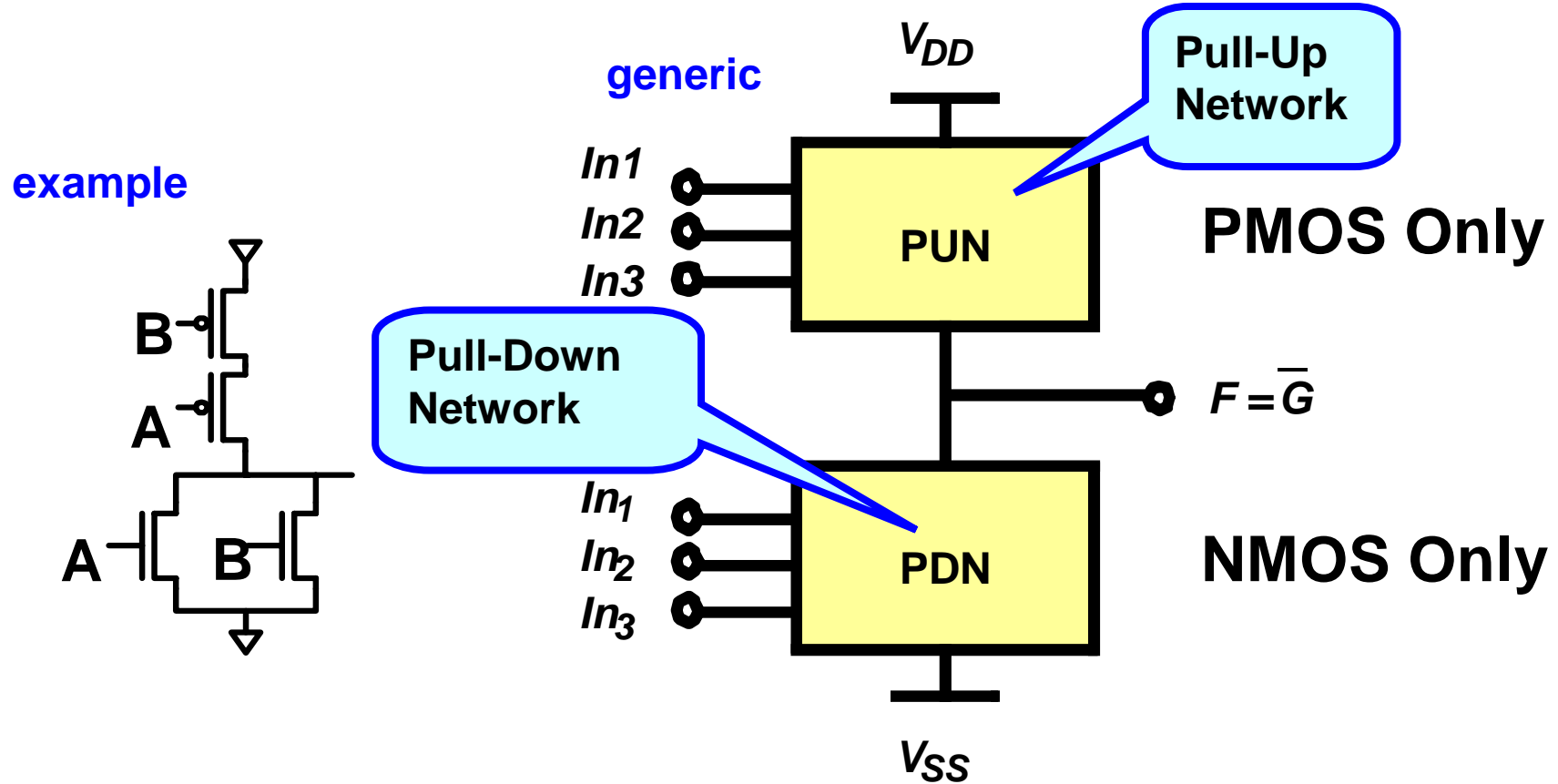

- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**

Mutual Exclusive PDN and PUN

$$\text{Out} = (AB + C)'$$

 

C	B	A	P D N	P U N	Out
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

} PDN Off
 } PUN On

 } PUN Off
 } PDN On

For all Complementary Static CMOS Gates, either the PUN or the PDN is conducting, but never both.

Complementary Static CMOS (2)


- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN
 - series \Leftrightarrow parallel
 - nmos \Leftrightarrow pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need $2N$ transistors for N -input gate

Implementation of Combinational Logic

- How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?

 
- Example: $Y = \overline{(A + BC)}D$

- Remember: only inverting gates available



Implementation of Combinational Logic

 - Example: $Y = \overline{(A + BC)D}$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path \Rightarrow DELAY





transistors logic depth

- Q: Can this be improved?

Improved Gate Level Implementation

  
■ Using DeMorgan $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



■ Q: Can this be further improved?


Complex CMOS Logic Gates

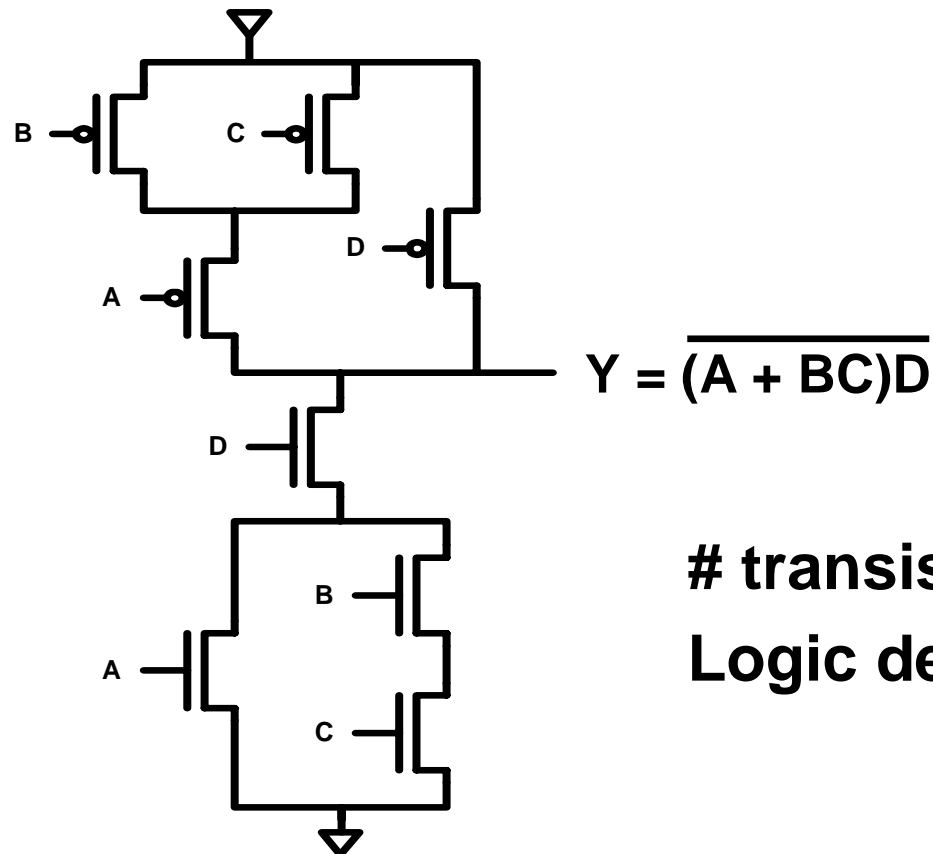- Restriction to basic NAND, NOR etc. **not necessary**
- Easy to synthesize **complex gates**



How to Synthesize Complex Gates

$$Y = \overline{(A + BC)D}$$

 


- Using tree representation of Boolean function
- *Operator* with branches for *operands*
- As a **series-parallel** network


	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

Complex Gate Synthesis Example

$$\bar{Y} = (A + (BC))D$$

 


	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

 

Recipe

- Write $\bar{Y} = f(\text{inputs})$
- Decompose f in tree form
- Realize tree branches according to table at bottom-left
- Use inverted inputs if necessary

And-Or-Invert Gate

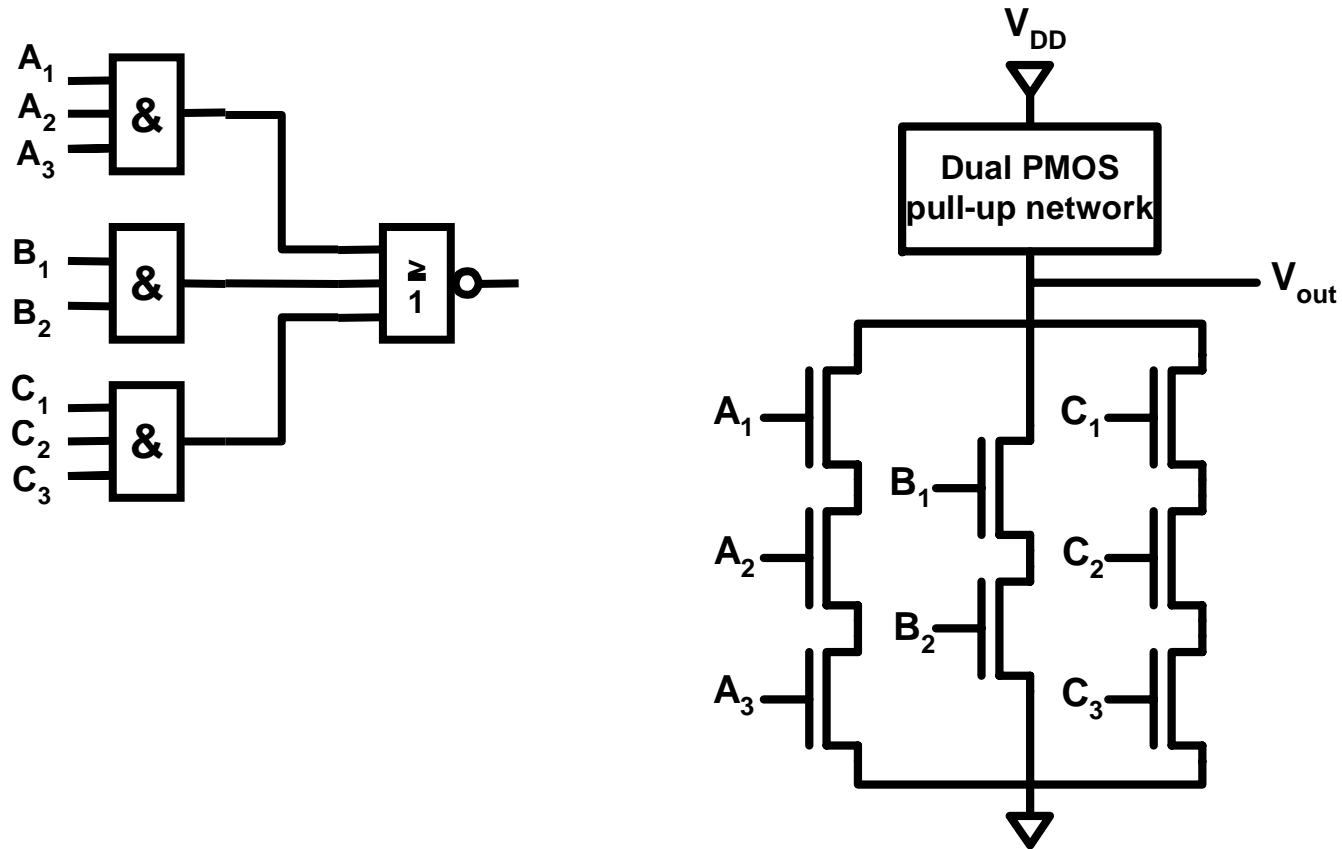

And-Or-Invert Example


- From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$


$\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

 


\bar{A} , \bar{B} to be created with extra inverters (or by restructuring previous circuits)

And-Or-Invert Improvement

 

$$Y = \overline{\bar{A}BC + A\bar{B}C}$$

12 transistors

 


$$Y = \overline{(\bar{A}B + A\bar{B})C}$$

10 transistors

2-level logic minimization: see Katz (CS1), § 2.3

CMOS Complex Gate Sizing


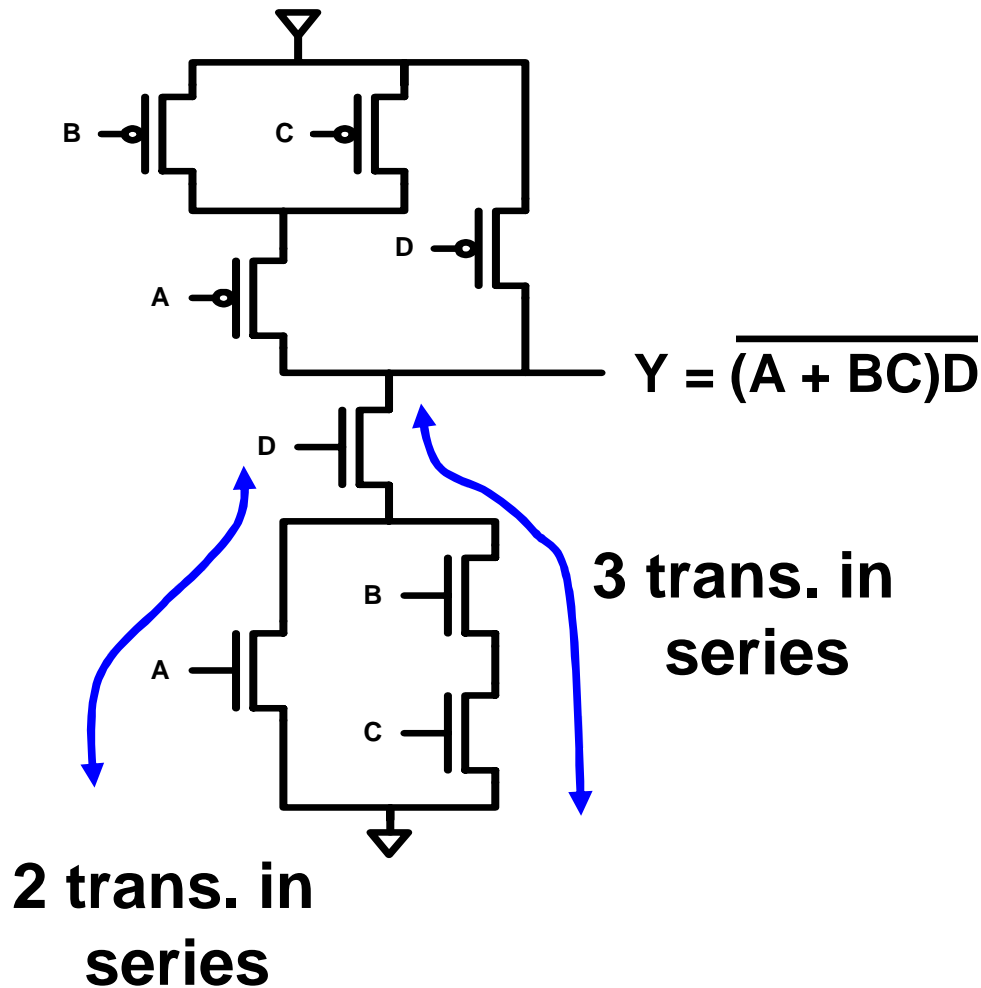


- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

CMOS Complex Gate Sizing

- Assume all transistors will have minimum length L
- Determine W_n for PDN transistor of inverter that would give the desired 'drive strength'
- For each transistor in PDN of complex gate do the following:
 - Determine the length l of the longest PDN chain in which it participates
 - Set $W = l W_n$
- Repeat this procedure for PUN, using W_p for PUN transistor of inverter.



Gate Sizing

  

- **W/L ratios**
- **what are the W/L of 2-input NAND for same drive strength?**

0-th order calculation


Exercise

 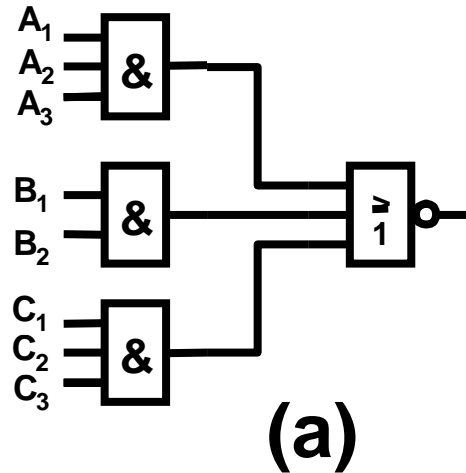

Exercise:

- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, **assume $PU/PD = 3$**
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same PU/PD)
- Compare sum of gate areas in (a) and (b). Note: area \sim width

Avoid Large Fan-In

 

C linear in N


R linear in N

Delay \propto **RC quadratic** in N

Empirical

Delay = $a_1 FI + a_2 FI^2 + a_3 FO$


Data-Dependent Timing

 

$$t_{PHL} = 0.69R_N C_L$$

$$t_{PLH} = 0.69R_P C_L$$

 You should be able to identify the transistor paths that charge or discharge C_L , and calculate resulting RC delay model, including effects of wires and fan-out



$$t_{PHL} = 0.69(R_N \times 2)C_L$$

$$t_{PLH} = 0.69R_p C_L$$



$$t_{PLH} = 0.69(R_p/2)C_L$$

Series connection

One input goes low

Two inputs go low,
parallel connection



Data-dependent VTC: 2nd order effects

  

- Charge at 'int'
- Body effect in M_2
- Short-circuit currents

- Don't need to be able to work with these effects
- But remember: there is more going on than shown by our simple, 1st order model

Data-dependent Timing (2).

 
 


Input Data Pattern	Delay (pS)
$A = B = 0 \rightarrow 1$	69
$A = 1, B = 0 \rightarrow 1$	62
$A = 0 \rightarrow 1, B = 1$	50
$A = B = 1 \rightarrow 0$	35
$A = 1, B = 1 \rightarrow 0$	76
$A = 1 \rightarrow 0, B = 1$	57


Ratioed logic

Pass transistor logic

Pseudo NMOS Ratioed Logic

  

 - ☺ Reduced area
- ☺ Reduced capacitances
- ☹ Increased V_{OL}
- ☹ Reduced noise margins
- ☹ Static dissipation



Ratioed Logic V_{OL} Computation.

$$I_{Dn} \text{ (linear)} = I_{Dp} \text{ (saturation)}$$

Exercise: verify these assumptions/steps

$$k_n \left((V_{DD} - V_{Tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left((-V_{DD} - V_{Tp})V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn})V_{OL} \approx k_p (-V_{DD} - V_{Tp})V_{DSAT}$$


Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} |V_{DSAT}| \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSAT}|$$

Pass-transistor and Pass-gate circuits


Pass Transistor Logic

 - Save area, capacitances
- Need complementary inputs (extra inverters)



But remember:

NMOS vs. PMOS, pull-down vs. pull-up

 

- PMOS is better pull-up
- NMOS is better pull-down

TUD/EE ET1205 EC/GS 0506 - © NvdM


09-May-06

5 combinational 12



Pass Transistor Logic

 - Save area, capacitances
- Need complementary inputs (might mean extra inverters)
- Reduced V_{OH} , noise margins




- $V_{OH} = V_{DD} - \left(V_{Tno} + \gamma \left(\left(\sqrt{|2\phi_f|} + V_{OH} \right) - \sqrt{|2\phi_f|} \right) \right)$
- Static dissipation in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by complementary pass gates (NMOS + PMOS parallel)

 Exercise: Why is there static dissipation in next conventional gate?

Pass Gates

- Remedy: use an N-MOS and a P-MOS in parallel




- Pass gates **eliminate** some of the **disadvantages** of simple pass-transistors
- But also some of the **advantages**
- Design remains a **trade-off!**

Pass-gate a.k.a. Transmission-gate


 
Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?



Pass Transistor Logic.

  - Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$ (S' is easier notation for S-bar = S-inverse = \overline{S})
- $Y = ((AS)' (BS)')'$ allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8) transistors (see also Katz, section 4.2)



Summary

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
 - **Complex Logic Gates**
 - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**