 


## MODULE 6



## SEQUENTIAL ELEMENTS

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 1

P	7.1	Introduction	326 – 327
P	7.1.1	Timing Metrics for Sequential Circuits	327 – 328
P	7.1.2	Classification of Memory Elements	328 – 330
	7.2	Static Latches and Registers	330
P	7.2.1	The Bistability Principle	330 – 332
P	7.2.2	Multiplexer-Based Latches	332 – 333
P	7.2.3	Master-Slave Edge-Triggered Register	333 – 335
I		Timing Properties of Multiplexer-Based Master ....	335 – 339
O	7.2.4	Low-Voltage Static Latches	339 – 341
P	7.2.5	Static SR Flip-Flops — Writing Data by Pure Force	341 – 344
I	7.3	Dynamic Latches and Registers	344
I	7.3.1	Dynamic Transmission-Gate Edge-Triggered Registers	344 – 346
O	7.3.2	C2MOS — A Clock-Skew Insensitive Approach	346 – 350
O	7.3.3	True Single-Phase Clocking Register (TSPCR)	350 – 354
O	7.4	Alternative Register Styles	354 – 358
P	7.5	Pipelining: An Approach to Optimize Sequential Circuits	358 – 360
P	7.5.1	Latch versus register based pipelines	360
O	7.5.2	NORA-CMOS A logic style for pipelined circuits	361 – 363
	7.6	Nonbistable Sequential Circuits	
P	7.6.1	The Schmitt Trigger	364 – 367
O	7.6.2	Monostable Sequential Circuits	367 – 368
I	7.6.3	Astable Circuits	368 – 370
O	7.7	Perspective: Choosing a Clocking Strategy	370 – 371
P	7.8	Summary	371 – 372

§ 7.5 Will be discussed with module 08 timing design

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 2


## Sequential Elements - Outline

- Background
  - Timing, terminology, classification
- Static Flipflops
  - Latches
  - Registers
- Dynamic Flipflops
  - Latches
  - Registers
- Non-bistable elements
  - Schmitt Trigger

■ Much of this material has already been covered in DS1 (v Genderen), Katz Section 6.1  
 ■ Here we will add transistor-level implementation, dynamic flipflops



[Sorin Cotofana]

 


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 3
 
## FSM with Positive Edge Triggered Registers



- Flip-flops provide **memory/state**
- VLSI uses predominantly **D-type flip-flops**

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 4

## Memory elements

- Store a **temporary value**, remember a **state**
- Typically controlled by **clock**.
- May have load signal, etc.
- In CMOS, memory is created by:
  - **capacitance** (dynamic);
  - **feedback** (static).
- Also see [http://en.wikipedia.org/wiki/Flip-flop\\_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 5

## Variations in memory elements

- Form of required clock signal.
- How behavior of data input around clock affects the stored value.
- When the stored value is presented to the output.
- Whether there is ever a combinational path from input to output.

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 6

### Timing Metrics Reminder

$t_{c-q}$  : delay from clock (edge) to Q  
 $t_{su}$  : setup time  
 $t_{hold}$  : hold time  
 $t_{plogic}$  : worst case propagation delay of logic  
 $t_{cd}$  : best case propagation delay (contamination delay)  
 $T$  : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 7

### Nomenclature

**Beware for confusion**

	Katz (CS1)	Rabaey
Latch	Level sensitive storage element	Level sensitive storage element
Register	Group of storage elements	Edge triggered storage element
Flip Flop	Edge triggered storage element	Bistable element using feedback

$CLK = CK = \phi$

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 8

### Latches vs. Registers

<p><b>Latch</b></p> <div style="border: 1px solid black; padding: 5px;"> <p>Level-sensitive</p> <p>Transparent when clock is active</p> <p>Clock active high: positive latch</p> <p>Clock active low: negative latch</p> <p>Faster, smaller</p> </div>	<p><b>Register</b></p> <div style="border: 1px solid black; padding: 5px;"> <p>Edge-triggered</p> <p>Input and output isolated</p> <p>Sampling on 0 → 1 clock: positive edge triggered</p> <p>Sampling on 1 → 0 clock: negative edge triggered</p> <p>Safer</p> </div>
--	--

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 9

### Static vs. Dynamic Memory Elements.

<p><b>Static</b></p> <div style="border: 1px solid black; padding: 5px;"> <p>Operate through positive feedback</p> <p>Preserve state as long as power is on</p> <p>Can work when clock is off</p> <p>More robust</p> </div>	<p><b>Dynamic</b></p> <div style="border: 1px solid black; padding: 5px;"> <p>Store charge on (parasitic) capacitor</p> <p>Charge leaks away (in milliseconds)</p> <p>Clock must be kept running (for periodic refresh)</p> <p>Faster, smaller</p> </div>
---	---

Rabaey: bistable elements are called Flip Flops

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 10

### Static Latches and Registers

- Latches → can be gated or not
- Registers

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 11

### Positive Feedback: Bi-Stability

- |Loop-gain| in A,B << 1
- A,B: stable points
- |Loop-gain| in C >> 1
- C: meta-stable point

§ 7.2.1

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 12

### SR-Latch

Truth Table 1:

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

← forbidden

Truth Table 2:

S	R	Q	$\bar{Q}$
1	1	Q	$\bar{Q}$
0	1	1	0
1	0	0	1
0	0	1	1

← forbidden

§ 7.2.5

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 13

### Clocked SR-Latch

Truth Table:

S	R	Q	$\bar{Q}$
1	1	Q	$\bar{Q}$
0	1	1	0
1	0	0	1
0	0	1	1

← forbidden

- Katz: gated latch
- Positive latch (active on CK high)
- Naïve implementation
- 16 transistors
- D latch requires 9xN, 9xP
- Larger area, cost, power

- Construction of D-latch
- D-latch, D-register most common in VLSI

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 14

### CMOS Clocked SR-Latch

Truth Table:

S	R	Q	$\bar{Q}$
1	1	Q	$\bar{Q}$
0	1	1	0
1	0	0	1
0	0	1	1

← forbidden

$\phi = CK$

- Save 6 PMOS transistors and 2 NMOS
- D-latch requires 7 x N, 3 x P (instead of 9xN, 9xP)

**Q:** Is this a **ratioed** design or not? Does it consume static power?

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 15

### Multiplexer-Based Latches

Negative Latch

Multiplexer

Restoration

Recirculating latch

§ 7.2.2

Mux-based latches much more common in modern dig. IC's

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 16

### Recirculating latch

- Quasi-static, static on one phase
- Feedback restores value
- Requires 4 x N, 4 x P, minimum size (compare 7 x N, 3 x P, non-minimum size)
- $\phi_1$  and  $\phi_2$  inverse but should be non-overlapping
- Can suffer from charge sharing (when  $\phi$  not non-overlapping)
- $C_{in}$  and  $C_{load}$  form communicating vessels when Output connected directly to input

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 17

### Insensitive for Charge Sharing

- Non ratioed
- High load to CLK

Uni-directionality of this inverter prevents coupling between Q and D

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 18

### Recirculating NMOS Latch.

- Degraded 1 at X
- Lower noise margin, higher delay, power

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 19

### Latch Designs can Suffer from Race Problems

Signal can race around during  $\phi = 1$

§ 7.2.3

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 20

### Registers

- Not transparent—use multiple storage elements to isolate output from input.
- Master-slave, edge triggered principle

§ 7.2.3

§ 6.1.4-5

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 21

### Master-slave operation

- $\phi = 0$ :
  - master latch is disabled;
  - slave latch is enabled, but master latch output is stable,
  - so output does not change.
- $\phi = 1$ :
  - master latch is enabled, loading value from input;
  - slave latch is disabled, maintaining old output value.

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 22

CMOS Flip-Flop Construction

CMOS technology allows a very different approach to flip-flop design and construction. Instead of using logic gates to connect the clock signal to the master and slave sections of the flip-flop, a CMOS flip-flop uses transmission gates to control the data connections. (See the CMOS gate structure page for a closer look at the transmission gate stack.)

The result is that a controllable flip-flop can be built with only inverters and transmission gates — a very small and simple structure for an IC.

The basic CMOS D flip-flop is shown below:

www.play-hookey.com

clickable



link

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 24
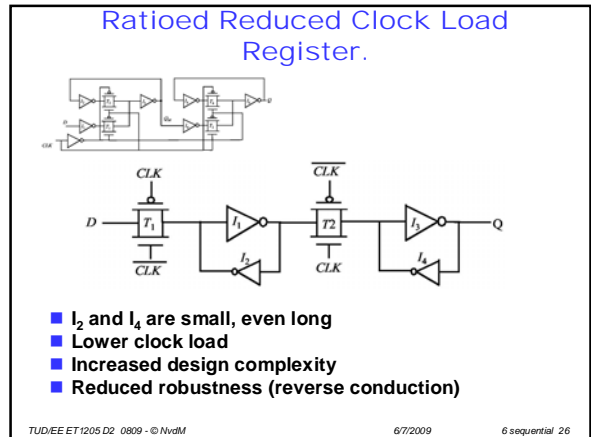 
### Transistor Level Master Slave Positive Edge Triggered Register

- Robust Design
- Can eliminate  $I_1$  and  $I_2$ , however, they make design more robust (avoid charge sharing, robust input)
- High Clock Load (8 x)

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 24






### Non-bistable Elements


- Schmitt Trigger

Was discussed in P-lab

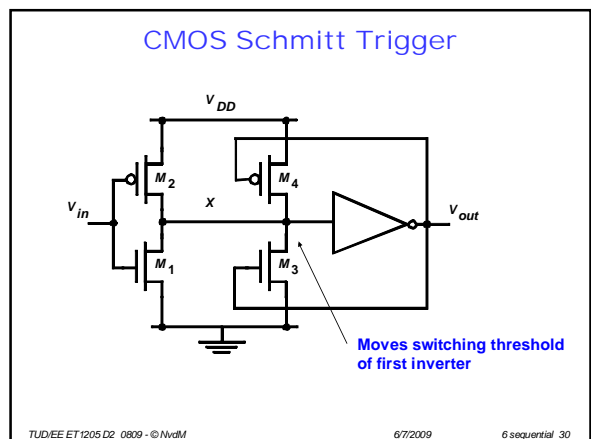  TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 6 sequential 27



## Schmitt Trigger Simulated VTC

 


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 31

## CMOS Schmitt Trigger (2).

 

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 32

## Summary

- **Background**
  - Timing, terminology, classification
- **Static Flipflops**
  - Latches
  - Registers
- **Dynamic Flipflops**
  - Latches
  - Registers
- **Non-bistable elements**
  - Schmitt Trigger

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

6 sequential 33