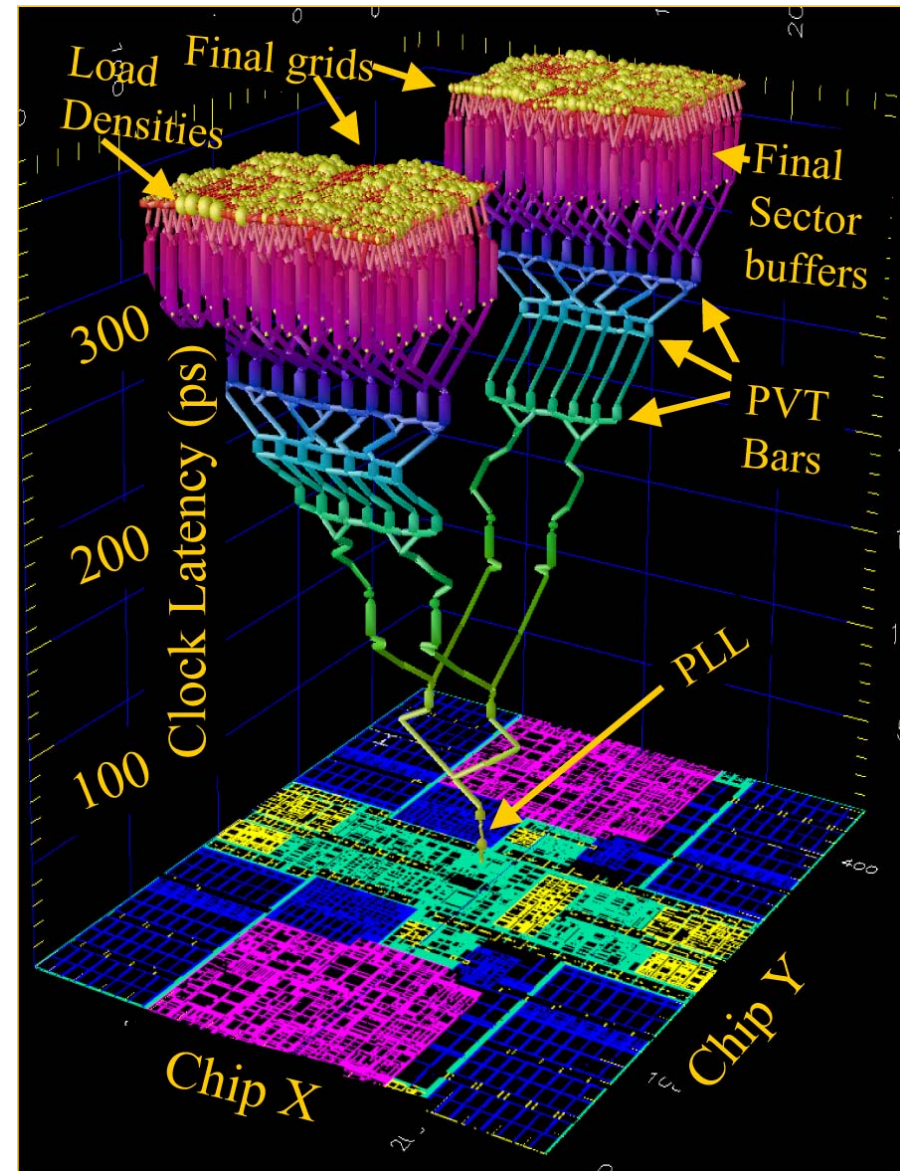


# MODULE 7

## TIMING DESIGN



# Course Material for Timing Design

<b>P</b>	<b>10.1</b>	<b>Introduction</b>	<b>492</b>
<b>I</b>	<b>10.2</b>	<b>Timing Classification</b>	<b>492 – 495</b>
<b>P</b>	<b>10.3.1</b>	<b>Synchronous Timing Basics</b>	<b>495 – 500</b>
<b>I</b>		<b>Clock Jitter</b>	<b>500</b>
<b>I</b>		<b>The combined impact of Skew and Jitter</b>	<b>501 – 502</b>
<b>I</b>	<b>10.3.2</b>	<b>Sources of Skew and Jitter</b>	
<b>I</b>	<b>10.3.3</b>	<b>Clock Distribution Techniques</b>	
<b>O</b>	<b>10.3.4</b>	<b>Latch-Based Clocking</b>	<b>516 – 518</b>
<b>O</b>	<b>10.4-10.7</b>	<b>Self-Timed Circuit Design – Future Directions</b>	<b>519 – 551</b>
<b>P</b>	<b>7.5 – 7.5.1 (!)</b>	<b>Pipelining</b>	<b>358-361</b>

***Material from Chapter 10, one section from Chapter 7***

# Outline


- **Timing Design Background and Motivation**
  - **Delay variations, impact**
  - **Sequential circuits, synchronous design**
  - **Pipelining, metrics reminder**
- **The Clock Skew Problem**
- **Controlling Clock Skew**
- **Case Study**

**Get basic appreciation of some  
system level design issues**

# Design of LARGE Integrated Circuits

- **Correct signal**
  - **Logic value**
  - **Right level (restoring logic, ...)**
- **At right place**
  - **Interconnect (R, C, L)**
  - **Busses**
  - **Off-chip drivers, and receivers**
- **At right time**
  - **How to cope with (uncertain) delay**

# Case Study: IBM Power6 CPU

 


- introduced 21 may 2007
- 64 bit, dual core
- 790 million transistors
- 4.7 (5+) GHz
- 65nm SOI, 10 Cu levels interconnect
- 2 Cores
- 8 MB on-chip level2 cache
- processor bandwidth: 300GB/sec
- 1953 signal I/O, 5449 power I/O

<http://en.wikipedia.org/wiki/POWER6>

<http://www-03.ibm.com/press/us/en/pressrelease/21580.wss>



# IBM 65nm SOI Technology

 


**Gate oxide: 1.05 nm ~ 5 atom layers in Si (!!)**


# Uncertain Delay

- **Data-dependent Delay**
- **Short and long combinational paths**
- **Device parameters variations (§3.4)**
  - Batch to batch  $V_t$  threshold voltage
  - Wafer to wafer  $k'$  transconductance
  - Die to die  $W, L$  dimensions
- **Supply Variations**
  - IR drop,  $dl/dt$  drop, ringing,
- **Interconnect Delay**
  - Don't know length of line during logic design
  - Delay at begin of line smaller than at end
  - Interconnect parameter variability

# Delay Along a Wire (Module 3)

 

 - Signal on RC line exhibits **finite propagation** speed
- **Delay** at beginning of line smaller than at end
- Follows from solving **diffusion equation**
- **Elmore delay model** also predicts propagation behavior (only approximately)





$$T_{Di} = \sum_{k=1}^N R_{ik} C_k$$

- **Exercise:** draw this graph for  $N = 3$ ,  $N = 6$ , or use integration to solve limit for  $N \rightarrow \infty$



# Delay of Clock Wire

  

$$R = 0.07 \Omega/\square, C = 0.04 \text{ fF}/\mu\text{m}^2$$


$$W = \text{Width}, r = R/W, c = C \cdot W$$

**5ns compares with 200 MHz**
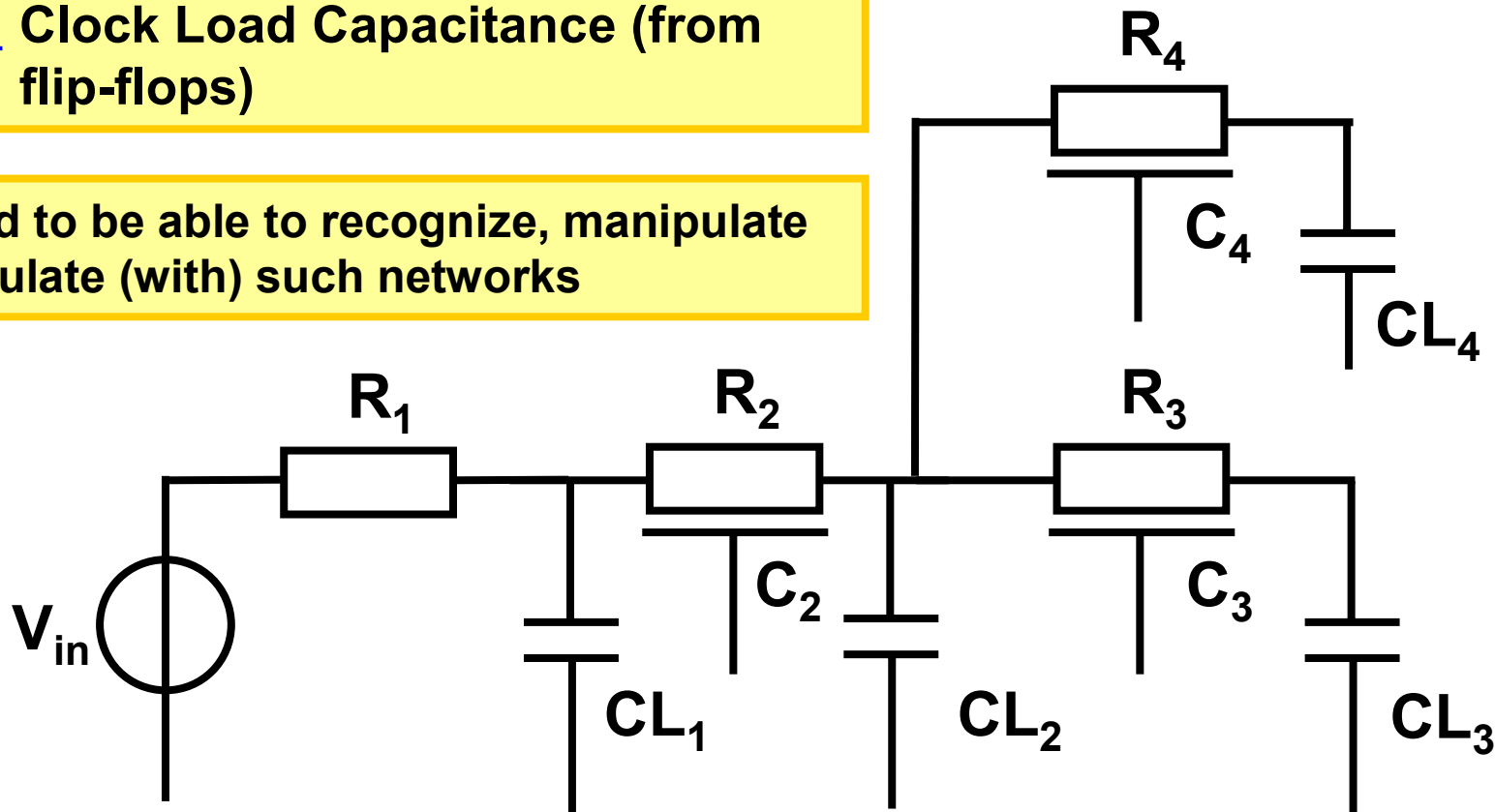
# Canonical Clock Tree Network

$R_1$  Clock Driver Output Resistance  
 $R_2$ - $R_4$  Clock Line Segment Resistance  
 $C_2$ - $C_4$  Clock Line Segment Capacitance  
 $CL_1$ - $CL_4$  Clock Load Capacitance (from flip-flops)

You need to be able to recognize, manipulate and calculate (with) such networks



# Impact of Uncertain Delay.

- **Combinational circuits** will eventually **settle** at correct output values when inputs are stable
- **Sequential circuits**
  - **Have state**
  - **Must guarantee storing of correct signals at correct time**
  - **Require ordered computations**

# Sequential Circuits

- Sequential circuits require **ordered computation**
- Several ways for **imposing ordering**
  - ✓ ■ **Synchronous (clock)**
  - ✗ ■ **Asynchronous (unstructured)**
  - ✗ ■ **Self-timed (negotiation)**

- **Clock works like an orchestra conductor**







# Synchronous Design

- **Global Clock Signal**
- **Synchronicity may be defeated by**
  - **Delay uncertainty** in clock signal
  - **Relative timing errors: clock skew**
  - **Slow** logic paths
  - **Fast** logic paths

# Timing Metrics Reminder

 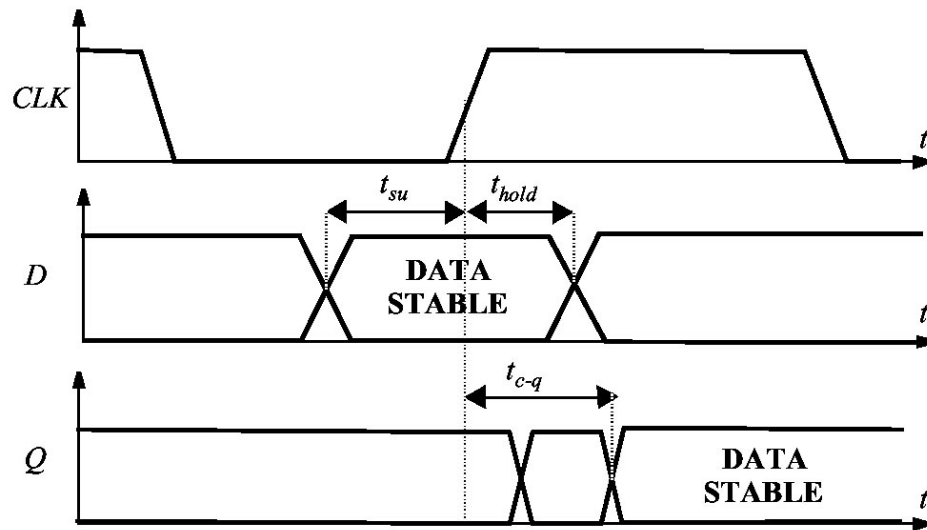

$t_{c-q}$  : delay from clock (edge) to Q

$t_{su}$  : setup time

$t_{hold}$  : hold time

$t_{plogic}$  : worst case propagation delay of logic


$t_{cd}$  : best case propagation delay  
(contamination delay)

$T$  : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

# Sequential Circuit Timing.

 


$$T_{clk} > t_{c-q} + t_{plogic} + t_{su}$$

$$t_{plogic} = t_{p,add} + t_{p,abs} + t_{p,log}$$

**How to reduce  $T_{clk}$ ?**

# Pipelined Laundry System


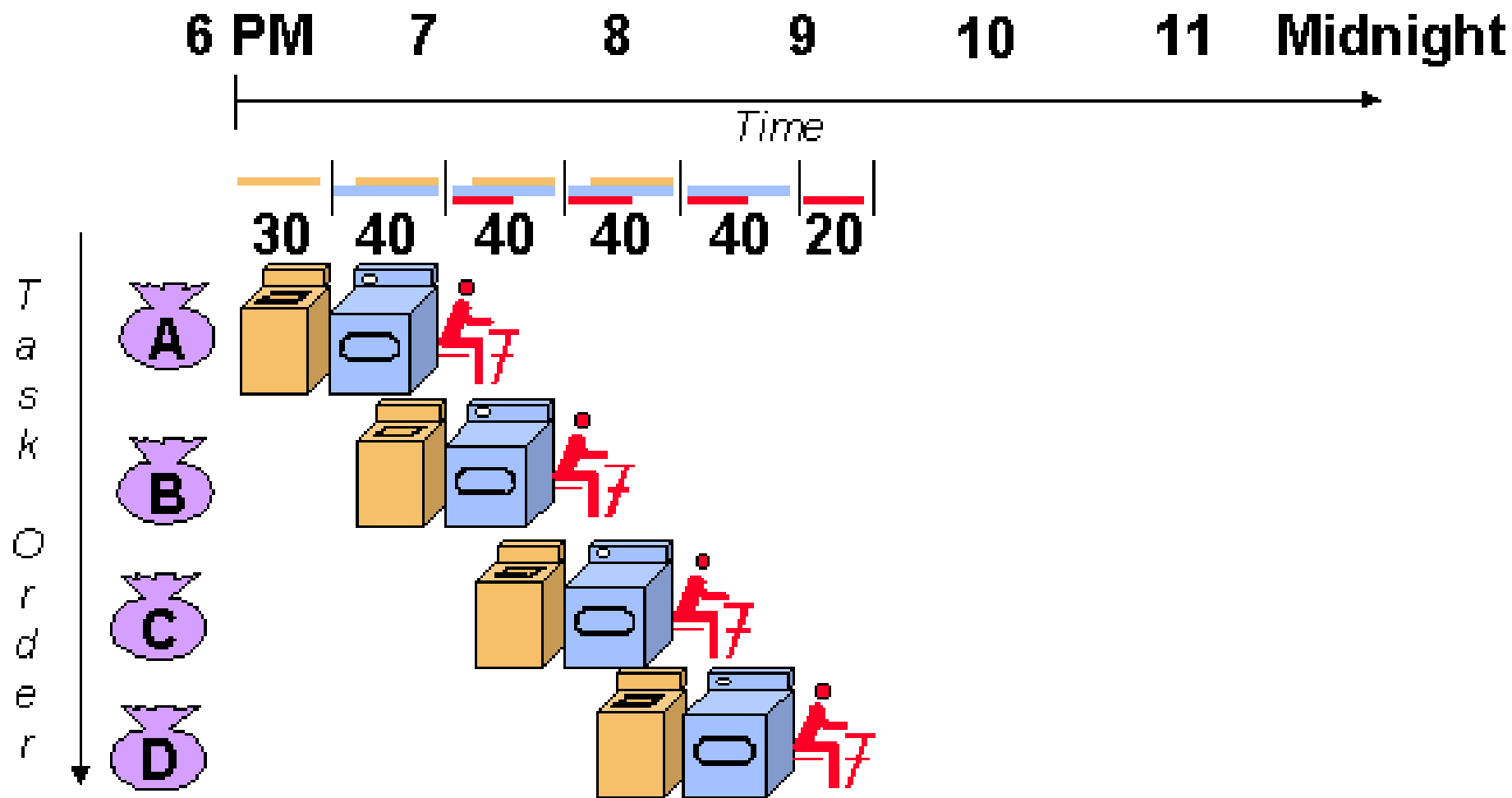


Also: <http://en.wikipedia.org/wiki/Pipelining>

From <http://cse.stanford.edu/class/sophomore-college/projects-00/risc/pipelining/index.html>  
 which credited <http://www.ece.arizona.edu/~ece462/Lec03-pipe/>



# Pipelining

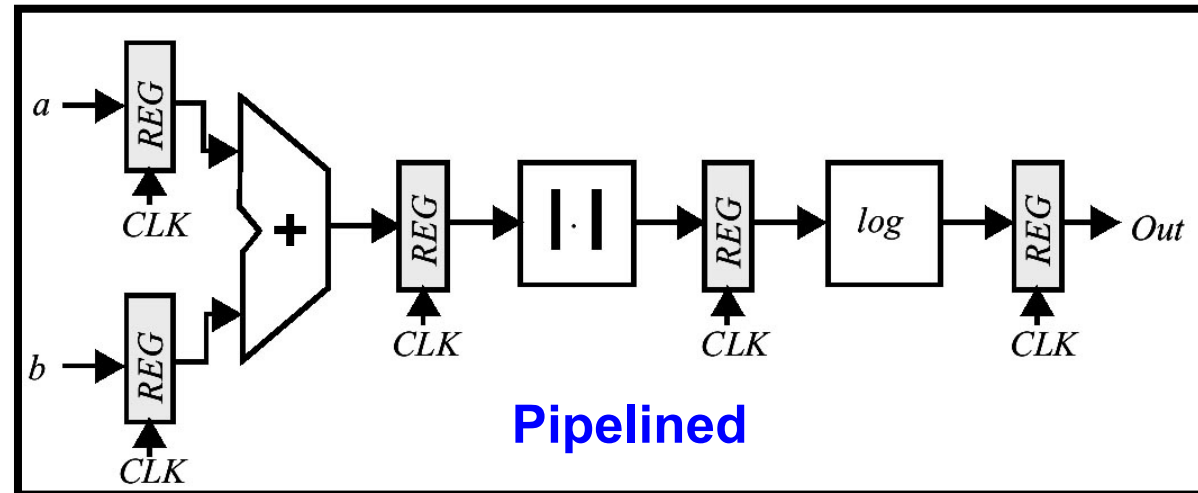 

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log( a_1 + b_1 )$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log( a_2 + b_2 )$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log( a_3 + b_3 )$



$$T_{clk} > t_{c-q} + \max(t_{p,add}, t_{p,abs}, t_{p,log}) + t_{su}$$

- Improve resource utilization
- Increase functional throughput


# Pipelining Observations.

- Very popular/effective measure to increase functional **throughput and resource utilization**
- At the cost of increased **latency**
- All high performance microprocessors excessively use pipelining in **instruction fetch-decode-execute sequence**
- Pipelining efficiency may fall dramatically because of **branches** in program flow
  - Requires emptying of pipeline and **restarting**
  - Partially remedied by **advanced branch prediction techniques**
- But all is dictated by **GHz marketing drive**
  - All a customer asks is: **“How many GHz?”**
  - Or says: **“Mine is ... GHz!”**

**Bottom line: more flip-flops, greater timing design problems**

 
# The Clock Skew Problem

- In Single Phase Edge Triggered Clocking
- In Two Phase Master-Slave Clocking



# The Clock Skew Problem



**Clock Rates  $\gg$  1 Ghz in CMOS**

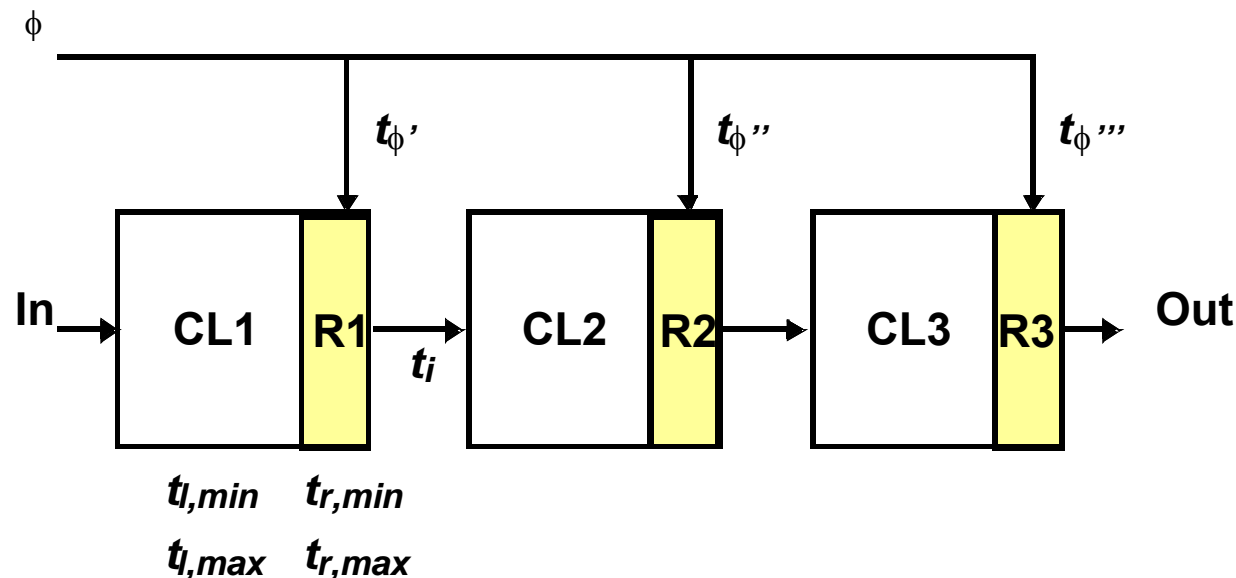


- **Clock Edge Timing Depends upon Position**
  - **Because clock network forms distributed RC line with lumped load capacitances at multiple sites (see earlier slide)**
- **(Relative) Clock Skew  $\delta = t_{\phi}'' - t_{\phi}'$**
- **Clock skew can take significant portion of  $T_{clk}$**



# Positive and Negative Skew

  
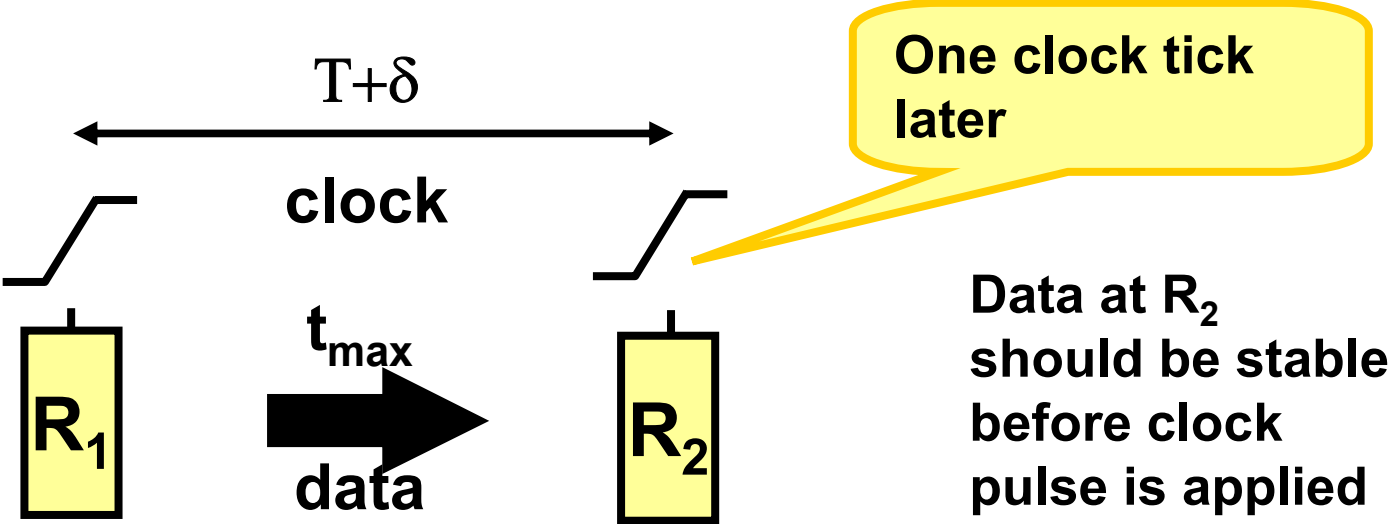
# Edge-Triggered Slow Path Skew Constraint



**Timing constraint** ( $t_i$  = interconnect delay)


$$T + \delta \geq t_{\max} = t_{p,\text{logic}} + t_i + t_{c-q,\text{max}} + t_{\text{su}}$$

Internal delay of flip-flop

$$T \geq t_{\max} - \delta$$

■ **Minimum Clock Period Determined by Maximum Delay between Latches minus skew**
 
# Edge-Triggered Fast Path Skew Constraint



## Timing constraint

$$\delta \leq t_{min} = t_{cd,logic} + t_i + t_{c-q,min} - t_{hold}$$

- **Maximum Clock Skew Determined by Minimum Delay between Latches**

# Clock Constraints in Edge-Triggered Logic.

$$T \geq t_{\max} - \delta$$

$$\delta \leq t_{\min}$$

## ■ Observe:

- Minimum Clock Period Determined by Maximum Delay between Registers minus clock skew
- Maximum Clock Skew Determined by Minimum Delay between Registers

## ■ Conclude:

- Positive skew must be bounded
- Negative skew reduces maximum performance

# Controlling Clock Skew


## Case Study



# Countering Clock Skew Problems

- Routing the clock in **opposite direction** of data (negative skew)
  - Hampers performance
  - Dataflow not always uni-directional
  - Maybe at sub circuit (e.g. datapath) level
  - Other approaches needed at global chip-level
  - Useful skew (or beneficial skew) is serious concept
- Enlarging **non-overlap periods** of clock [only with two-phase clocking]
  - Hampers performance
  - Can theoretically always be made to work
  - Delay in clock network may require impractical/excessively large scheduled  $T_{\phi_{12}}$  to guarantee minimum  $T_{\phi_{12}}$  everywhere across chip
  - Is becoming less popular for large high performance chips

# Dataflow not unidirectional

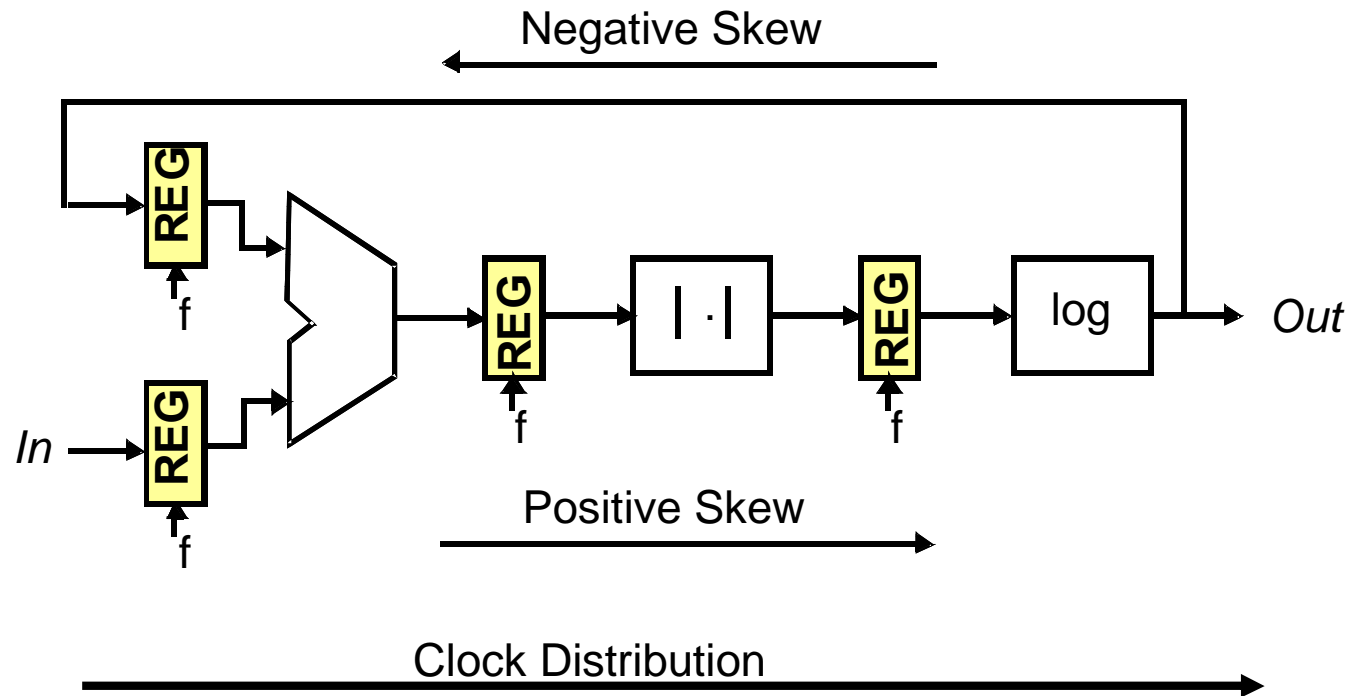


- Data and Clock Routing
- Cannot unambiguously route clock in opposite direction of data
- Need bounded skew



# Need bounded Skew

- **Bounded skew most practical measure to guarantee functional correctness without reducing performance**
- **Clock Network Design**
  - **Interconnect material**
  - **Shape of clock-distribution network**
  - **Clock driver, buffers**
  - **Clock-line load**
  - **Clock signal rise and fall times**
  - **...**


# H-tree Clock Network

 

- All blocks equidistant from clock source  $\Rightarrow$  **zero (relative) skew**
- **Sub blocks** should be small enough to ignore intra-block skew
- In practice perfect H-tree shape **not realizable**



**Observe: Only Relative Skew Is Important**
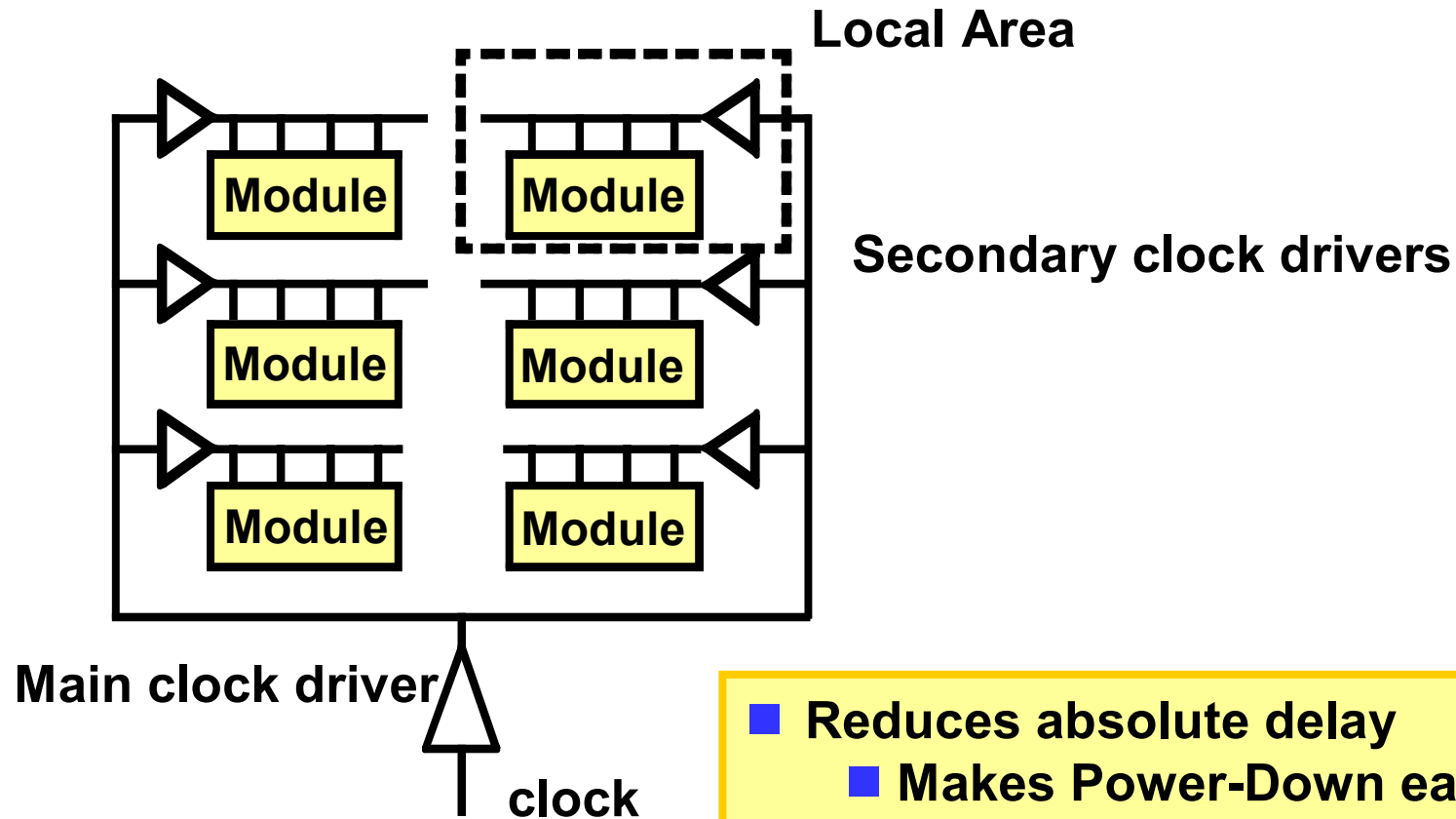
# Clock Network with Distributed Buffering



- Reduces absolute delay
  - Makes Power-Down easier
  - Easier of-chip communication
- Sensitive to variations in Buffer Delay


# Power6 Clock Distribution

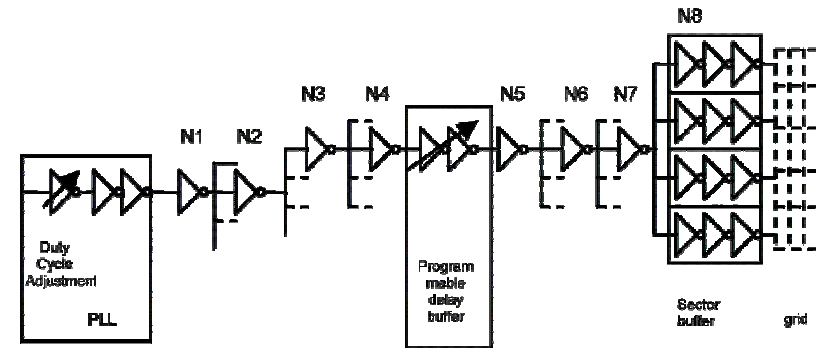 


■ Latency ~ cycle time

friedrich, isscc 2007


# Power6 Clock Distribution

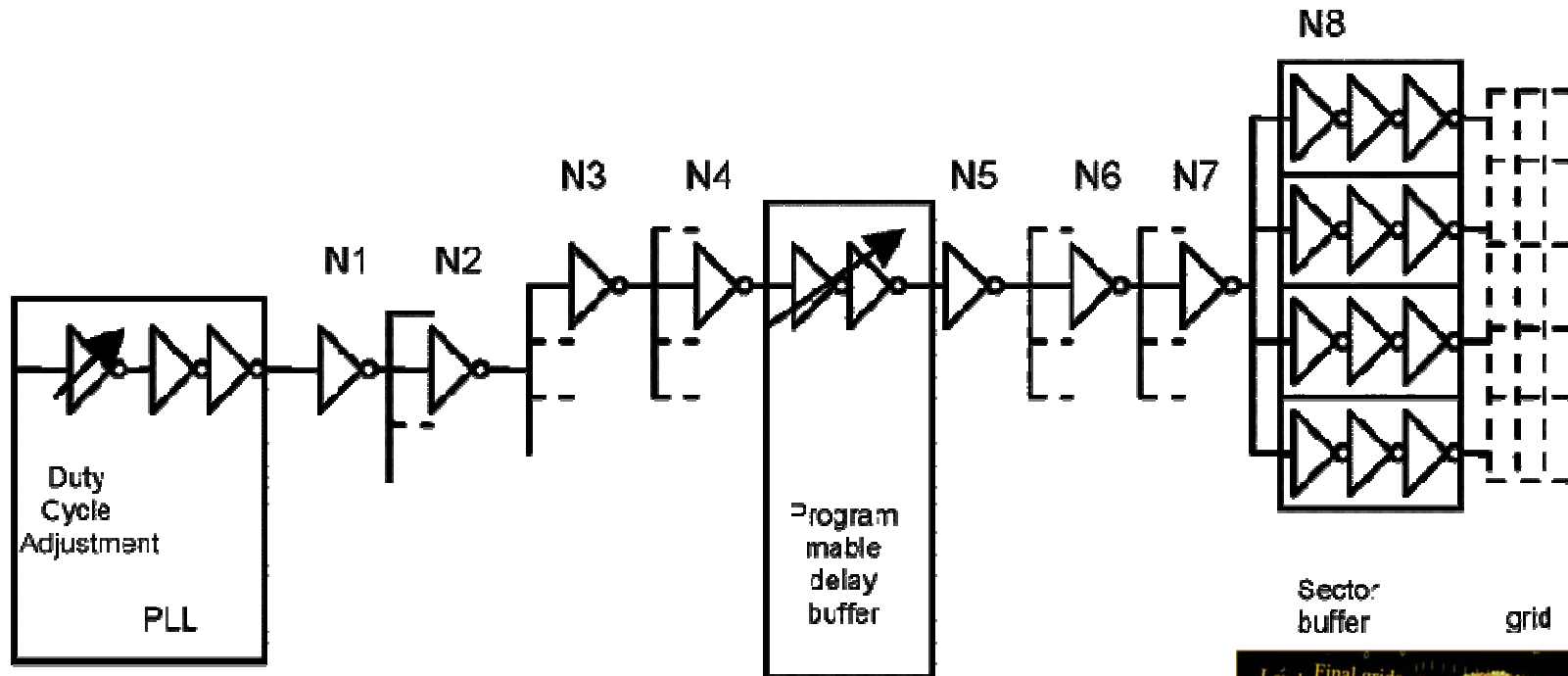

stolt, jssc 2008

 

# IBM Power6 Physical Design Flow

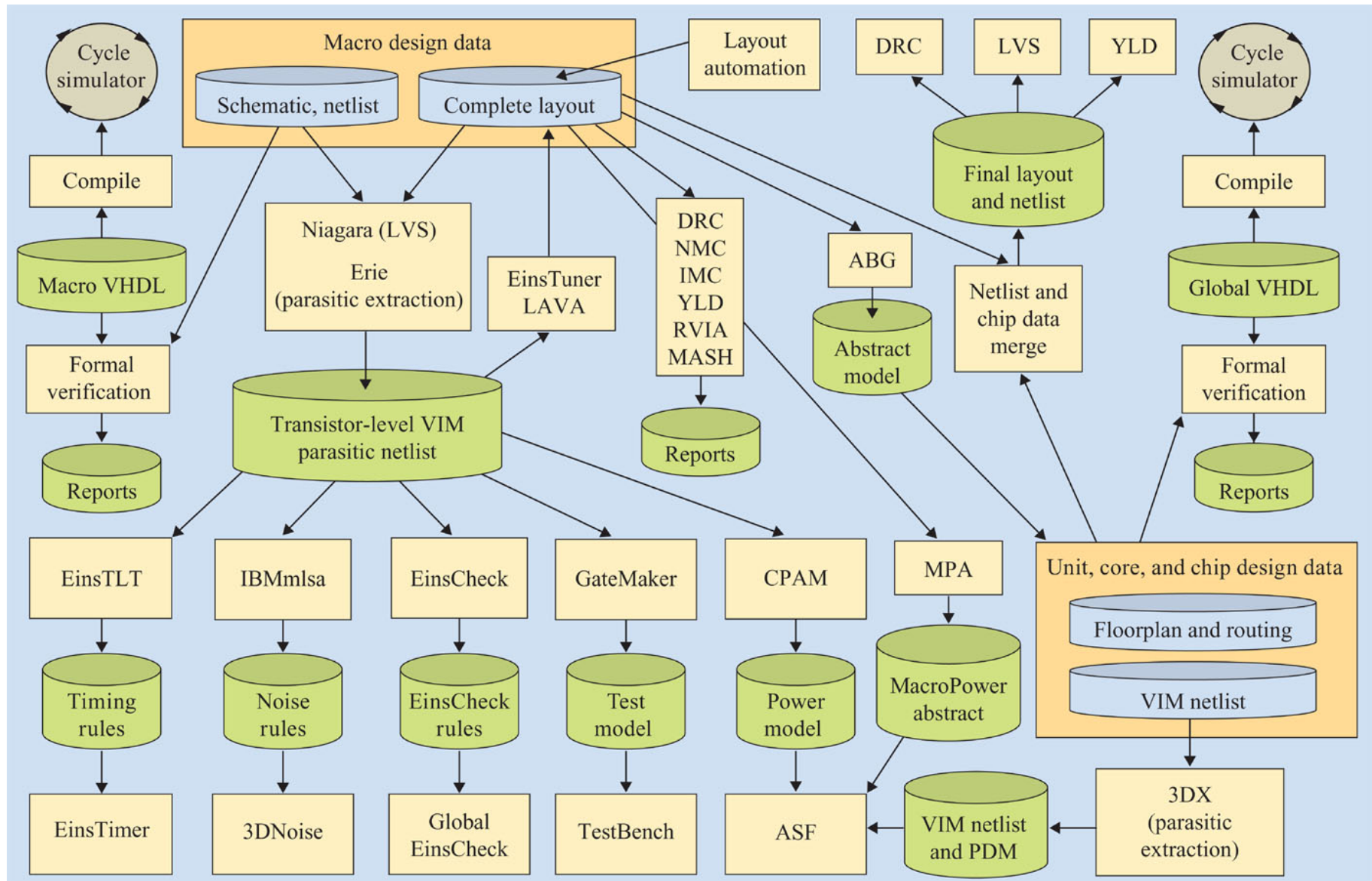

berridge, ibmjrd 2007

# Timing Design.

- **Clocking Scheme is important design decision**
- **Influences**
  - **Power**
  - **Robustness**
  - **Ease of design, design time**
  - **Performance**
  - **Area, shape of floor plan**
- **Needs to be planned early in design phase**
- **But is becoming design bottle neck nevertheless**
  - **Clock frequencies increase**
  - **Die sizes increase**
  - **Clock skew significant fraction of  $T_{clk}$**
- **Alternatives**
  - **Asynchronous or self-timed**

Not in this course





# Summary

- **Timing Design Background and Motivation**
  - **Delay variations, impact**
  - **Sequential circuits, synchronous design**
  - **Pipelining, metrics reminder**
- **The Clock Skew Problem**
- **Controlling Clock Skew**
- **Case Study**

**Got basic appreciation of some  
system level design issues?**