 


MODULE 7

TIMING DESIGN



TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 1

Course Material for Timing Design

P	10.1	Introduction	492
I	10.2	Timing Classification	492 – 495
P	10.3.1	Synchronous Timing Basics	495 – 500
I		Clock Jitter	500
I		The combined impact of Skew and Jitter	501 – 502
I	10.3.2	Sources of Skew and Jitter	
I	10.3.3	Clock Distribution Techniques	
O	10.3.4	Latch-Based Clocking	516 – 518
O	10.4-10.7	Self-Timed Circuit Design – Future Directions	519 – 551
P	7.5 – 7.5.1 (!)	Pipelining	358-361

Material from Chapter 10, one section from Chapter 7

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 2

Outline

- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
- The Clock Skew Problem
 - Controlling Clock Skew
- Case Study

Get basic appreciation of some system level design issues

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 3

Design of LARGE Integrated Circuits


- Correct signal
 - Logic value
 - Right level (restoring logic, ...)
- At right place
 - Interconnect (R, C, L)
 - Busses
 - Off-chip drivers, and receivers
- At right time
 - How to cope with (uncertain) delay

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 4

Case Study: IBM Power6 CPU

 

- introduced 21 may 2007
- 64 bit, dual core
- 790 million transistors
- 4.7 (5*) GHz
- 65nm SOI, 10 Cu levels interconnect
- 2 Cores
- 8 MB on-chip level2 cache
- processor bandwidth: 300GB/sec
- 1953 signal I/O, 5449 power I/O

<http://en.wikipedia.org/wiki/POWER6>


<http://www-03.ibm.com/press/us/en/pressrelease/21580.wss>

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 5

IBM 65nm SOI Technology

 

Gate oxide: 1.05 nm ~ 5 atom layers in Si (!!)

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 6

Uncertain Delay


- Data-dependent Delay
- Short and long combinational paths
- Device parameters variations (§3.4)
 - Batch to batch V_t threshold voltage
 - Wafer to wafer k' transconductance
 - Die to die W, L dimensions
- Supply Variations
 - IR drop, dI/dt drop, ringing,
- Interconnect Delay
 - Don't know length of line during logic design
 - Delay at begin of line smaller than at end
 - Interconnect parameter variability

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 7

Delay Along a Wire (Module 3)

 


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 8

Delay of Clock Wire

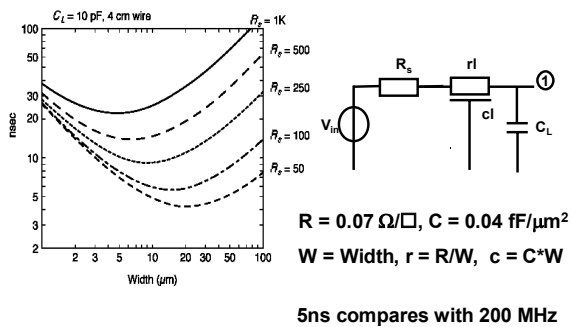


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 9

Canonical Clock Tree Network

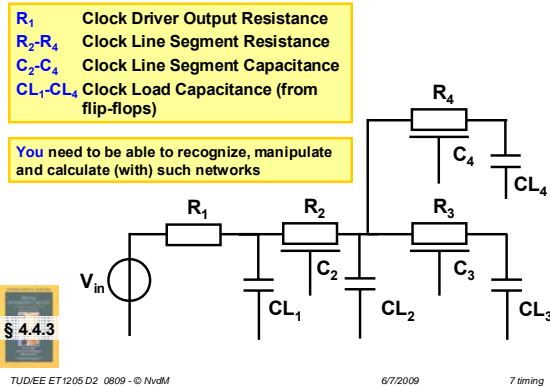

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 10

Impact of Uncertain Delay

- Combinational circuits will eventually settle at correct output values when inputs are stable
- Sequential circuits
 - Have state
 - Must guarantee storing of correct signals at correct time
 - Require ordered computations

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 11

Sequential Circuits

- Sequential circuits require ordered computation
- Several ways for imposing ordering
 - ✓ ■ Synchronous (clock)
 - ✗ ■ Asynchronous (unstructured)
 - ✗ ■ Self-timed (negotiation)

■ Clock works like an orchestra conductor



TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 12

Synchronous Design


- Global Clock Signal
- Synchronicity may be **defeated** by
 - Delay uncertainty in clock signal
 - Relative timing errors: **clock skew**
 - Slow logic paths
 - Fast logic paths

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 13

Timing Metrics Reminder

 

- t_{c-q} : delay from clock (edge) to Q
- t_{su} : setup time
- t_{hold} : hold time
- t_{plogic} : worst case propagation delay of logic
- t_{cd} : best case propagation delay (contamination delay)
- T : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 14

Sequential Circuit Timing.

 


How to reduce T_{clk} ?

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 15

Pipelined Laundry System

 


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 16

Pipelining

 

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$	$ a_1 + b_1 $	
2	$a_2 + b_2$	$ a_2 + b_2 $	
3	$a_3 + b_3$	$ a_3 + b_3 $	$\log(a_3 + b_3)$
4	$a_4 + b_4$	$ a_4 + b_4 $	$\log(a_4 + b_4)$
5	$a_5 + b_5$	$ a_5 + b_5 $	$\log(a_5 + b_5)$

- $T_{clk} > t_{c-q} + \max(t_{p,add}, t_{p,abs}, t_{p,log}) + t_{su}$
- Improve resource utilization
 - Increase functional throughput

§ 7.5

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 17

Pipelining Observations.

- Very popular/effective measure to increase functional **throughput and resource utilization**
- At the cost of increased **latency**
- All high performance microprocessors excessively use pipelining in **instruction fetch-decode-execute sequence**
- Pipelining efficiency may fall dramatically because of **branches** in program flow
 - Requires emptying of pipeline and **restarting**
 - Partially remedied by **advanced branch prediction techniques**
- But all is dictated by GHz marketing drive
 - All a customer asks is: "How many GHz?"
 - Or says: "Mine is ... GHz!"

Bottom line: **more flip-flops, greater timing design problems**

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 18

The Clock Skew Problem

- In Single Phase Edge Triggered Clocking
- In Two Phase Master-Slave Clocking




TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 19

The Clock Skew Problem

Clock Rates >> 1 Ghz in CMOS

 


- Clock Edge Timing Depends upon Position
 - Because clock network forms distributed RC line with lumped load capacitances at multiple sites (see earlier slide)
- (Relative) Clock Skew $\delta = t_{p''} - t_{p'}$
- Clock skew can take significant portion of T_{clk}

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 20

Positive and Negative Skew

 


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 21

Edge-Triggered Slow Path Skew Constraint

 

Timing constraint (t_i = interconnect delay)
 $T + \delta \geq t_{max} = t_{p,logic} + t_i + t_{c-q,max} + t_{su}$ (Internal delay of flip-flop)

$T \geq t_{max} - \delta$


■ **Minimum Clock Period Determined by Maximum Delay between Latches minus skew**

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 22

Edge-Triggered Fast Path Skew Constraint

 

Timing constraint
 $\delta \leq t_{min} = t_{cd,logic} + t_i + t_{c-q,min} - t_{hold}$

■ **Maximum Clock Skew Determined by Minimum Delay between Latches**

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 23

Clock Constraints in Edge-Triggered Logic.

$T \geq t_{max} - \delta$ $\delta \leq t_{min}$

- **Observe:**
 - Minimum Clock Period Determined by Maximum Delay between Registers minus clock skew
 - Maximum Clock Skew Determined by Minimum Delay between Registers
- **Conclude:**
 - Positive skew must be bounded
 - Negative skew reduces maximum performance

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 24

Controlling Clock Skew

Case Study



§10.3.3

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 25

Countering Clock Skew Problems


- Routing the clock in **opposite direction** of data (negative skew)
 - Hampers performance
 - Dataflow not always uni-directional
 - Maybe at sub circuit (e.g. datapath) level
 - Other approaches needed at global chip-level
 - Useful skew (or beneficial skew) is serious concept
- Enlarging **non-overlap periods** of clock [only with two-phase clocking]
 - Hampers performance
 - Can theoretically always be made to work
 - Delay in clock network may require impractical/excessively large scheduled $T_{\phi 12}$ to guarantee minimum $T_{\phi 12}$ everywhere across chip
 - Is becoming less popular for large high performance chips

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 26

Dataflow not unidirectional

 

- Data and Clock Routing
- Cannot unambiguously route clock in opposite direction of data
- Need bounded skew

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 27

Need bounded Skew


- Bounded skew most practical measure to guarantee functional correctness without reducing performance
- Clock Network Design
 - Interconnect material
 - Shape of clock-distribution network
 - Clock driver, buffers
 - Clock-line load
 - Clock signal rise and fall times
 - ...

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 28

H-tree Clock Network

 

- All blocks equidistant from clock source \Rightarrow **zero (relative) skew**
- **Sub blocks** should be small enough to ignore intra-block skew
- In practice perfect H-tree shape **not realizable**


Observe: Only Relative Skew Is Important

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 29

Clock Network with Distributed Buffering



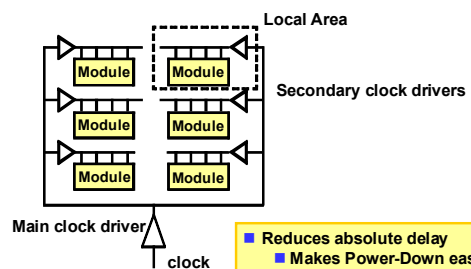


- Reduces absolute delay
 - Makes Power-Down easier
 - Easier of-chip communication
- Sensitive to variations in Buffer Delay

TUD/EE ET1205 D2 0809 - © NvdM

6/7/2009

7 timing 30

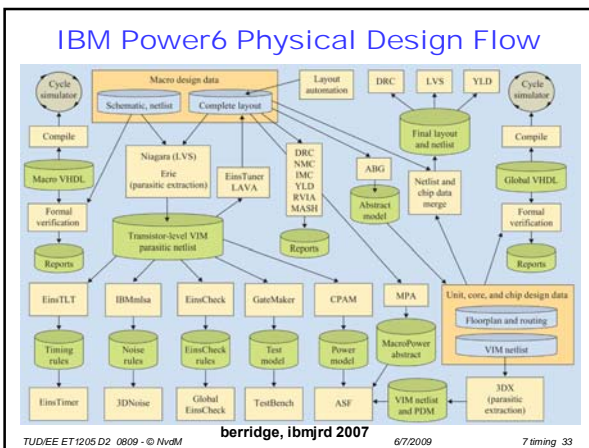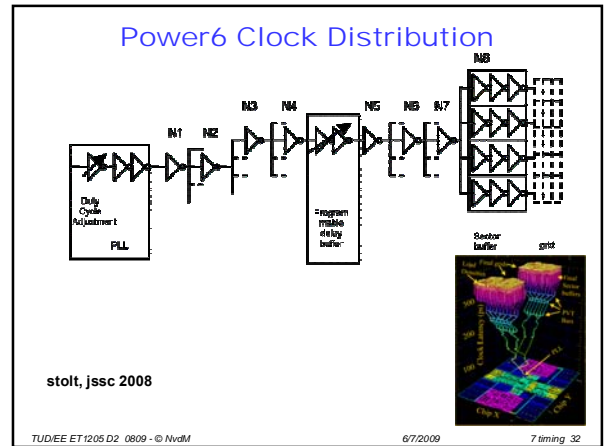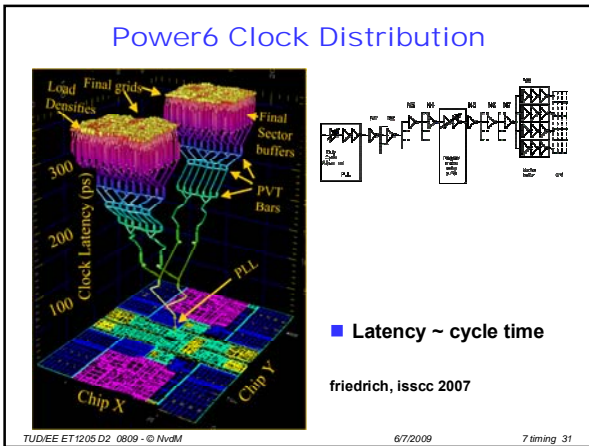

- ### Timing Design.
- Clocking Scheme is important design decision
 - Influences
 - Power
 - Robustness
 - Ease of design, design time
 - Performance
 - Area, shape of floor plan
 - Needs to be planned early in design phase
 - But is becoming design bottle neck nevertheless
 - Clock frequencies increase
 - Die sizes increase
 - Clock skew significant fraction of T_{clk}
 - Alternatives
 - Asynchronous or self-timed
- Not in this course 😊
- TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 7 timing 34

- ### Summary
- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
 - The Clock Skew Problem
 - Controlling Clock Skew
 - Case Study
- Got basic appreciation of some system level design issues?**
- TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 7 timing 35