

## MODULE 8

### MODULARITY

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 1

## Course Material for Modularity

### Chapter 11

P = primair, I = illustratie, O = overslaan

P	11.1	Introduction	560
P	11.2	Datapaths in Digital Processor Architectures	560-561
P	11.3	The Adder	561
P	11.3.1	The Binary Adder: Definitions	561-564
P	11.3.2	The Full Adder: Circuit Design Consideration	564-578
I	11.3.2	Manchester Carry Chain Adder	568-570
O	11.3.3	The Binary Adder: Logic Design Considerations	571-586
P	11.4	The Multiplier	586
P	11.4.1	The Multiplier: Definitions	586-587
P	11.4.2	Partial-Product Generation	587-589
P	11.4.3	Partial-Product Accumulation	589-592
O		The Tree Multiplier	592-593
I	11.4.4	Final Addition	593-594
P	11.5	The Shifter	595
P	11.5.1	Barrel Shifter	595-596
P	11.5.2	Logarithmic Shifter	596
O	11.6	Other Arithmetic Operators	596-600
O	11.7	Power and speed trade-offs	600-618
P	11.8	Perspective: Design as a Trade-off	618-619
P	11.9	Summary	619-620

2008-2009: the multiplier and shifter (§11.4-5) will be skipped

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 2

## Outline

- Background on Modular Design
  - Hierarchy, reuse, regularity
  - Architecture, bit-slicing
- Adder Design
- Multiplier Design
- Shifter Design
- Layout Strategies (regularity)
- Design as a Trade-Off

contains a lot of reminders


Get further appreciation of some system level design issues

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 3

## Arithmetic Circuits

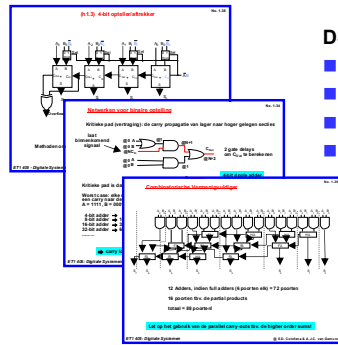

DS:

- Number systems
- Intro of full-adders
- Critical paths
- Intro comb. multiplier

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 4

## Adder Design

- Adders are fundamental building blocks
  - Digital filtering (DSP): MP3 en/decoder, GSM, GPS, ...
  - Data processing
  - Multiplication
  - Address arithmetic
  - ...
- Good performance is key
- Many architectures
  - ✓ Static adder
  - ✗ Dynamic adder (Manchester Carry Chain)
  - ✗ Pipelined Adder
  - ✗ Carry-Bypass, Carry Lookahead, Carry Select
  - ✗ ...
- Design trade-offs, optimization
  - ✓ Architecture level
  - ✓ Logic level
  - ✓ Circuit level
  - ✓ Layout level

Most effective  
↑  
↓  
Least effective




TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 5

## Full-Adder

 

C <sub>in</sub>	B	A	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Add three one-bit numbers  
Equivalently: count # 1's in A, B, C<sub>i</sub>  
Output as 2-bit number <C<sub>out</sub>S>

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009


8 modularity 6

### The Ripple-Carry Adder

 

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 7

### The Binary Adder

 

$$S = A \oplus B \oplus C_i = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$$

AND-OR expressions for sum and carry

$$C_o = AB + BC_i + AC_i$$

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 8

### Naïve Complementary CMOS Implementation


- Use DeMorgan to convert AND-OR expressions for SUM and CARRY to NAND-NAND

PQ + RS =  $\overline{\overline{PQ} \overline{RS}}$  (example)

Q: What is advantage of NAND-NAND over NOR-NOR? Consider drive strength vs. area

 **Transistor Count**

- 3 x INVERT
- 3 x NAND-2
- 5 x NAND-3
- 1 x NAND-4



Can do better using more clever boolean factoring, but...

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 9

### Full-Adder Boolean Factoring


$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i = ABC_i + \bar{C}_i(A + B + C_i)$$

$$C_o = AB + BC_i + AC_i = AB + (A + B)C_i$$

C <sub>in</sub>	B	A	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 10
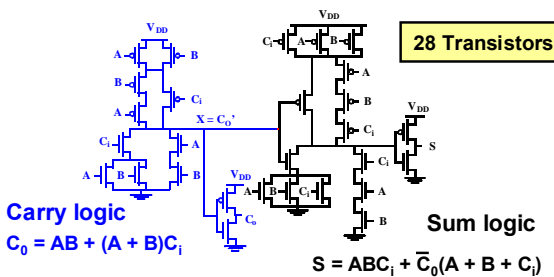
### Improved Complementary Static Full Adder



TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 11

### Ripple-Carry Adder Delay

 

- Worst case delay through full carry path (ripple carry)
- Linear with the number of bits (N)
- $T_{adder} = (N-1) T_{carry} + \text{Max}(T_{carry}, T_{sum})$
- $T_{adder} = O(N)$  "T<sub>adder</sub> is of Order N" means linear with N
- Goal: Make the fastest possible carry path circuit

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 12

### Adder Evaluation

**Carry Chain:**

- Long PMOS chains
- High C at X
- 2 (inverting) stages

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 13

### Inversion Property

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_0(A, B, C_i) = C_0(\bar{A}, \bar{B}, \bar{C}_i)$$

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 14

### Minimize Critical Path by Reducing Inverting Stages

- Can eliminate inverter in carry from each FA
- Need 2 different types of cells, but both with inverting carry – will require only one stage per bit

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 15

### Eliminate Inverter In Carry.

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 16

### Multiplier Design

- Multipliers are fundamental building blocks too
  - Digital Signal Processing (DSP): MP3 en/decoder, GSM, GPS, ...
  - Data processing
  - Address arithmetic
  - ...
- Good performance is key, often they are the performance bottleneck
- Multipliers are complex arrays of adders
- Many architectures
  - ✓ Basic Array Multiplier
  - ✗ Bit-serial
  - ✗ Booth-encoding multiplier
  - ✗ Baugh-Wooley multiplier
  - ✗ Wallace tree multiplier
  - ✗ ...
- Design trade-offs, optimization
  - ✓ Architecture level, Logic level, Circuit level, Layout level

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 17

### The Binary Multiplication

Example:  $42 \times 11 = 462$

Each partial product formed by bitwise AND operation

Partial products are shifted before being added

Conclusion: similar to decimal multiplication

$$X_{10} \times Y_{10} = \sum_{i=0}^{M-1} \left( \sum_{j=0}^{N-1} X_i Y_j 10^{i+j} \right)$$

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 18

### The Array Multiplier

$X = 1010$   
 $Y = 1011$   
 $X \times Y_0 \times 2^0 = 1010$   
 $X \times Y_1 \times 2^1 = 1010$   
 $X \times Y_2 \times 2^2 = 01110$   
 $X \times Y_3 \times 2^3 = 10110$   
 $X \times Y = 1001110$

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 19

### The MxN Array Multiplier — Critical Path

$t_{mult} \approx [(M - 1) + (N - 2)]t_{carry} + (N - 1)t_{sum} + t_{and}$   
 Requires comparable carry and sum delays

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 20

### Adder Cells in Array Multiplier

#### Identical Delays for Carry and Sum

A	B	C <sub>i</sub>	S	C <sub>o</sub>	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

$P = A \oplus B$   
 If  $P = 1$  then  $S = \bar{C}_i$ ,  $C_o = C_i$   
 If  $P = 0$  then  $S = C_i$ ,  $C_o = A$

$2 \times$  transmission gate XOR for  $P, \bar{P}$  (Fig 11.17)  
 Multiplexers for  $S, C_o$

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 21

### Carry-Save Multiplier

$t_{mult} \approx (N - 1)t_{carry} + t_{and} + t_{merge}$  (assuming  $t_{add} \approx t_{carry}$ )  
 Use fastest possible adder for final vector merging  
 Will be larger, use more power, etc, but need only one row!

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 22

### Multiplier Floorplan

X signals are routed vertically across each column ("broadcast")  
 Y signals are broadcasted horizontally across rows

**Regularity!**

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 23

### Multipliers — Summary.

- Optimization Goals Different Vs Binary Adder
- Once Again: Identify Critical Path
- Other possible techniques
  - Logarithmic versus Linear (Wallace Tree Mult)
  - Data encoding (Booth)
  - Pipelining

**GLIMPSE AT SYSTEM LEVEL OPTIMIZATION**

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 24

## Shifter Design


- Shifters are fundamental building blocks too
  - Floating point units
  - Scalers
  - Multiplication by constant numbers (add and shift)
  - ...
- Constant shifting is only interconnect
- Programmable shifting requires active circuitry
- Usually dominated by interconnect
- Architectures
  - Barrel Shifter
  - Logarithmic Shifter
  - ...
- Design trade-offs, optimization
  - Architecture level, Logic level, Circuit level, Layout level
  - Simpler compared to Adder, Multiplier, hence less rewarding
- Good example of pay-off of structural design

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 25

## The Binary Shifter

 


- Multibit shifters by cascading
- M stages for M-bit shift
- Complex and slow for larger M
- More structured approach needed

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 26

## The Barrel Shifter

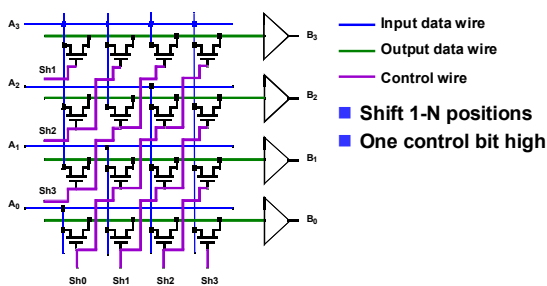


- Need M stages for M-bit shift
- Signal passes only one pass-transistor => delay?
- Area Dominated by Wiring, not (always) by # transistors

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 27

## 4x4 Barrel Shifter

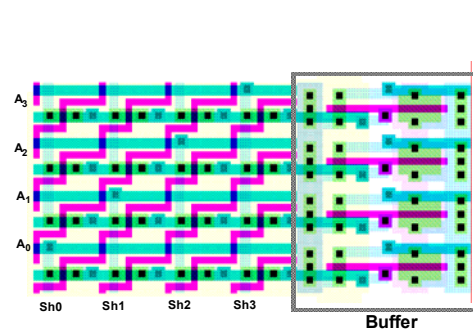


TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 28

## Logarithmic Shifter

 


- Section i shifts  $2^{(i-1)}$  bits
- Need only  $\log_2 M$  stages for M-bit shift

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 29

## 0-7 bit Logarithmic Shifter

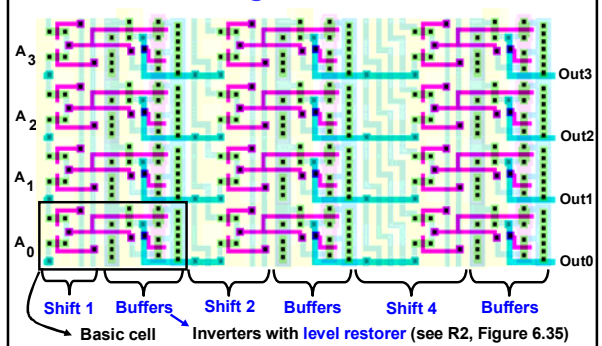

Exercise: decipher layout of basic cell and draw transistor circuit

TU/EE ET1205 D2 0809 - © NvdM

6/7/2009

8 modularity 30

### Size Comparison

- $M$  is maximum bit displacement,  $K = \log_2 M$
- For large  $M$ , width is dominated by vertical metal wires
- Disregard buffer size, **only count vertical wires**
- Barrel shifter needs 1 control and 1 data wire per stage
- # Wires:  $2M$
- Log shifter needs 2 control +  $2^{i-1}$  data wires for stage  $i$
- # Wires:  $2K + (1 + 2 + 4 + \dots + 2^{K-1}) = 2K + 2^K - 1 = 2 \log_2 M + M - 1$
- Log shifter will have smaller area for larger  $M$ !

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 31

### Speed Comparison.

**Exercise**

- Discuss the relative speeds of both shifters, as a function of  $M$  (see discussion in book). Consider:
  - Number of sections
  - Input capacitance at the buffers (including diffusion areas of the driving pass-transistors)
  - Number of buffers (necessity of buffers)
  - The number of pass-transistors the signal has to pass
  - ...

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 32

### Layout Strategies (regularity)

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 33

### Bit-Sliced Design

- Tile identical processing elements
- Rows for each bit
- Columns for each function
- Control from top (often with *control-slice*)
- (Example orientation)

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 34

### Layout Strategies for Bit-Sliced Datapaths




Approach I — Signal and power lines parallel

Approach II — Signal and power lines perpendicular

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 35
 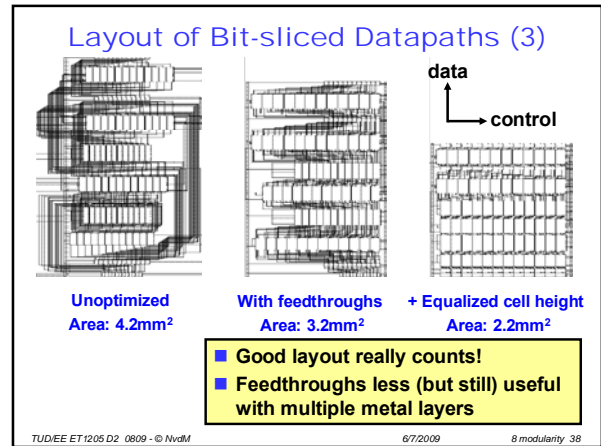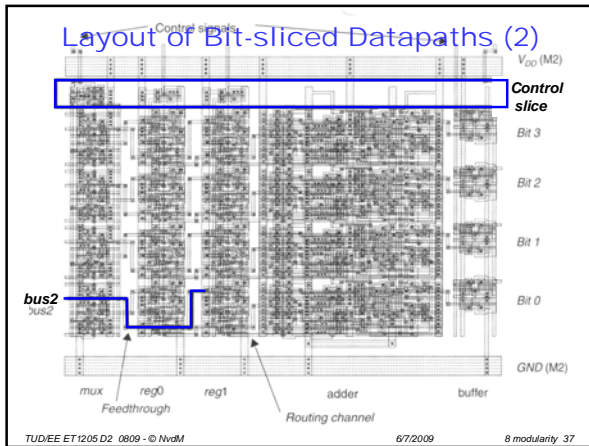
### Layout of Bit-sliced Datapaths

TUD/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 36



### VLSI Design.

- Select **right structure**
- Determine and optimize **critical timing path** for speed
- Optimize rest for **area** (cost) and/or **power** and/or **design time**
- Consider **layout** aspects

**Regularity and modularity are a VLSI designer's best friends**

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 40

### Summary.

- Background on Modular Design
  - Hierarchy, reuse, regularity
  - Architecture, bit-slicing
- Adder Design
- Multiplier Design
- Shifter Design
- Layout Strategies (regularity)
- Design as a Trade-Off

**Got further appreciation of some system level design issues?**

TU/EE ET1205 D2 0809 - © NvdM 6/7/2009 8 modularity 41