

Antwoorden HS 5

1 a $w_n = 1.0 \mu\text{m}$ $l_n = 0.25 \mu\text{m}$
 $w_p = 0.5 \mu\text{m}$ $l_p = 0.25 \mu\text{m}$

1 c nee

2 b $0.34 < \frac{k_p}{k_n} < 0.41$ (V_M kan bepaald worden met HSPICE)

3 a $V_{IL} = 0.607V$ $V_{IH} = 0.87V$

c $V_{ML} = 0.607V$ $V_{MH} = 1.63V$

d (1) $\rightarrow 0W$ (2) $\rightarrow 81.75mW$

g hogere R geeft grotere gain, maar ook assymetrie (VTC schaft naar links)

4 a $t_{phh} = 155\text{ns}$ }
 $t_{phl} = 9.05\text{ns}$ } aug 82 ns

c static: $82mW$

dynamic: $f_{max} = \frac{1}{82\text{ns}} = 12.2 \text{ MHz} \Rightarrow 0.225mW$

5 a

$$\text{Circuit A} \rightarrow V_{OH} = 1.765V$$

$$V_{OL} = 0.263V$$

$$V_M = 1.269V$$

$$\text{Circuit B} \rightarrow V_{OH} = 2.5V$$

$$V_{OL} = 0V$$

$$V_M = 1.095V$$

5 c verwoelf (is SPICE simulatie voor nodig)

5 d CMOS beter (ckt B)

6 a $V_x = 1.7014V$

b (snelheid)verzadiging of ckt

c $V_{out\ max} = V_{DD} - 2V$

d $\left. \begin{array}{l} 1) V_M = 0.745V \\ 2) V_M = 1.325V \end{array} \right\} 0.745 \leq V_M \leq 1.325$

7 a 2.5V (linear)

b ~~return~~ $\approx 12mV$

c $P_{static} = 21.55\mu W$