 


Interconnect



Course Material for Interconnect


Chapter 4, 2nd ed.

P = primair, I = Illustratie, O = overslaan


P	4.1	Introduction	136
P	4.2	A First Glance	136 – 138
P	4.3	Interconnect Parameters	138 – e.v.
O		So far we have (onder example 4.2)	147 – 148
O	4.3.3	Inductance	148 – 150
P	4.4	Electrical Wire Models	150 – 156
I	4.4.4	Distributed rc line – <i>hiervoor is vervangende stof</i>	156 – 159 (1)
O	4.4.5	The transmission line	159 – e.v.
O	4.5	Spice wire models	170 – 171
I	4.5.3	Perspective: a look into the future	171 – 174

Replacement voor Distributed RC line: Elmore Delay


Interconnect

 

 - Wires are **not ideal** interconnections
- They may have non-negligible **capacitance, resistance, inductance**
- These are called **wire parasitics**
- Can **dominate** performance of chip
- Must be accounted for during **design**
- Using **approximate models**
- Detailed **post-layout verification** also necessary




Wires

 

Interconnect Hierarchy




Cross-section of IBM 0.13 μ process

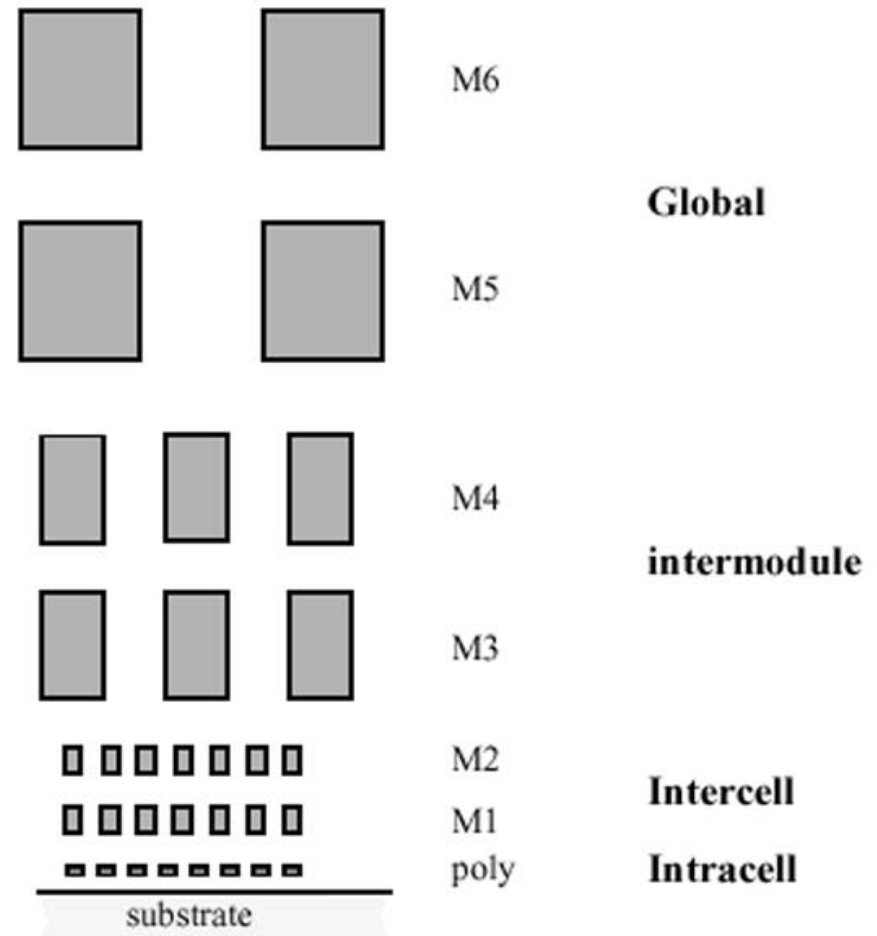

Example Interconnect Hierarchy for typical 0.25 μ process (Layer Stack)

45 nm Interconnect Technology

 

8 interconnect layers in 45 nm technology

[Ingerly – iitc – 2008]

Outline




- **Capacitance**
 - Area/perimeter model, coupling**
- **Resistance**
 - Sheet resistance**
- **Interconnect delay**
 - Delay metrics, rc delay, Elmore delay**

Capacitance

- Area/perimeter model, coupling




Wake Up! Models ahead!

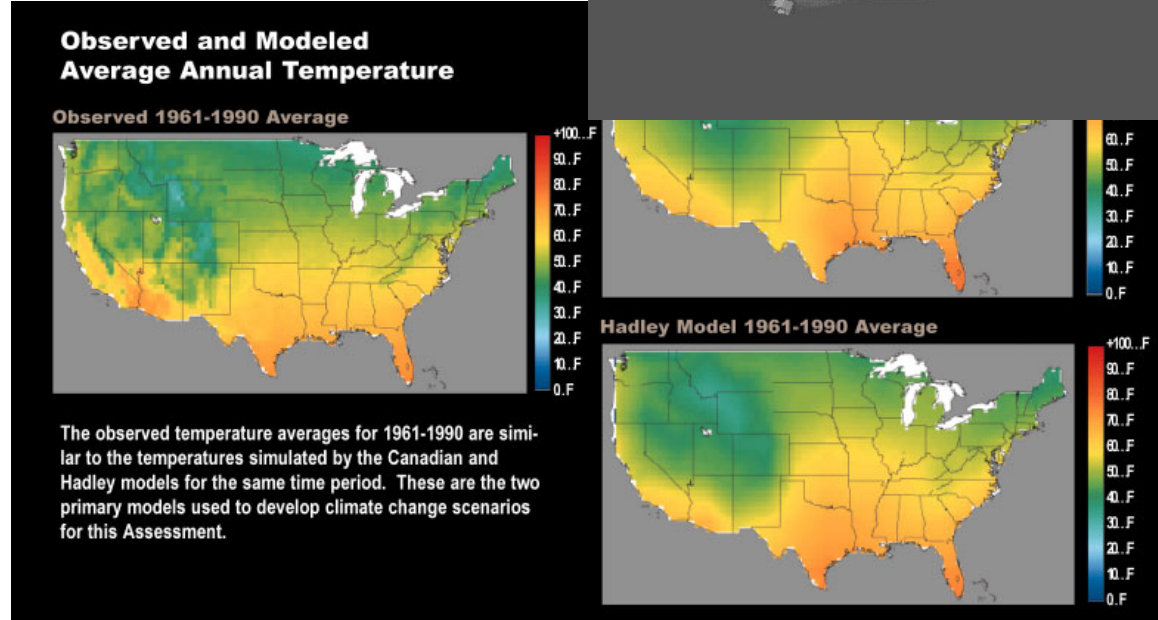  

6 entries found for **model**.
To select an entry, click on it.

model[1,noun]
model[2,verb]
model[3,adjective]
animal model
role model
Watson-Crick model

Go

Main Entry: **¹mod·el** 

Pronunciation: ˈmɑː-dəl

Function: *noun*

Etymology: Middle French *modelle*, from Old Italian *modello*, from (assumed) Vulgar Latin *modellus*, from Latin *modulus* small measure, from *modus*

1 *obsolete* : a set of plans for a building

2 *dialect British* : COPY, IMAGE

3 : structural design <a home on the *model* of an old farmhouse>

4 : a usually miniature representation of something; *also* : a pattern of something to be made

5 : an example for imitation or emulation

6 : a person or thing that serves as a pattern for an artist; *especially* : one who poses for an artist

7 : ARCHETYPE

8 : an organism whose appearance a mimic imitates

9 : one who is employed to display clothes or other merchandise : MANNEQUIN

(as an atom) that cannot be directly observed

12 : a system of postulates, data, and inferences presented as a mathematical description of an entity or state of affairs

13 : VERSION


13 : VERSION

Modeling


- An **abstraction** of (the properties) of something to help **understanding** and **predicting** its behavior
- **Domain Specific**: weather, climate, economy, stock market, ...
- Different models for something to **answer different questions**
- **Black-Box** modeling vs. **Physically Based**

After Einstein:

 
<a model> should be as simple as possible, but not simpler



Wire Capacitance - Parallel Plate

 
 
$$C = \frac{\epsilon_0 \epsilon_r W l}{d}$$




$$\frac{C}{l} = \epsilon_0 \epsilon_r \frac{w}{h}$$

$$\epsilon_0 = 8.85 \text{ pF/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

Wire Capacitance – Fringing Fields

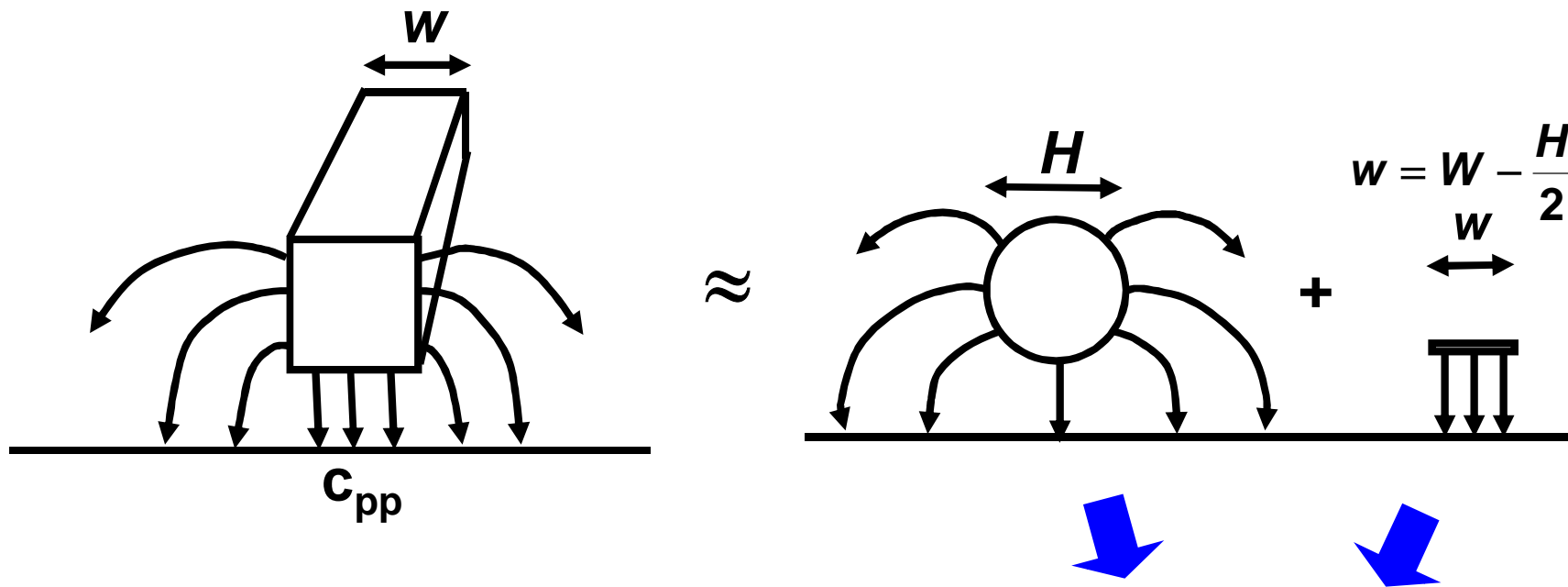

$$C_{wire} = C_{fringe} + C_{pp} = \frac{2\pi\epsilon d_i}{\log(t_{di}/H)} + \frac{W\epsilon d_i}{t_{di}}$$

- Works reasonably well in practice
- Not directly applicable for interconnects with varying widths


Wire Capacitance – Area/Perimeter Model

- C_a was calculated with modified wire width
- Formula inapplicable for irregular interconnects (non-constant width)




- More practical approximation

$C = A \times C_a + P \times C_p$	<i>units</i>	<i>alternative</i>
$A = \text{Area}$	m^2	μm^2
$C_a = \text{Area capacitance}$	F / m^2	$aF / \mu m^2$
$P = \text{Perimeter}$	m	μm
$C_p = \text{Perimeter capacitance}$	F / m	$aF / \mu m$

 

$$C = \square \times C_a + \square \times C_p$$

Area / Perimeter Capacitance Model

 



$$C = \square \times C_a + \square \times C_p$$

■ **Question:** How to derive C_a, C_p ?

How accurate is this model?

Derivation of C_a, C_p



$C \uparrow$
[aF/ μm]

 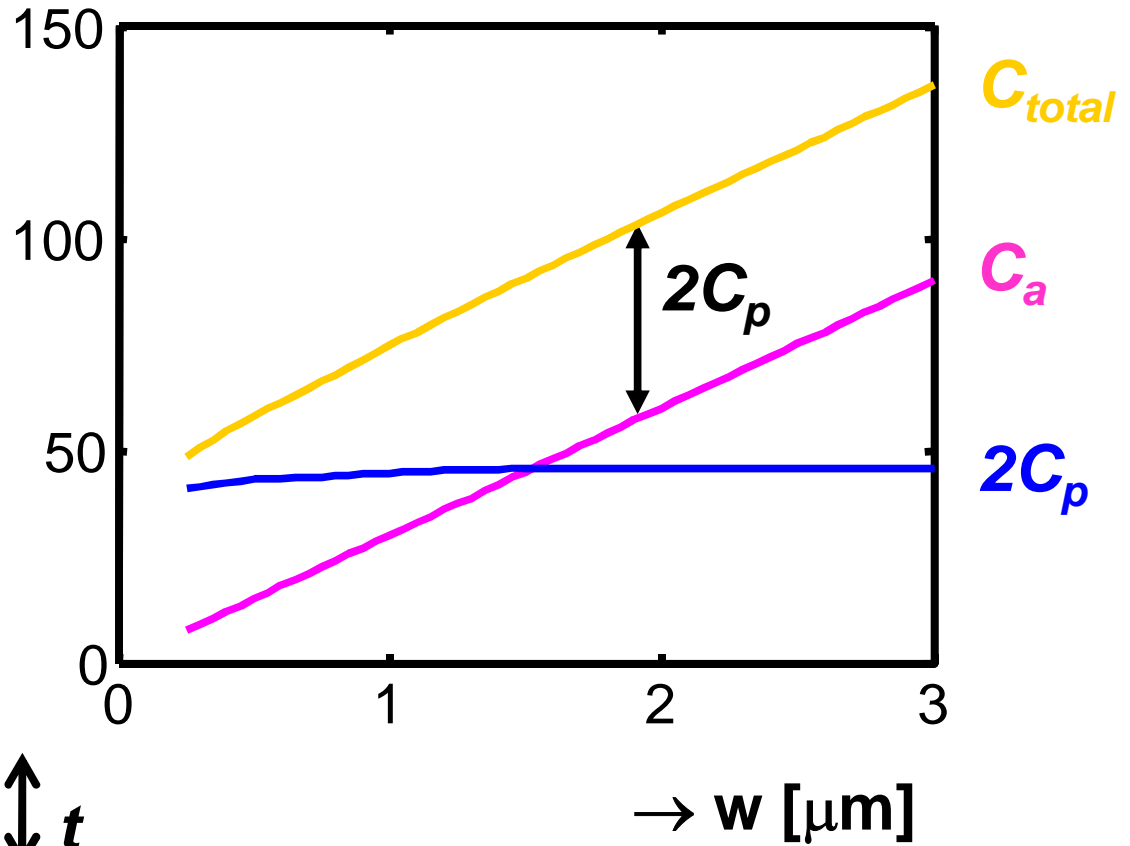

Derivation of C_a, C_p

- **2D (cross-section) numerical computation (or measurement)**
- **C_l : total wire capacitance per unit length**
- **$C_a = \varepsilon_0 \varepsilon_r / h$**
- **$C_p = \frac{1}{2}(C_l - C_a \times w)$**
- **C_p depends on $t, h \rightarrow$ determined by technology, layer**
- **C_p would depend slightly on w (see previous graph), this dependence is often ignored in practice**


Area / Perimeter Capacitance

  

- C_p dominates for many wires
- C_p may not be neglected
- A constant value for C_p is usually a good approximation
- C_p is sometimes called C_f (fringe capacitance)

Interconnect Capacitance Design data

 - See Table 4.2 (or inside backside cover)
- Example: M1 over Field vs. M1 over Active (hypothetical)



M1 over Active	M1 over Field	Unit
$C_a = 41$	$C_a = 30$	$aF/\mu m^2$
$C_p = 47$	$C_p = 40$	$aF/\mu m$

Capacitance Data (Table 4.2)



INTERCONNECT MODELS

Wire area and fringe capacitances (for 0.25 μm CMOS process)


Rows represent the top plate of the capacitor, and columns represent the bottom plate. The area capacitances are expressed in $\text{aF}/\mu\text{m}^2$, while the fringe capacitances (given in the shaded rows) are in $\text{aF}/\mu\text{m}$.

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88	←bottom					
	54	←fringe					
Al1	30	41	57	←bottom			
	40	47	54	←fringe			
Al2	13	15	17	36			
	25	27	29	45			

Coupling Capacitances

  


Coupling Capacitances (2).

 


- $C_T = C_{1g} + C_{12} = C_{2g} + C_{12}$ fairly constant
- Use that as first order model
- Interconnect capacitance design data (e.g. Table 4.3)
- In practice: many pages of very many numbers
- Or: field solvers

Resistance

- Sheet resistance

 

Wire Resistance

 


- Proportional to l
- Inversely proportional to w and t (cross-sectional area)
- Proportional to ρ : specific resistance, material property [Ωm]
- $R = \rho l / wt$
- Aluminum: $\rho = 2.7 \times 10^{-8} \Omega\text{m}$
Copper: $\rho = 1.7 \times 10^{-8} \Omega\text{m}$

Sheet Resistance


- $R = \rho l/wt$
- t, ρ constant for layer, technology
- $R = R_s l/w$
- R_s : sheet resistance [$\Omega/$]
resistance of a square piece of interconnect
other symbol: R_s
- Interconnect resistance design data e.g. Table 4.5 (or inside back-cover)

Interconnect Resistance

 - Assume $R_{\square} = 40 \Omega$
- Estimate the resistance between A and B in the wire below.


 
$$R_{AB} \approx 6 \times 40 = 240 \Omega$$



$$R_{CD} \approx 11 \times 40 = 440 \Omega$$

Engineering is about making controlled approximations to something that is too complicated to compute exactly, while ensuring that the approximate answer still leads to a working (functional, safe, ...) system

Exercise.

An interconnect line is made from a material that has a resistivity of $\rho = 4 \mu\Omega\text{-cm}$. The interconnect is 1200 \AA thick, where 1 Angstrom (\AA) is 10^{-10} m . The line has a width of $0.6 \mu\text{m}$.


- a) Calculate the sheet resistance R_{\square} of the line.
- b) Find the line resistance for a line that is $125 \mu\text{m}$ long.

Interconnect delay

- Delay metrics, rc delay, Elmore delay




Delay

 

- Model driver as linearized Thevenin source V , R_s , assume step input
- Model load as C_L
- Wire is an RC network (two-port)

Wire Capacitance

 


Assume wire behaves purely capacitive

$$(C_w + C_L) \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_s} = 0$$

$$V_{out} = V_{in} - \tau \frac{dV_{out}}{dt} \quad \tau = R_s (C_w + C_L)$$

$$V_{out} = (1 - e^{-t/\tau}) V_{in}$$

Wire Resistance

 


Now, assume wire capacitance *and* resistance

- $\tau = (R_s + R_w)(C_w + C_L)$


- Is this a good model?

- R and C are **distributed** along the wire


Uniform RC Line

 


Symbol

 

[Always] use first order model

 


RC Delay (Uniform RC Line)

 

**Basic π -model
of wire**

Equivalent Time Constant

 


- Multiple time-constants
- Need for one “equivalent” number
- Offered by *Elmore Delay* T_D

$$T_D = R_S C_W / 2 + (R_S + R_W)(C_W / 2 + C_L)$$


- Effective “one number” model for delay

How to
compute
Elmore
Delay?


Equivalent Time Constant

 
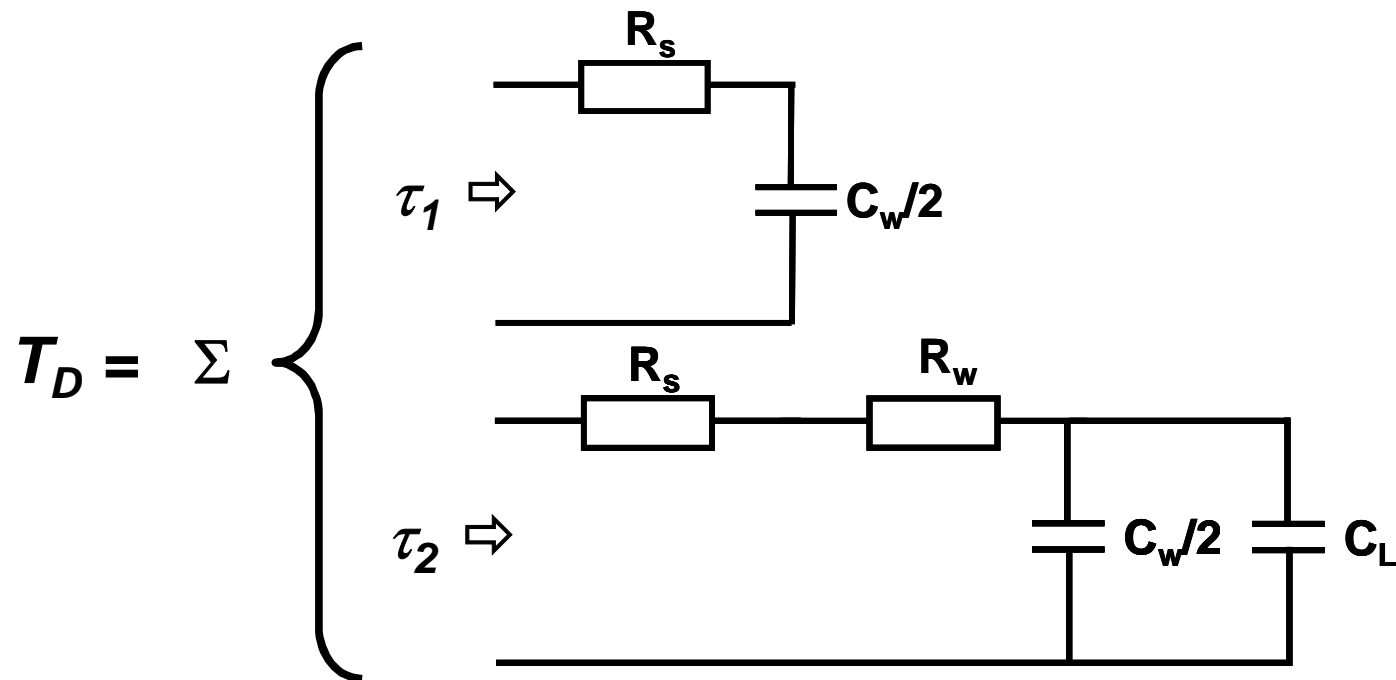
$$T_D = R_S C_W / 2 + (R_S + R_W)(C_W / 2 + C_L)$$



Shared Path Resistance

 


■ Define: R_{ij} = Resistance from node i to input

■ Example: $R_{11} = R_1$ $R_{22} = R_1 + R_2$ $R_{33} = R_1 + R_2 + R_3$

■ Define: R_{ik} = Shared path resistance to input for node i and k

■ $R_{12} = R_1$ $R_{13} = R_1$ $R_{23} =$

Elmore Delay for RC ladders

 

■ Define: $T_{Di} = \sum_{k=1}^N R_{ik} C_k$

Elmore Delay


We will use $0.69 \times T_{di}$ as approximation of wire delay ($t_{50\%}$)

■ $T_{D1} = R_{11}C_1 + R_{12}C_2 + R_{13}C_3 =$
 $= R_1C_1 + R_1C_2 + R_1C_3$


$T_{D3} = R_{31}C_1 + R_{32}C_2 + R_{33}C_3 =$
 $= R_1C_1 + (R_1 + R_2)C_2 + (R_1 + R_2 + R_3)C_3$

■ $T_{D2} =$


Elmore Delay for Distributed RC Lines

 

Symbol

 


Symmetric π -model

 

- **Theorem:** For Elmore Delay calculations, each uniform distributed RC section is equivalent to a symmetric π -model

Canonical Driver-Line-Load

 

$$\begin{aligned} \blacksquare T_{D_1} &= R_s \frac{cl}{2} + (R_s + rl) \left(C_L + \frac{cl}{2} \right) \\ &= R_s (cl + C_L) + rl C_L + \frac{1}{2} rcl^2 \end{aligned}$$


■ Delay quadratic in line length

Shared Path Resistance for Tree Structures

In order to compute Elmore Delay at node 3:

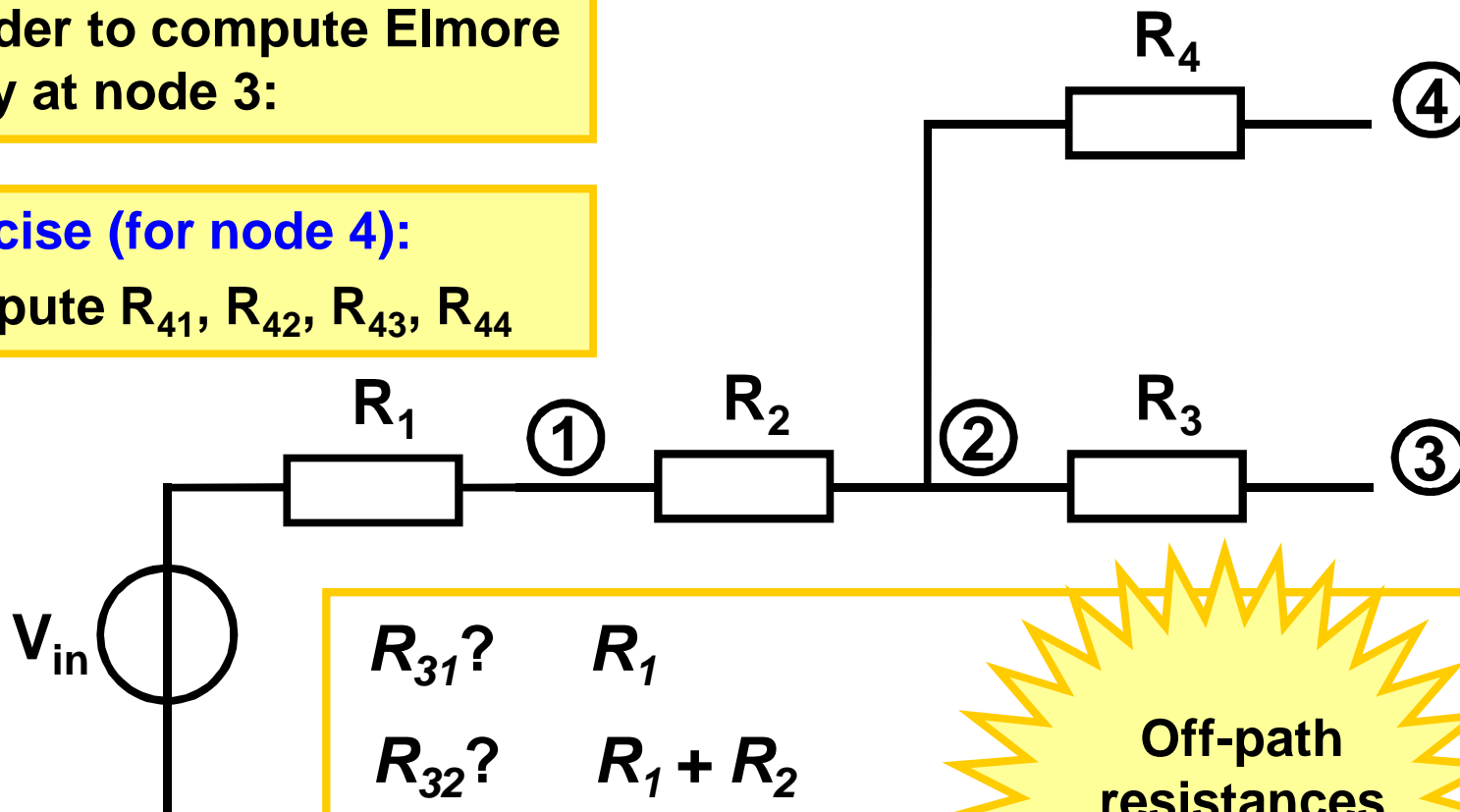Exercise (for node 4):


Compute R_{41} , R_{42} , R_{43} , R_{44}



$R_{31}?$	R_1
$R_{32}?$	$R_1 + R_2$
$R_{33}?$	$R_1 + R_2 + R_3$
$R_{34}?$	$R_1 + R_2$


Off-path resistances don't count

Elmore Delay for Tree Structures.

 

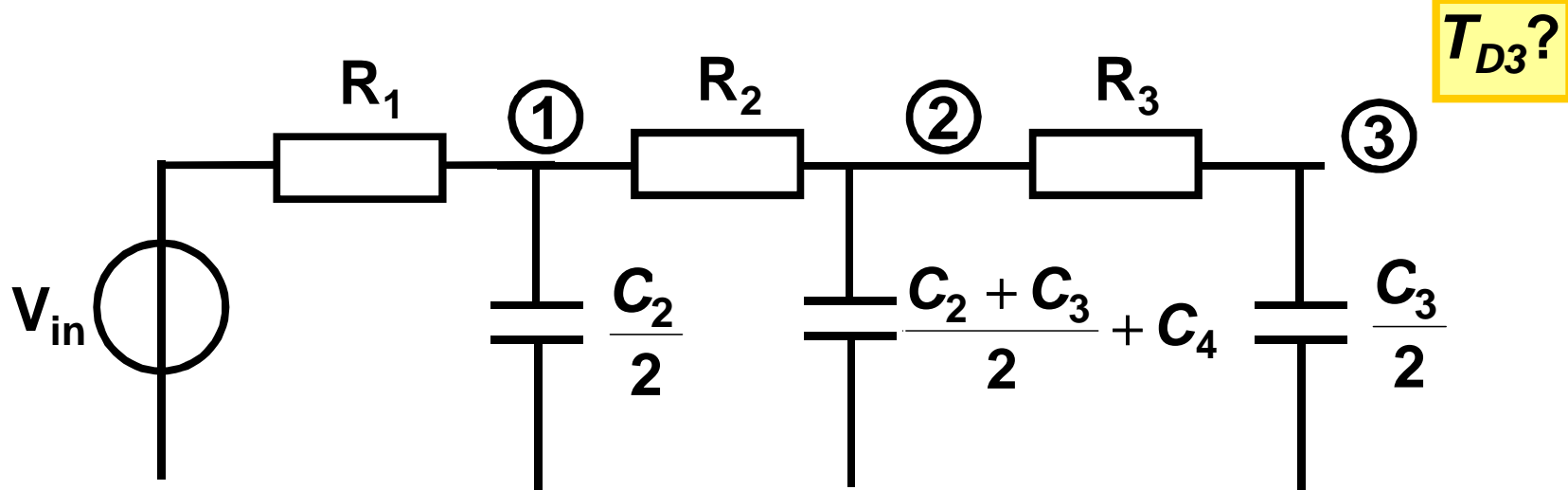Exercise: Compute T_{D1} , T_{D2} , T_{D3} , T_{D4}

- Replace RC lines by π -sections
- Given observation node i , then only resistances along the path from input to node i can possibly count
- Make others zero
- Compute as if RC ladder



Summary

- **Capacitance**
Area/perimeter model, coupling
- **Resistance**
Sheet resistance
- **Interconnect delay**
Delay metrics, rc delay, Elmore delay