

Course Material for Interconnect

Chapter 4, 2nd ed.

P = primair, I = Illustratie, O = overslaan

P	4.1	Introduction	136
P	4.2	A First Glimpse	136 – 138
P	4.3	Interconnect Parameters	138 – e.v.
O		So far we have (onder example 4.2)	147 – 148
O	4.3.3	Inductance	148 – 150
P	4.4	Electrical Wire Models	150 – 156
I	4.4.4	Distributed rc line – <i>hiervoor is vervangende stof</i>	156 – 159 (1)
O	4.4.5	The transmission line	159 – e.v.
O	4.5	Spice wire models	170 – 171
I	4.5.3	Perspective: a look into the future	171 – 174

Replacement voor Distributed RC line: Elmore Delay

TUD/EE ET1205 D2 0910 - © NvdM 3 interconnect 2

Interconnect

- Wires are **not ideal** interconnections
- They may have non-negligible **capacitance, resistance, inductance**
- These are called **wire parasitics**
- Can **dominate** performance of chip
- Must be accounted for during **design**
- Using **approximate models**
- Detailed **post-layout verification** also necessary

§4.2

TUD/EE ET1205 D2 0910 - © NvdM 3 interconnect 3

Wires

← IBM CMOS 7S copper process, 0.16 μm

TUD/EE ET1205 D2 0910 - © NvdM 3 interconnect 4

Interconnect Hierarchy

Cross-section of IBM 0.13 μm process

Example Interconnect Hierarchy for typical 0.25 μm process (Layer Stack)

Global: M6, M5

intermodule: M4, M3

Intercell: M2

Intracell: M1, poly, substrate

TUD/EE ET1205 D2 0910 - © NvdM 3 interconnect 5

45 nm Interconnect Technology

8 interconnect layers in 45 nm technology [Ingerly – iitc – 2008]

TUD/EE ET1205 D2 0910 - © NvdM 3 interconnect 6

Outline

- Capacitance
 - Area/perimeter model, coupling
- Resistance
 - Sheet resistance
- Interconnect delay
 - Delay metrics, rc delay, Elmore delay

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 7

- Capacitance
 - Area/perimeter model, coupling



TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 8

Wake Up! Models ahead!

Annual production for US (48) and FRU with (Market & Sales model)

Observed and Modeled Average Annual Temperature

The observed temperature averages for 1961-1990 are similar to the temperatures simulated by the Canadian and Mexico models for the same time period. There are the two primary models used to develop climate change scenarios for this Assessment.

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 9

Merriam-Webster Online Dictionary

6 entries found for model.
To select an entry, click on it.

model ¹ noun

1 : a thing that serves as a pattern for an artist especially : one who poses for an artist

2 : a person or thing that serves as a pattern for an artist especially : one who poses for an artist

3 : structural design - a house on the model of an old farmhouse

4 : a usually miniature representation of something; also : a pattern of something to be made

5 : an example for imitation or emulation

6 : a person or thing that serves as a pattern for an artist especially : one who poses for an artist

7 : ABBREVIATION

8 : an organism whose appearance mimics another

9 : one who is employed to display clothes or other merchandise in a window

(as an atom) **cannot** be directly observed

12 : a system of postulates, data, and inferences presented as a mathematical description of an entity or state of affairs

13 : version

TUD/EE ET1205 D2 0910 - © NvdM


3interconnect 10

Modeling

- An **abstraction** of (the properties) of something to help **understanding** and **predicting** its behavior
- **Domain Specific**: weather, climate, economy, stock market, ...
- Different models for something to **answer different questions**
- **Black-Box** modeling vs. **Physically Based**

After Einstein:

 
<a model> should be as simple as possible, but not simpler



TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 11

Wire Capacitance - Parallel Plate

 

$$C = \frac{\epsilon_0 \epsilon_r W l}{d}$$

$$\frac{C}{l} = \epsilon_0 \epsilon_r \frac{w}{h}$$

$$\epsilon_0 = 8.85 \text{ pF/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 12

Wire Capacitance - Fringing Fields

$$C_{\text{wire}} = C_{\text{fringe}} + C_{\text{pp}} = \frac{2\pi\epsilon d_i}{\log(t_{\text{di}}/H)} + \frac{w\epsilon d_i}{t_{\text{di}}}$$

- Works reasonably well in practice
- Not directly applicable for interconnects with varying widths

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 13

Wire Capacitance - Area/Perimeter Model

- C_a was calculated with modified wire width
- Formula inapplicable for irregular interconnects (non-constant width)
- More practical approximation

	units	alternative
A = Area	m^2	μm^2
C_a = Area capacitance	F/m^2	$aF/\mu m^2$
P = Perimeter	m	μm
C_p = Perimeter capacitance	F/m	$aF/\mu m$

$$C = \square \times C_a + \square \times C_p$$

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 14

Area / Perimeter Capacitance Model

$C = \square \times C_a + \square \times C_p$

- Question:** How to derive C_a, C_p ?
- How accurate is this model?

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 15

Derivation of C_a, C_p

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 16

Derivation of C_a, C_p

- 2D (cross-section) numerical computation (or measurement)
- C_I : total wire capacitance per unit length
- $C_a = \epsilon_0 \epsilon_r / h$
- $C_p = \frac{1}{2}(C_I - C_a \times w)$
- C_p depends on t, h → determined by technology, layer
- C_p would depend slightly on w (see previous graph), this dependence is often ignored in practice

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 17


Area / Perimeter Capacitance

- C_p dominates for many wires
- C_p may not be neglected
- A constant value for C_p is usually a good approximation
- C_p is sometimes called C_f (fringe capacitance)

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 18

Interconnect Capacitance Design data

 - See Table 4.2 (or inside backside cover)
- Example: M1 over Field vs. M1 over Active (hypothetical)



M1 over Active	M1 over Field	Unit
$C_a = 41$	$C_a = 30$	$aF/\mu m^2$
$C_p = 47$	$C_p = 40$	$aF/\mu m$

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 19

Capacitance Data (Table 4.2)

INTERCONNECT MODELS


Wire area and fringe capacitances (for 0.25 μm CMOS process)
 Rows represent the top plate of the capacitor, and columns represent the bottom plate. The area capacitances are expressed in $aF/\mu m^2$, while the fringe capacitances (given in the shaded rows) are in $aF/\mu m$.

	Field	Active	Poly	A11	A12	A13	A14
Poly	88	\leftarrow bottom \leftarrow fringe					
A11	30	41	57	\leftarrow bottom \leftarrow fringe			
A12	13	15	17	36			
	25	27	29	45			

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 20


Coupling Capacitances

 

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 21

Coupling Capacitances (2).

 

- $C_T = C_{1g} + C_{12} = C_{2g} + C_{12}$ fairly constant
- Use that as first order model
- Interconnect capacitance design data (e.g. Table 4.3)
- In practice: many pages of very many numbers
- Or: field solvers

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 22

Resistance


- Sheet resistance



TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 23

Wire Resistance

 

- Proportional to l
- Inversely proportional to w and t (cross-sectional area)
- Proportional to ρ : specific resistance, material property [Ωm]
- $R = \rho l / wt$
- Aluminum: $\rho = 2.7 \times 10^{-8} \Omega m$
- Copper: $\rho = 1.7 \times 10^{-8} \Omega m$

TUD/EE ET1205 D2 0910 - © NvdM

3interconnect 24

Sheet Resistance


- $R = \rho l / wt$
- t, ρ constant for layer, technology
- $R = R_s l / w$
- R_s : sheet resistance [Ω / \square]
resistance of a square piece of interconnect
other symbol: R_s
- Interconnect resistance design data e.g. Table 4.5 (or inside back-cover)

TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 25

Interconnect Resistance

 - Assume $R_{\square} = 40 \Omega$
- Estimate the resistance between A and B in the wire below.



Engineering is about making controlled approximations to something that is too complicated to compute exactly, while ensuring that the approximate answer still leads to a working (functional, safe, ...) system

TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 26

Exercise.

An interconnect line is made from a material that has a resistivity of $\rho = 4 \mu\Omega\text{-cm}$. The interconnect is 1200 Å thick, where 1 Angstrom (Å) is 10^{-10} m. The line has a width of $0.6 \mu\text{m}$.

- Calculate the sheet resistance R_{\square} of the line.
- Find the line resistance for a line that is $125 \mu\text{m}$ long.

TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 27

Interconnect delay


- Delay metrics, rc delay, Elmore delay



TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 28

Delay

 


- Model driver as linearized Thevenin source V, R_s , assume step input
- Model load as C_L
- Wire is an RC network (two-port)

TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 29

Wire Capacitance

 

Assume wire behaves purely capacitive

$$(C_w + C_L) \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_s} = 0$$

$$V_{out} = V_{in} - \tau \frac{dV_{out}}{dt} \quad \tau = R_s(C_w + C_L)$$

$$V_{out} = (1 - e^{-t/\tau}) V_{in}$$

TUD/EE ET1205 D2 0910 - © NvdM

3 Interconnect 30

Wire Resistance

Now, assume wire capacitance *and* resistance

- $\tau = (R_s + R_w)(C_w + C_L)$
- Is this a good model?
- R and C are **distributed** along the wire

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 31

Uniform RC Line

$\lim N \rightarrow \infty$

Symbol

[Always] use first order model

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 32

RC Delay (Uniform RC Line)

Basic π -model of wire

- $\tau?$

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 33

Equivalent Time Constant

- Multiple time-constants
- Need for one "equivalent" number
- Offered by **Elmore Delay T_D**

$T_D = R_s C_w/2 + (R_s + R_w)(C_w/2 + C_L)$

How to compute Elmore Delay?

- Effective "one number" model for delay

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 34

Equivalent Time Constant

$T_D = \Sigma \left\{ \begin{array}{l} \tau_1 \Rightarrow \\ \tau_2 \Rightarrow \end{array} \right.$

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 35

Shared Path Resistance

- Define: R_{ij} = Resistance from node i to input
- Example: $R_{11} = R_1$ $R_{22} = R_1 + R_2$ $R_{33} = R_1 + R_2 + R_3$
- Define: R_{jk} = Shared path resistance to input for node i and k
- $R_{12} = R_1$ $R_{13} = R_1$ $R_{23} =$

TUD/EE ET1205 D2 0910 - © NvdM 3 Interconnect 36

Elmore Delay for RC ladders

Define: $T_{Di} = \sum_{k=1}^N R_{ik} C_k$

Elmore Delay

We will use $0.69 \times T_{di}$ as approximation of wire delay ($t_{50\%}$)

$T_{D1} = R_{11}C_1 + R_{12}C_2 + R_{13}C_3 = R_1C_1 + R_1C_2 + R_1C_3$

$T_{D3} = R_{31}C_1 + R_{32}C_2 + R_{33}C_3 = R_1C_1 + (R_1 + R_2)C_2 + (R_1 + R_2 + R_3)C_3$

$T_{D2} =$

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 37

Elmore Delay for Distributed RC Lines

Symbol

Symmetric π -model

Theorem: For Elmore Delay calculations, each uniform distributed RC section is equivalent to a symmetric π -model

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 38

Canonical Driver-Line-Load

$T_{D1} = R_s \frac{cl}{2} + (R_s + rl) \left(C_L + \frac{cl}{2} \right)$

$= R_s(cl + C_L) + rlC_L + \frac{1}{2} rcl^2$

Delay quadratic in line length

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 39

Shared Path Resistance for Tree Structures

In order to compute Elmore Delay at node 3:

Exercise (for node 4): Compute $R_{41}, R_{42}, R_{43}, R_{44}$

$R_{31}?$ R_1
 $R_{32}?$ $R_1 + R_2$
 $R_{33}?$ $R_1 + R_2 + R_3$
 $R_{34}?$ $R_1 + R_2$

Off-path resistances don't count

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 40

Elmore Delay for Tree Structures.

Replace RC lines by π -sections

Given observation node i, then only resistances along the path from input to node i can possibly count

Make others zero

Compute as if RC ladder

Exercise: Compute $T_{D1}, T_{D2}, T_{D3}, T_{D4}$

$T_{D3}?$

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 41

Summary

- Capacitance
 - Area/perimeter model, coupling
- Resistance
 - Sheet resistance
- Interconnect delay
 - Delay metrics, rc delay, Elmore delay

TUD/EE ET1205 D2 0910 - © NvdM 3interconnect 42