

Module 4  
CMOS INVERTER

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 1

Course Material for Inverter  
Chapter 5, 2nd ed.  
P = primair, I = Illustratie, O = overslaan

P	5.1	Introduction	180
P	5.2	The Static CMOS inverter - intuitive	181 - 184
P	1.3.2	Functionality and Robustness	18 - 27
P	5.3	Evaluating the Robustness ...	184 - 191
I	5.3.3	Robustness Revisited	191 - 193
P	1.3.3	Performance	27 - 30
I	5.4	Performance of the CMOS inverter	193 - 213
P	1.3.4	Power and Energy Consumption	30 - 31
I	5.5	Power, Energy, and Energy-Delay	213 - 223
O	5.5.2	Static Consumption	223 - 225
O	5.5.3	Putting it All Together	225 - 227
O	5.5.4	Analyzing Power Consumption using SPICE	227 - 229.
O	5.6	Perspective: Technology scaling...	229 - 231
P	5.7	Summary	232 - 233

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 2

The CMOS Inverter - Outline

- First Glance
- Digital Gate Characterization
- Static Behavior (Robustness)
  - VTC
  - Switching Threshold
  - Noise Margins
- Dynamic Behavior (Performance)
  - Capacitances
  - Delay
- Power
  - Dynamic Power, Static Power, Metrics

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 3

The CMOS Inverter: A First Glance

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 4

CMOS Inverters (1)

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 5

CMOS Inverter Operation Principle

$V_{OH} = V_{DD}$   $V_{OL} = 0$

§ 5.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 6

### Digital Gate Fundamental Parameters

- **Functionality**
- **Reliability, Robustness**
- **Area**
- **Performance**
  - Speed (delay)
  - Power Consumption
  - Energy

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 7

### The Ideal Inverter

$R_i = \infty$   
 $R_o = 0$   
 $g = -\infty$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 8

### Static CMOS Properties.

Basic inverter belongs to class of **static circuits**: output always connected to either  $V_{DD}$  or  $V_{SS}$ . **Not ideal but:**

- Rail to rail voltage swing
- Ratio less design
- Low output impedance
- Extremely high input impedance
- No static power dissipation
- Good noise properties/margins

**Exercise:** prioritize the list above

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 9

### Voltage Transfer Characteristic (VTC)

§ 5.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 10

### Load Line (Ckt Theory)

**Exercise:**  
 The blue load line A corresponds to  $R =$    
 The orange load line B corresponds to  $R =$    
 With load line A and  $V_{GS} = 1V$ ,  $V_{out} =$    
 Draw a graph  $V_{out}(V_{in})$  for load line A and B

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 11







### PMOS Load Lines

**Goal:** Combine  $I_{Dn}$  and  $I_{Dp}$  in one graph

**Kirchoff:**  
 $V_{in} = V_{DD} + V_{GSp}$   
 $I_{Dn} = -I_{Dp}$   
 $V_{out} = V_{DD} + V_{DSp}$

  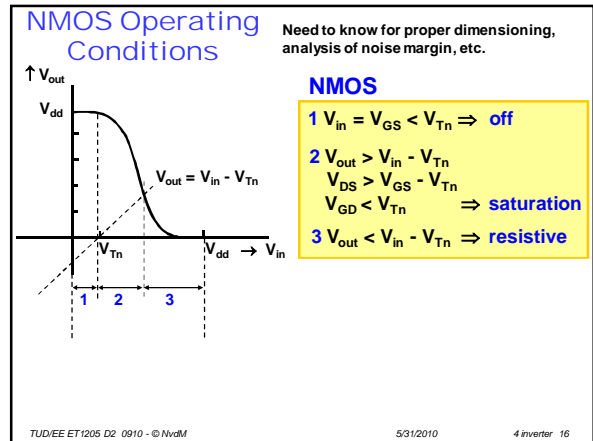   **Example:**  $V_{DD}=5V$   
 $V_{in} = V_{DD} + V_{GSp}$   
 $I_{Dn} = -I_{Dp}$   
 $V_{out} = V_{DD} + V_{DSp}$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 12



### Inverter Static Behavior

- Regeneration
- Noise margins
- Delay metrics

§ 5.3

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 19

### The Realistic Inverter

**Ideal Inverter**

$R_i = \infty$   
 $R_o = 0$   
 $g = -\infty$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 20

### The Regenerative Property

**A chain of inverters**

■ **Regenerative Property:** ability to regenerate (repair) a weak signal in a chain of gates

Ex. 1.4

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 21

### The Regenerative Property (2)

(a) A chain of inverters.

(b) Regenerative gate

(c) Non-regenerative gate

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 22

### The regenerative Property (3)

**Exercise:** what is the output voltage of a chain of 4 inverters with a piece-wise linear VTC passing through (0, 10), (4,8), (6,2) and (10,0) [Volt], as the result of an input voltage of 5.5 [Volt].

**Exercise:** discuss the behavior for an input of 5 [Volt]

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 23


### Exercise Answer


**Ongeveer: 5.5 → 3.5 → 8.5 → 0.75 → 9.75**

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 24
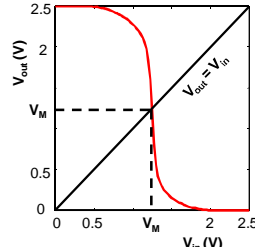
### Inverter Switching Threshold

- Not the device threshold  $V_m = f(R_{onnp}, R_{onp})$
- Point of  $V_{in} = V_{out}$







■ Try to set  $W_n, L_n, W_p, L_p$  so that VTC is symmetric as this will improve noise margins  
optimize NMOS-PMOS ratio

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 25

### Inverter Switching Threshold

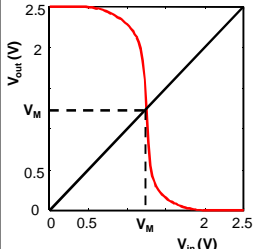

Balanced NMOS and PMOS sizes

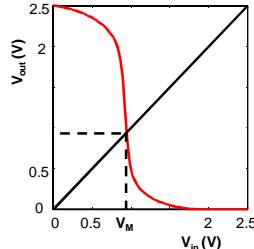


Strong NMOS, Weak PMOS

$V_M = f(W_n/W_p)$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 26
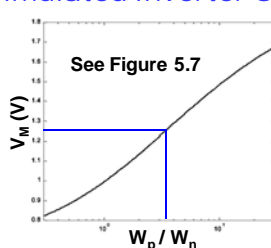
### Simulated Inverter Switching Threshold



See Figure 5.7

**Electrical Design Rule**  
 $W_p \approx 2.5 W_n$


■ Assumes  $L_p = L_n$   
■ Should be applied consistently

- Symmetrical VTC  $\Rightarrow V_m \approx \frac{1}{2} V_{DD} \Rightarrow W_p/W_n \approx \square$
- In practice: choose somewhat smaller value of  $W_p/W_n$
- Why?

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 27
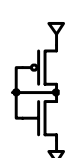
### Inverter Switching Threshold Analytical Derivation

- $V_M$  is  $V_{in}$  such that  $V_{in} = V_{out}$
- $V_{DS} = V_{GS} \Leftrightarrow V_{GD} = 0 \Rightarrow$  saturation
  - Assume  $V_{DSAT} < V_M - V_T$  (velocity saturation)
  - Ignore channel length modulation (for simplicity – is it allowed?)
- $V_M$  follows from
  - $I_{DSATn}(V_M) = -I_{DSATp}(V_M)$
- Q: Given desired value of  $V_M$ , what is the required W/L ratio?



§ 5.3.1

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 28

### Inverter Switching Threshold Analytical Derivation (ctd)

$$I_{DSATn}(V_M) = -I_{DSATp}(V_M) \quad I_D = kV_{DSAT}(V_{GS} - V_T - V_{DSAT}/2)$$

$$\Leftrightarrow k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2) = -k_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)$$

$$\Leftrightarrow \frac{k_p}{k_n} = \frac{-V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \quad k = \frac{W}{L} k'$$


$$\Rightarrow \frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)}$$

■ See Example 5.1:  
■  $(W/L)_p = 3.5 (W/L)_n$  for typical conditions and  $V_M = \frac{1}{2} V_{DD}$   
■ Usually:  $L_n = L_p$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 29
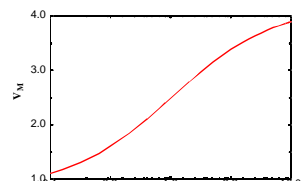
### Inverter Switching Threshold w/o Velocity Saturation.

- Long channel approximation
- Applicable with low  $V_{DD}$



**Exercise (Problem 5.1):**  
derive  $V_M$  for long-channel approximation as shown below

$$V_M = \frac{r(V_{DD} - V_{Tp} + V_{Tn})}{1+r} \quad \text{with} \quad r = \sqrt{\frac{-k_p}{k_n}}$$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 30

### Noise in Digital Integrated Circuits

(a) Inductive coupling (b) Capacitive coupling (c) Power and ground noise

■ Study behavior of static CMOS Gates with noisy signals

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 31

### Noise Margins

“1”  $V_{OH}$   
 $V_{IH}$   
 Undefined Region  
 $V_{IL}$   
 “0”  $V_{OL}$

■  $V_{OL}$  = Output Low Voltage  
 ■  $V_{IL}$  = Input Low Voltage  
 ■  $V_{OH}, V_{IH} = \dots$

§ 1.3.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 32

### Noise Margins

■  $NM_H = V_{OH} - V_{IH}$  = High Noise Margin  
 ■  $NM_L = V_{IL} - V_{OL}$  = Low Noise Margin

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 33

### Noise Margin for Realistic Gates

Slope = -1  
 Slope = -1

Exercise: explain significance of slope = -1 for noise margin

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 34

### Noise Margin Calculation

Piece-wise linear approximation of VTC

$g = \text{gain factor (slope of VTC)}$

We know how to compute  $V_M$   
 Next: how to compute  $g$

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = -\frac{V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$

§ 5.3.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 35


### Different Gain

Steep slope, high gain  
 Less steep slope, lower gain

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 36

### Noise Margin Calculation (2)

- Approximate  $g$  as the slope in  $V_{out}$  vs.  $V_{in}$  at  $V_{in} = V_M$
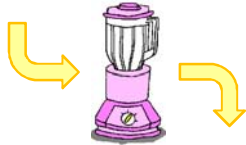
$$k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn} / 2)(1 + \lambda_n V_{out}) + k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp} / 2)(1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$


$$g = \frac{dV_{out}}{dV_{in}} \Big|_{V_{in}=V_M} \approx \frac{1+r}{(V_M - V_T - V_{DSATp} / 2)(\lambda_n - \lambda_p)} \quad r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 37

### Noise Margin Calculation (3)

$$g = \frac{dV_{out}}{dV_{in}} \Big|_{V_{in}=V_M} \approx \frac{1+r}{(V_M - V_T - V_{DSATp} / 2)(\lambda_n - \lambda_p)} \quad r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

- Mostly determined by technology
- See example 5.2


- Exercise:** verify calculation
- Exercise:** explain why we add channel length modulation to the  $I_D$  expressions (we did not do this to determine  $V_M$ )

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 38

### Dynamic Behavior (Performance)


- Capacitances
- Delay

- But: we take much simpler model for capacitances compared to book.
- See the syllabus.
- § 5.4.1 of book is only illustration.



TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 39


### CMOS Inverters

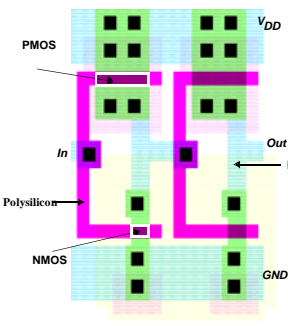

- What causes the delay?
- What is  $R_{on}$ ?
- Where are the capacitances?
- Which capacitances determine  $T_p$ ?


TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 40

### Delay Definitions

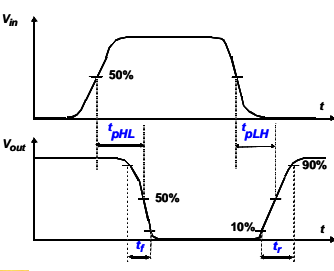


$$t_p = \frac{1}{2}(t_{pHL} + t_{pLH})$$

$t_p$ : property of gate  
 $t_r, t_f$ : property of signal



TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 41

### CMOS Inverter Rise/Fall Delay

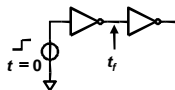

- Goal: determine  $t_f, t_r$  and  $t_p$
- First: compute relevant capacitances
- Second: determine equivalent  $R_{on}$
- Third: compute RC delay ( $\tau$ ) and scale result
- Assume: ideal source, step input

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 42

### Modeling

From module 1- devices

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 43

### Modeling (2)

$R = R_{on1}$   
 $C = C_{D1} + C_{D2} + C_{G3} + C_{G4}$   
 $V_s = 0$   
 Frequently, we only include  $C_{Gi}$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 44

### Modeling (3)

- Delay can be modeled using RC circuit
  - First order simplified model
- R is (linearized) on-resistance of active transistor
- C is sum of (linearized) C's that are switched
  - Typically,  $C_G$  of driven gate,  $C_D$  of driving gate
  - Plus relevant interconnect C
  - Might need to include interconnect R in model
- $V_s$  is final voltage of delay node (initial voltage determined by previous state)

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 45

### RC Delay Review (1)

$$v_C(t) = v_C(\infty) + (v_C(t_0) - v_C(\infty))e^{-(t-t_0)/\tau}$$

$$RC \frac{dv_C}{dt} = V_s - v_C$$

$$v_C = V_s(1 - e^{-\frac{t}{RC}})$$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 46

### RC Delay Review (2)

- Response can be normalized with respect to  $\tau=RC$  and  $V_s = v_C(t = \infty)$

$v_C = V_s(1 - e^{-\frac{t}{RC}})$   
 $\frac{v_C}{V_s} = (1 - e^{-t/\tau})$

Example:  $(1 - e^{-2}) = 0.86$

Each  $\tau$ -step gives 63% of remaining swing

swing	time
0-50%	$0.69 \tau$
0-63%	$1.0 \tau$
10%-90%	$2.2 \tau$
0-90%	$2.3 \tau$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 47

$$\frac{v_C}{V_s} = (1 - e^{-t/\tau})$$

$$\Downarrow$$

$$0.5 = (1 - e^{-t_{50\%}/\tau})$$

$$\Downarrow$$

$$0.5 = e^{-t_{50\%}/\tau}$$

$$\Downarrow$$

$$2 = e^{t_{50\%}/\tau}$$

$$\Downarrow$$

$$\ln(2) = 0.69 = t_{50\%}/\tau$$


$$\Downarrow$$

$$t_{50\%} = 0.69 \tau$$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 48



Inverter Propagation Delay Summary.

 


$$t_{pHL} = 0.69 R_{eq} C_L$$

$$t_{pLH} = 0.69 R_{eq} C_L$$

$$t_p = \frac{1}{2} (t_{pHL} + t_{pLH}) \quad \text{Propagation time}$$


Propagation Delay w. Wire Resistance

 


$$t_{pHL} = 0.69 R_{eq} (C_{out} + 0.5 C_W) + 0.69 (R_{eq} + R_W) (0.5 C_W + C_{in})$$

■ See module 3, interconnect

Equivalent Ron (Req)

 

(a) Schematic

 


(b) trajectory traversed on ID-VDS curve.

$$R_{eq} = \frac{1}{2} \left[ \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right]$$

$$\approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$

See 3-devices, example 3.8

Impact of Rise Time on Delay

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

Empirical from the first edition of book

Delay as a function of VDD


 


Fig.5.17

CMOS Inverter Propagation Delay

 

Alternative current-based estimate for  $T_p$  assuming velocity saturation

$$T_{pHL} = \frac{C_L V_{swing}}{I_{av}} \approx \frac{C_L V_{DD}}{2 I_{DSAT} (1 + \frac{3}{4} \lambda V_{DD})}$$

Pr. 5.4

Exercise (Problem 5.4): Derive the expression above

### Ring Oscillator

Frequently used to obtain  $T_p$  by measurement (or simulation)

$N$ : number of inverters

$T_p$ : propagation delay

$T$ : period of oscillation

§ 1.3.3

$$T = 2 \times T_p \times N \Leftrightarrow T_p = T/2N$$

Exercise: explain the factor 2 in the expression above

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 55

### Fan-in and Fan-out.

§ 1.3.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 56

### Power

- Dynamic Power
- Static Power
- Metrics

www.quitpc.com

24 hours audio playback time

§ 5.5

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 57

### CMOS Power Dissipation

- Power dissipation is a **very important** circuit characteristic
- CMOS has relatively low static dissipation
- Power dissipation was the reason that CMOS technology won over bipolar and NMOS technology for digital IC's
- (Extremely) high clock frequencies increase dynamic dissipation
- Low  $V_T$  increase leakage
- Advanced IC design is a continuous struggle to contain the power requirements!

§ 1.3.4

§ 5.5

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 58

### Power Density

**Estimate**

- Furnace: 2000 Watt,  $r=10\text{cm}$   $\rightarrow P \approx 6\text{Watt/cm}^2$
- Processor chip: 100 Watt,  $3\text{cm}^2$   $\rightarrow P \approx 33\text{Watt/cm}^2$

Power-aware design, design for low power, is blossoming subfield of VLSI Design

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 59

### Where Does Power Go in CMOS

- **Dynamic Power Consumption**  
Charging and discharging capacitors
- **Short Circuit Currents**  
Short circuit path between supply rails during switching
- **Leakage**  
Leaking diodes and transistors  
May be important for battery-operated equipment

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 4 inverter 60

### Dynamic Power

#### Dynamic Power


- $E_i$  = energy of switching event  $i$ 
  - (to first order) independent of switching speed
  - depends on process, layout
- Power = Energy/Time  
average power:  $P_{avg} = \frac{1}{T} \sum_i E_i$
- $E_i$  = Power-Delay-Product P-D
  - important quality measure
- Energy-Delay-Product E-D
  - combines power\*speed performance

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 61

### Transition Energy

 

- Assume 1→0→1 transition at input
- Load cap must be charged and discharged again
- How much energy is delivered by power supply?

- Energy is power x time
- Assume timing of input signal such that output swing is complete
- Power supply only delivers energy for charging the capacitor
- Energy on capacitor is dissipated upon discharging


$$E_{delivered} = \int_0^{\infty} P(t) dt$$

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 62

### Low-to-High Transition Energy

 

$E_{VDD}$ : Energy delivered by supply

$$\begin{aligned} E_{VDD} &= \int_0^{\infty} i(t) V_{DD} dt \\ &= \int_0^{\infty} C \frac{dv_0}{dt} V_{DD} dt \\ &= \int_0^{V_{DD}} C V_{DD} dv_0 = [C V_{DD} v_0]_0^{V_{DD}} \\ &= C V_{DD}^2 \end{aligned}$$


- Transition energy does not depend on switching speed
- Only on load capacitance and (square of) supply voltage

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 63

### Low-to-High Transition Energy

 

$E_{diss}$ : Energy dissipated in transistor


$$\begin{aligned} E_{diss} &= \int_0^{\infty} i(V_{DD} - v_0) dt \\ &= \int_0^{\infty} i V_{DD} dt - \int_0^{\infty} i v_0 dt \\ &= E_{VDD} - E_C = \frac{1}{2} C V_{DD}^2 \end{aligned}$$

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 64

### High-to-Low Transition Energy

 

Equivalent circuit


- On high-to-low transition, supply does not deliver energy
- Any energy that is on capacitor after charging, is destroyed (converted into heat, dissipated) upon discharging
- Show that this is all the energy on C:  $\frac{1}{2} C V_{DD}^2$

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 65

### Dissipation Cycle

 

In one cycle:

- Source delivers  $C V_{DD}^2$  upon charging C
- Half of that is dissipated in pull-up transistor
- Rest is stored on capacitor
- And is completely destroyed upon discharging C
- So,  $C V_{DD}^2$  is energy expended per cycle

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 66

## CMOS Dynamic Power Dissipation.

$$\text{Energy} = E_{\text{charge}} + E_{\text{discharge}}$$

$$\text{Power} = \frac{\text{Energy}}{\text{Time}} = \frac{\text{Energy}}{\text{transition}} \times \frac{\#\text{transitions}}{\text{time}}$$

$$= CV_{DD}^2 \times f$$

- Independent of transistor on-resistances
- Can only reduce  $C$ ,  $V_{DD}$  or  $f$  to reduce power
- In this formula,  $f$  accounts for switching activity (not necessarily a simple regular waveform)
- Can also include probability of switching explicitly, take  $\alpha$  as switching factor

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 67

## Summary

- First Glance
- Digital Gate Characterization (§ 1.3)
- Static Behavior (Robustness) (§ 5.3)
  - VTC
  - Switching Threshold
  - Noise Margins
- Dynamic Behavior (Performance) (§ 5.4)
  - Capacitances
  - Delay
- Power (§ 5.5)
  - Dynamic Power, Static Power, Metrics

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

4 inverter 68