

**MODULE 5**

**COMBINATIONAL LOGIC**

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 1

**Course Material for Combinational**

Extra: Slides about how to implement a static combinational gate with NMOS/PMOS transistors, given the Boolean function

P	6.1	Introduction	236
P	6.2	Static CMOS Design	236 – 237
P	6.2.1	Complementary CMOS	237 – 242
I		Propagation Delay of Complementary CMOS gates	242 – 249
I		Design Techniques for large fan-in	249 – 251
O		Optimizing performance in combinational networks	251 – 257
O		Power consumption in CMOS logic gates	257 – 263
P	6.2.2	Ratioed Logic	263 – 267
I		How to build even better loads	267 – 268
P	6.2.3	Pass-transistor basics	269 – 270
I		Example 6.10	271 – 272
O		Diversen	272 – 277
P		Solution 3: Transmission gate logic	277 – 280
I		Rest of § 6.2.3	280 – 284
I	6.3	Dynamic CMOS Design	
I	6.3.1	Dynamic Logic: Basic Principles	284 – 286
I	6.3.2	Speed and Power Dissipation of Dynamic Logic	287 – 290
I	6.3.3	Signal Integrity Issues in Dynamic Design	290 – 295
O	6.3.4	Cascading Dynamic Gates	295 – 303
P	6.4	Perspectives	303 – 306
P	6.5	Summary	306 – 307

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 2

**Combinational Logic - Outline**

- Conventional Static CMOS basic principles
- Complementary static CMOS
  - Complex Logic Gates
  - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic
- Dynamic CMOS gates → only illustration

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 3


**Complementary Static CMOS Basic Principles**

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 4

**Combinational vs. Sequential Logic**

 

(a) Combinational

(b) Sequential



Output = f(In)

Output = f(In, History)

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 5

**Reminder**

**DeMorgan Transformations**

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5combinational 6

### NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a **switch** controlled by its gate signal

**NMOS** switch **closes** when switch control input is **high**

$Y = X$  if **A and B**

$Y = X$  if **A or B**

§ 6.2.1

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 7

### PMOS Transistors in Series/Parallel Connection

**PMOS** switch closes when switch control input is **low**

$Y = X$  if ...

$Y = X$  if  **$\bar{A}$  and  $\bar{B}$**

$Y = X$  if  **$\bar{A}$  or  $\bar{B}$**

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 8

### 2-Input Nand

$Y = 1$  if  **$\bar{A}$  OR  $\bar{B}$**

$Y = 1$  if **A AND B**

$Y = 0$  if **A AND B**

DeMorgan

B	A	Y
0	0	1
0	1	1
1	0	1
1	1	0

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 9

### 2-Input Nand

$Y = \bar{A} \text{ AND } \bar{B}$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 10

### 2-input Nand/Nor

$Y = \overline{A \text{ AND } B}$

$Y = \overline{A \text{ OR } B}$


TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 11

### NMOS vs. PMOS, pull-down vs. pull-up

- PMOS is better pull-up
- NMOS is better pull-down

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 12

### Bad Idea

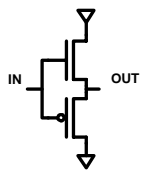

**Exercise:** Determine logic function  
 Determine  $V_{out}$   
 for  $V_{in} = V_{DD}$  and  $V_{in} = V_{SS}$   
 Why is this a bad circuit?

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 13

### CMOS Gate is Inverting.

Assume full-swing inputs (high =  $V_{DD}$ , low =  $V_{SS}$ )

- Highest output voltage of NMOS is  
 $V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$
- An 1 on NMOS gate can produce a **strong 0** at the drain, but not a strong 1
- Lowest output voltage of PMOS is  
 $V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$   
 (with  $V_{GS}, V_{Tp} < 0$  for PMOS)
- An 0 on PMOS gate can produce a **strong 1** at the drain, but not a strong 0
- Need NMOS for pull-down, PMOS for pull-up  
 A 1 at input can pull-down, 0 at input can pull-up  
 A 1 can produce a 0, a 0 can produce a 1

**Inverting behavior** For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates


TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 14

### Complementary static CMOS

- Complex Logic Gates
- VTC, Delay and Sizing

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 15

### Complementary Static CMOS

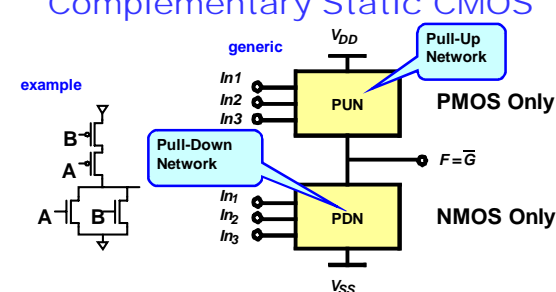


**§ 6.2.1**

- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 16

### Mutual Exclusive PDN and PUN

Out =  $(AB + C)'$

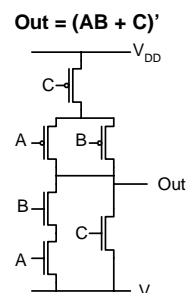

C	B	A	P D N	P U N	Out
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

} PDN Off, PUN On  
 } PUN Off, PDN On

**For all Complementary Static CMOS Gates, either the PUN or the PDN is conducting, but never both.**

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 17

### Complementary Static CMOS (2)

- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN  
 series  $\leftrightarrow$  parallel  
 nmos  $\leftrightarrow$  pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need 2N transistors for N-input gate

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 18

### Implementation of Combinational Logic

How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?

- Example:  $Y = \overline{(A + BC)}D$
- Remember: only inverting gates available



Ex. 6.2


TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 19

### Implementation of Combinational Logic

 - Example:  $Y = \overline{(A + BC)}D$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path  $\Rightarrow$  DELAY



# transistors       logic depth

Q: Can this be improved?


TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 20
 
### Improved Gate Level Implementation

- Using DeMorgan  $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



# transistors

Logic depth

- Q: Can this be further improved?


TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 21
 
### Complex CMOS Logic Gates

- Restriction to basic NAND, NOR etc. **not necessary**
- Easy to synthesize **complex gates**



# transistors: 8  
Logic depth: 1

TUD/EE ET1205 D2 0910 - © NvdM


5/31/2010

5 combinational 22
 
### How to Synthesize Complex Gates

$Y = \overline{(A + BC)}D$

- Using tree representation of Boolean function
- Operator with branches for operands
- As a series-parallel network



	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series


TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 23

### Complex Gate Synthesis Example

$\overline{Y} = (A + (BC))D$

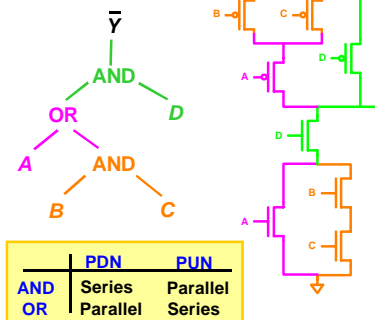

- Recipe
- Write  $Y = f(\text{inputs})$
  - Decompose  $f$  in tree form
  - Realize tree branches according to table at bottom-left
  - Use inverted inputs if necessary

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 24

### And-Or-Invert Gate

Dual PMOS pull-up network

$V_{DD}$   
 $V_{out}$

A<sub>1</sub> B<sub>1</sub> C<sub>1</sub>  
A<sub>2</sub> B<sub>2</sub> C<sub>2</sub>  
A<sub>3</sub> B<sub>3</sub> C<sub>3</sub>

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 25

### And-Or-Invert Example

■ From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$   
 $\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

$\bar{A}, \bar{B}$  to be created with extra inverters (or by restructuring previous circuits)

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 26

### And-Or-Invert Improvement

$Y = \bar{A}BC + A\bar{B}C$   
12 transistors

$Y = (\bar{A}B + A\bar{B})C$   
10 transistors

2-level logic minimization: see Brown (CS1), Ch. 4

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 27

### CMOS Complex Gate Sizing

$Y = (A + BC)D$

- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

2 trans. in series  
3 trans. in series

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 28

### CMOS Complex Gate Sizing

1. For all possible single pull-down paths:
  - a. Let  $L_{sum}$  be the sum of lengths of all transistors in path,
  - b. Compute  $W$  to give the desired drive strength to a transistor of this length  $L_{sum}$
2. For all transistors:
  - a. Set  $W$  to be the maximum found among all the paths of which the transistor is part
3. Repeat this procedure for PUN, using  $W_p$  for PUN transistor of inverter.

Assume all transistor lengths are equal  
Find  $(W/L)$ , such that PDN has strength of  $W/L=2$

$(W/L)_B = (W/L)_C = (W/L)_D = 6$   
 $(W/L)_A = 4$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 29

### Gate Sizing

- W/L ratios
- what are the W/L of 2-input NAND for same drive strength?

0-th order calculation

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 30

### Exercise

(a)

(b)

**Exercise:**

- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, **assume PU/PD = 3**
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same PU/PD)
- Compare sum of gate areas in (a) and (b). Note: area ~ width

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 31

### Avoid Large Fan-In

**C** of PUN **linear** in N  
**R** of PDN **linear** in N  
**Delay** ∝ RC **quadratic** in N

**Empirical**  
**Delay** =  $a_1FI + a_2FI^2 + a_3FO$

- Sizing can make R independent of N, at the (huge) cost of size
- Consider case of NOR your self

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 32

### Data-Dependent Timing

$t_{PHL} = 0.69R_N C_L$   
 $t_{PLH} = 0.69R_P C_L$

$t_{PHL} = 0.69(R_N \times 2)C_L$  **Series connection**  
 $t_{PLH} = 0.69R_P C_L$  **One input goes low**  
 $t_{PLH} = 0.69(R_P/2)C_L$  **Two inputs go low, parallel connection**

**You should be able to identify the transistor paths that charge or discharge  $C_L$ , and calculate resulting RC delay model, including effects of wires and fan-out**

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 33

### Data-dependent VTC: 2nd order effects

- Charge at 'int'
- Body effect in  $M_2$
- Short-circuit currents

- Don't need to be able to work with these effects
- But remember: there is more going on than shown by our simple, 1<sup>st</sup> order model

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 34

### Data-dependent Timing (2).

Input Data Pattern	Delay (pS)
A = B = 0 → 1	69
A = 1, B = 0 → 1	62
A = 0 → 1, B = 1	50
A = B = 1 → 0	35
A = 1, B = 1 → 0	76
A = 1 → 0, B = 1	57

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 35

### Ratioed logic

#### Pass transistor logic

TUD/EE ET1205 D2 0910 - © NvdM
5/31/2010
5 combinational 36

### Pseudo NMOS Ratioed Logic

- ☺ Reduced area
- ☺ Reduced capacitances
- ☹ Increased  $V_{OL}$
- ☹ Reduced noise margins
- ☹ Static dissipation

§ 6.2.2

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 37

### Ratioed Logic $V_{OL}$ Computation.

**Exercise: verify these assumptions/steps**

$I_{Dn} \text{ (linear)} = I_{Dp} \text{ (saturation)}$

$$k_n \left( (V_{DD} - V_{Tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left( (-V_{DD} - V_{Tp})V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn})V_{OL} \approx k_p (-V_{DD} - V_{Tp})V_{DSAT}$$

Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} |V_{DSAT}| \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSAT}|$$

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 38

### Pass-transistor and Pass-gate circuits

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 39

### Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (extra inverters)

**But remember:**

- PMOS is better pull-up
- NMOS is better pull-down

§ 6.2.3

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 40

### Pass Transistor Logic

- Save area, capacitances
- Need complementary inputs (might mean extra inverters)
- Reduced  $V_{OH}$ , noise margins
- $V_{OH} = V_{DD} - (V_{Tno} + \gamma(\sqrt{2\phi_f} + V_{OH}) - \sqrt{2\phi_f})$
- Static dissipation in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by complementary pass gates (NMOS + PMOS parallel)

**Exercise:** Why is there static dissipation in next conventional gate?

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 41

### Pass Gates

- Remedy: use an N-MOS and a P-MOS in parallel


- Pass gates eliminate some of the disadvantages of simple pass-transistors
- But also some of the advantages
- Design remains a trade-off!

**Pass-gate a.k.a. Transmission-gate**

TUD/EE ET1205 D2 0910 - © NvdM 5/31/2010 5 combinational 42
 
### Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?





TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 43
  
### Pass Transistor Logic.

- Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$  ('S' is easier notation for S-bar = S-inverse =  $\overline{S}$ )
- $Y = ((AS)' (BS)')'$  allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8, when including restoring inverter at output) transistors



TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 44

### Summary

- Conventional Static CMOS basic principles
- Complementary static CMOS
  - Complex Logic Gates
  - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic

TUD/EE ET1205 D2 0910 - © NvdM

5/31/2010

5 combinational 45