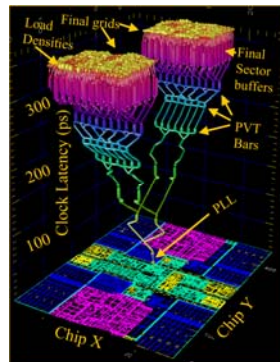


MODULE 7

TIMING DESIGN



TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 1

Course Material for Timing Design

| | | | |
|---|-----------------|---|-----------|
| P | 10.1 | Introduction | 492 |
| I | 10.2 | Timing Classification | 492 – 495 |
| P | 10.3.1 | Synchronous Timing Basics | 495 – 500 |
| I | | Clock Jitter | 500 |
| I | | The combined impact of Skew and Jitter | 501 – 502 |
| I | 10.3.2 | Sources of Skew and Jitter | |
| I | 10.3.3 | Clock Distribution Techniques | |
| O | 10.3.4 | Latch-Based Clocking | 516 – 518 |
| O | 10.4-10.7 | Self-Timed Circuit Design – Future Directions | 519 – 551 |
| P | 7.5 – 7.5.1 (!) | Pipelining | 358-361 |

Material from Chapter 10, one section from Chapter 7

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 2

Outline

- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
- The Clock Skew Problem
 - Controlling Clock Skew
- Case Study

Get basic appreciation of some system level design issues

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 3

Design of LARGE Integrated Circuits


- Correct signal
 - Logic value
 - Right level (restoring logic, ...)
- At right place
 - Interconnect (R, C, L)
 - Busses
 - Off-chip drivers, and receivers
- At right time
 - How to cope with (uncertain) delay

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 4

Case Study: IBM Power6 CPU

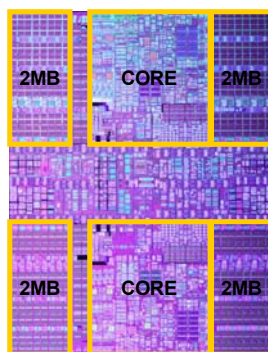

- introduced 21 may 2007
- 64 bit, dual core
- 790 million transistors
- 4.7 (5⁺) GHz
- 65nm SOI, 10 Cu levels interconnect
- 2 Cores
- 8 MB on-chip level2 cache
- processor bandwidth: 300GB/sec
- 1953 signal I/O, 5449 power I/O

<http://en.wikipedia.org/wiki/POWER6>


<http://www-03.ibm.com/press/us/en/pressrelease/21580.wss>

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 5

IBM 65nm SOI Technology

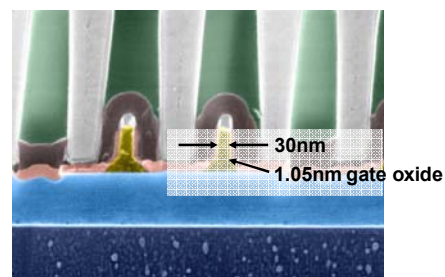

Gate oxide: 1.05 nm ~ 5 atom layers in Si (!!)

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 6

Uncertain Delay


- Data-dependent Delay
- Short and long combinational paths
- Device parameters variations (§3.4)
 - Batch to batch V_t threshold voltage
 - Wafer to wafer k' transconductance
 - Die to die W, L dimensions
- Supply Variations
 - IR drop, dI/dt drop, ringing,
- Interconnect Delay
 - Don't know length of line during logic design
 - Delay at begin of line smaller than at end
 - Interconnect parameter variability

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 7

Delay Along a Wire (Module 3)

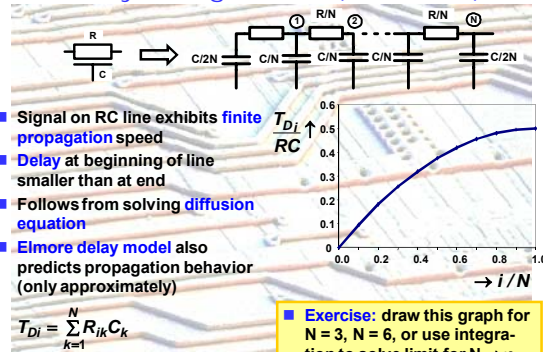


TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 8

Delay of Clock Wire

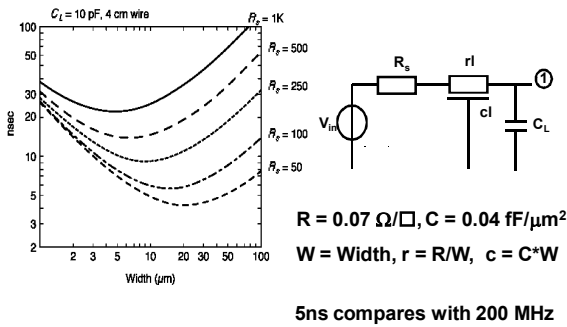


TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 9

Canonical Clock Tree Network

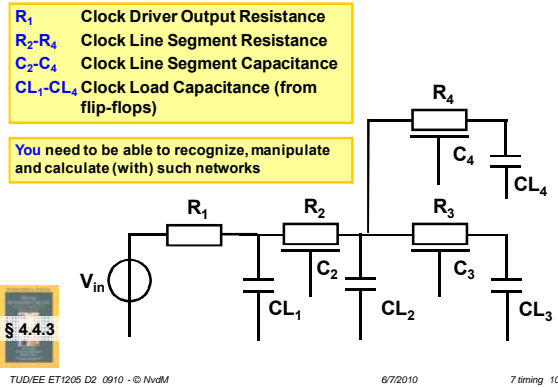

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 10

Impact of Uncertain Delay.

- Combinational circuits will eventually settle at correct output values when inputs are stable
- Sequential circuits
 - Have state
 - Must guarantee storing of correct signals at correct time
 - Require ordered computations

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 11

Sequential Circuits

- Sequential circuits require ordered computation
- Several ways for imposing ordering
 - ✓ Synchronous (clock)
 - ✗ Asynchronous (unstructured)
 - ✗ Self-timed (negotiation)

■ Clock works like an orchestra conductor



TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 12

Synchronous Design


- Global Clock Signal
- Synchronicity may be **defeated** by
 - Delay uncertainty in clock signal
 - Relative timing errors: **clock skew**
 - Slow logic paths
 - Fast logic paths

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 13

Timing Metrics Reminder

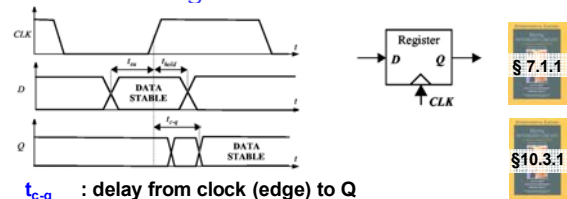

- t_{c-q} : delay from clock (edge) to Q
- t_{su} : setup time
- t_{hold} : hold time
- t_{plogic} : worst case propagation delay of logic
- t_{cd} : best case propagation delay (contamination delay)
- T : clock period

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 14

Sequential Circuit Timing.

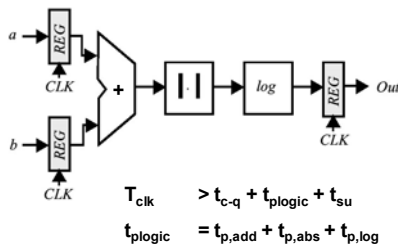


How to reduce T_{clk} ?

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 15

Pipelined Laundry System

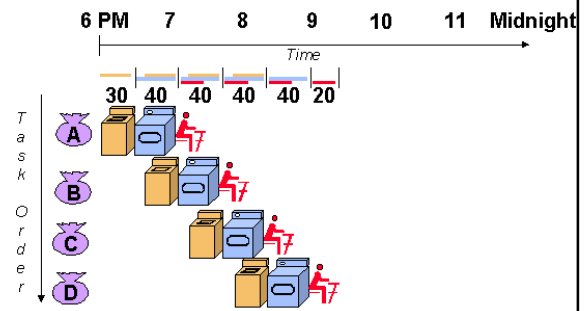

Also: <http://en.wikipedia.org/wiki/Pipelining>


From <http://cse.stanford.edu/class/sophomore-college/projects-00/risc/pipelining/index.html> which credited <http://www.ece.arizona.edu/~ece462/Lec03/pipe/>

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 16

Pipelining

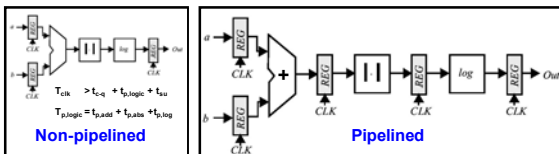

| Clock Period | Adder | Absolute Value | Logarithm |
|--------------|-------------|----------------|---------------------|
| 1 | $a_1 + b_1$ | $ a_1 + b_1 $ | |
| 2 | $a_2 + b_2$ | $ a_2 + b_2 $ | |
| 3 | $a_3 + b_3$ | $ a_3 + b_3 $ | $\log(a_3 + b_3)$ |
| 4 | $a_4 + b_4$ | $ a_4 + b_4 $ | $\log(a_4 + b_4)$ |
| 5 | $a_5 + b_5$ | $ a_5 + b_5 $ | $\log(a_5 + b_5)$ |

$$T_{clk} > t_{c-q} + \max(t_{p,add}, t_{p,abs}, t_{p,log}) + t_{su}$$

- Improve resource utilization
- Increase functional throughput

§ 7.5

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 17

Pipelining Observations.

- Very popular/effective measure to increase functional **throughput and resource utilization**
- At the cost of increased **latency**
- All high performance microprocessors excessively use pipelining in **instruction fetch-decode-execute sequence**
- Pipelining efficiency may fall dramatically because of **branches** in program flow
 - Requires emptying of pipeline and **restarting**
 - Partially remedied by **advanced branch prediction techniques**
- But all is dictated by **GHz marketing drive**
 - All a customer asks is: "How many GHz?"
 - Or says: "Mine is ... GHz!"

Bottom line: **more flip-flops, greater timing design problems**

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 18

The Clock Skew Problem

- In Single Phase Edge Triggered Clocking



§10.3.1

Brown
§7.15
§10.3.1


TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 19

The Clock Skew Problem

Clock Rates >> 1 Ghz in CMOS

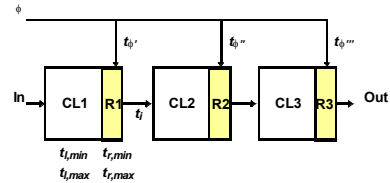


- Clock Edge Timing Depends upon Position
 - Because clock network forms distributed RC line with lumped load capacitances at multiple sites (see earlier slide)
- (Relative) Clock Skew $\delta = t_{\phi^2} - t_{\phi^1}$
- Clock skew can take significant portion of T_{clk}

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 20

Positive and Negative Skew

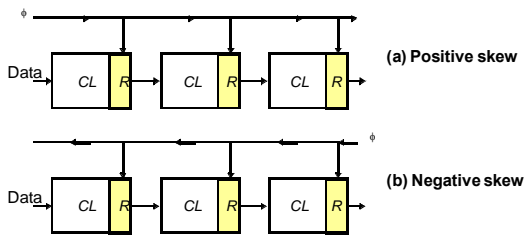


TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 21

Edge-Triggered Slow Path Skew Constraint

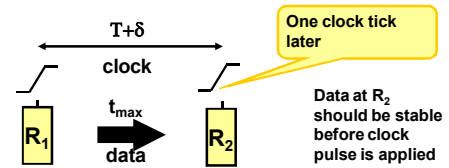

Timing constraint

$$T + \delta \geq t_{max} = t_{p,logic} + t_i + t_{c-q,max} + t_{su}$$

$$T \geq t_{max} - \delta$$


- Minimum Clock Period Determined by Maximum Delay between Latches minus skew

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 22

Edge-Triggered Fast Path Skew Constraint

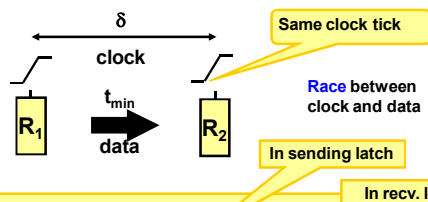

Timing constraint

$$\delta \leq t_{min} = t_{cd,logic} + t_i + t_{c-q,min} - t_{hold}$$

- Maximum Clock Skew Determined by Minimum Delay between Latches

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 23

Clock Constraints in Edge-Triggered Logic.

$$T \geq t_{max} - \delta$$

$$\delta \leq t_{min}$$

- Observe:
 - Minimum Clock Period Determined by Maximum Delay between Registers minus clock skew
 - Maximum Clock Skew Determined by Minimum Delay between Registers
- Conclude:
 - Positive skew must be bounded
 - Negative skew reduces maximum performance

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 24

Controlling Clock Skew

Case Study



§10.3.3

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 25

Countering Clock Skew Problems


- Routing the clock in **opposite direction** of data (negative skew)
 - Hampers performance
 - Dataflow not always uni-directional
 - Maybe at sub circuit (e.g. datapath) level
 - Other approaches needed at global chip-level
 - Useful skew (or beneficial skew) is serious concept
- Enlarging **non-overlap periods** of clock [only with two-phase clocking]
 - Hampers performance
 - Can theoretically always be made to work
 - Delay in clock network may require impractical/excessively large scheduled $T_{\phi 12}$ to guarantee minimum $T_{\phi 12}$ everywhere across chip
 - Is becoming less popular for large high performance chips

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 26

Dataflow not unidirectional

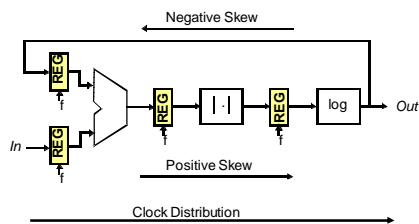

- Data and Clock Routing
- Cannot unambiguously route clock in opposite direction of data
- Need bounded skew

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 27

Need bounded Skew


- Bounded skew most practical measure to guarantee functional correctness without reducing performance
- Clock Network Design
 - Interconnect material
 - Shape of clock-distribution network
 - Clock driver, buffers
 - Clock-line load
 - Clock signal rise and fall times
 - ...

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 28

H-tree Clock Network

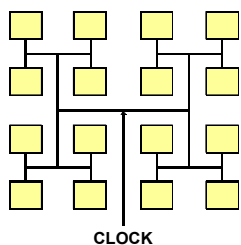

- All blocks equidistant from clock source \Rightarrow **zero (relative) skew**
- **Sub blocks** should be small enough to ignore intra-block skew
- In practice perfect H-tree shape **not realizable**


Observe: Only Relative Skew Is Important

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 29

Clock Network with Distributed Buffering



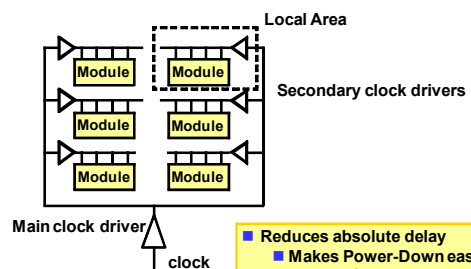


- Reduces absolute delay
 - Makes Power-Down easier
 - Easier of-chip communication
- Sensitive to variations in Buffer Delay

TUD/EE ET1205 D2 0910 - © NvdM

6/7/2010

7 timing 30

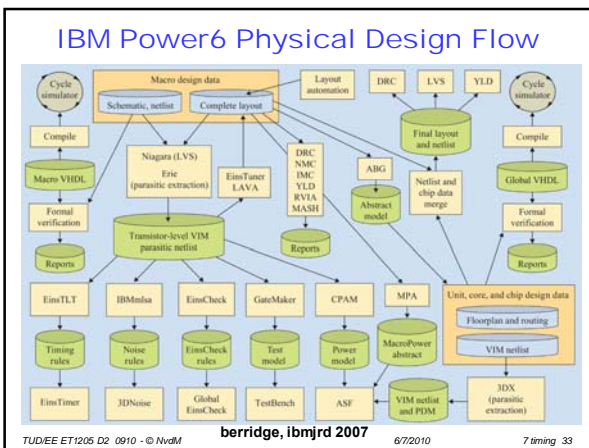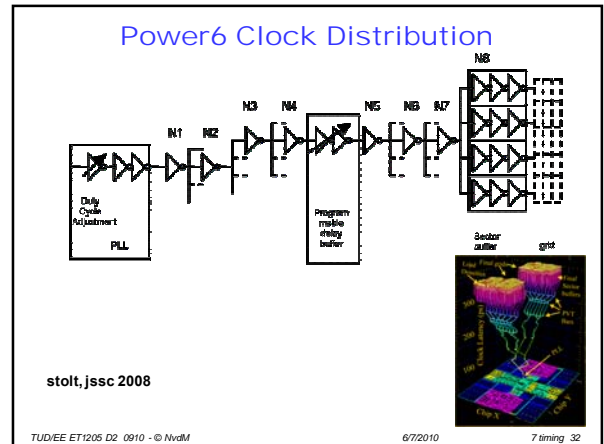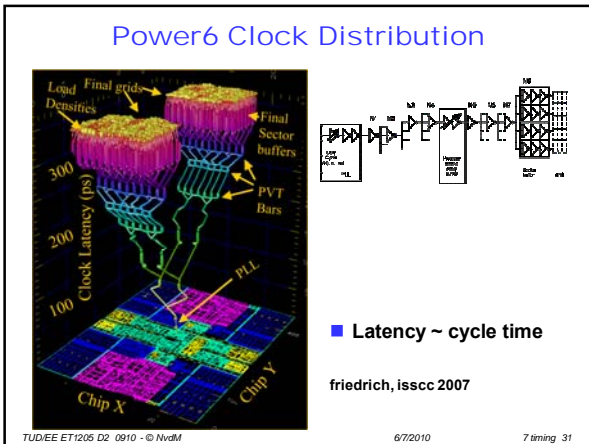

- ### Timing Design.
- Clocking Scheme is important design decision
 - Influences
 - Power
 - Robustness
 - Ease of design, design time
 - Performance
 - Area, shape of floor plan
 - Needs to be planned early in design phase
 - But is becoming design bottle neck nevertheless
 - Clock frequencies increase
 - Die sizes increase
 - Clock skew significant fraction of T_{clk}
 - Alternatives
 - Asynchronous or self-timed
- Not in this course 😊
- TUD/EE ET1205 D2 0910 - © NvdM 6/7/2010 7 timing 34

- ### Summary
- Timing Design Background and Motivation
 - Delay variations, impact
 - Sequential circuits, synchronous design
 - Pipelining, metrics reminder
 - The Clock Skew Problem
 - Controlling Clock Skew
 - Case Study
- Got basic appreciation of some system level design issues?
- TUD/EE ET1205 D2 0910 - © NvdM 6/7/2010 7 timing 35