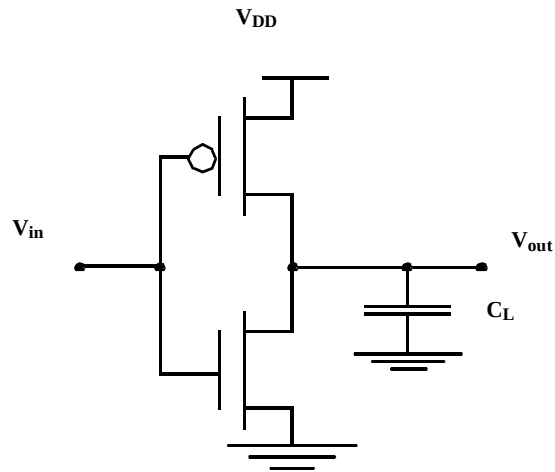


CMOS INVERTER

The CMOS Inverter - Outline

- **First Glance**
- **Digital Gate Characterization**
- **Static Behavior (Robustness)**
 - VTC
 - Switching Threshold
 - Noise Margins
- **Dynamic Behavior (Performance)**
 - Capacitances
 - Delay
- **Power**
 - Dynamic Power, Static Power, Metrics

The CMOS Inverter: A First Glance




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

3

CMOS Inverters (1)

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

4

CMOS Inverter Operation Principle

 


$$V_{OH} = V_{DD} \quad V_{OL} = 0$$



Digital Gate Fundamental Parameters

- Functionality
- Reliability, Robustness
- Area
- Performance
 - Speed (delay)
 - Power Consumption
 - Energy

The Ideal Inverter

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008


7

Static CMOS Properties

 

Basic inverter belongs to class of **static circuits**: output always connected to either V_{DD} or V_{SS} . **Not ideal but:**

 - Rail to rail voltage swing
- Ratio less design
- Low output impedance
- Extremely high input impedance
- No static power dissipation
- Good noise properties/margins



Exercise: prioritize the list above

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter


2/20/2008

8

Voltage Transfer Characteristic (VTC)



Load Line (Ckt Theory)

 

Exercise:

The **blue** load line A corresponds to $R =$

The **orange** load line B corresponds to $R =$

With load line A and $V_{GS} = 1V$, $V_{out} =$

Draw a graph $V_{out}(V_{in})$ for load line A and B

PMOS Load Lines



Goal: Combine I_{Dn} and I_{Dp} in one graph

Kirchoff:

$$V_{in} = V_{DD} + V_{GSp}$$

$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DSp}$$

  


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

11

CMOS Inverter Load Characteristics

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

12

CMOS Inverter VTC

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

13

Operating Conditions

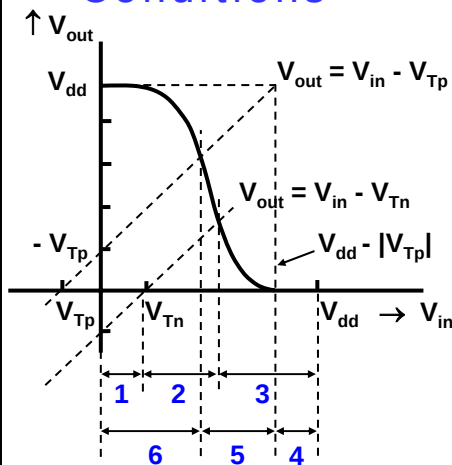Need to know for proper dimensioning, analysis of noise margin, etc.



Exercise: check results for PMOS

NMOS

- 1 $V_{in} = V_{GS} < V_{Tn} \Rightarrow$ **off**
- 2 $V_{out} > V_{in} - V_{Tn}$
 $V_{DS} > V_{GS} - V_{Tn}$
 $V_{GD} < V_{Tn} \Rightarrow$ **saturation**
- 3 $V_{out} < V_{in} - V_{Tn} \Rightarrow$ **resistive**

PMOS


- 4 $V_{in} > V_{DD} + V_{Tp} \Rightarrow$ **off**
- 5 $V_{out} < V_{in} - V_{Tp} \Rightarrow$ **saturation**
- 6 $V_{out} > V_{in} - V_{Tp} \Rightarrow$ **resistive**

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008


14

Operating Conditions

 

NMOS 1 off
2 saturation
3 resistive

PMOS 4 off
5 saturation
6 resistive

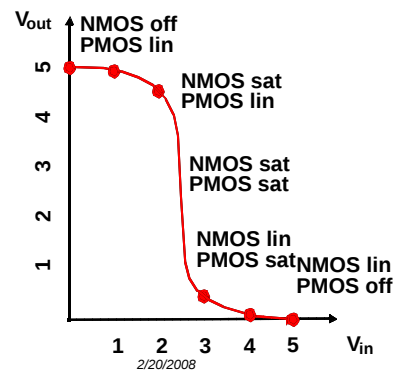

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

15

Inverter Static Behavior

- Regeneration
- Noise margins
- Delay metrics




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

16

The Realistic Inverter

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter


2/20/2008

17

The Regenerative Property

 

A chain of inverters

 

■ **Regenerative Property:** ability to regenerate (repair) a weak signal in a chain of gates




The regenerative property

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter


2/20/2008

18


The Regenerative Property (2)

 

(a) A chain of inverters.

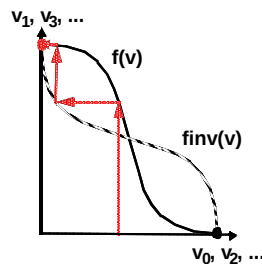


(b) Regenerative gate

 

(c) Non-regenerative gate

The regenerative Property (3)

 


Exercise: what is the output voltage of a chain of 4 inverters with a piece-wise linear VTC passing through (0, 10), (3,7), (7,1) and (10,0) [Volt], as the result of an input voltage of 6 [Volt].

Exercise: discuss the behavior for an input of 5 [Volt]

Inverter Switching Treshold


■ Not the device threshold $V_m = f(R_{onn}, R_{onp})$

■ Point of $V_{in} = V_{out}$

 

■ Try to set W_n, L_n, W_p, L_p so that VTC is symmetric as this will improve noise margins

optimize NMOS-PMOS ratio

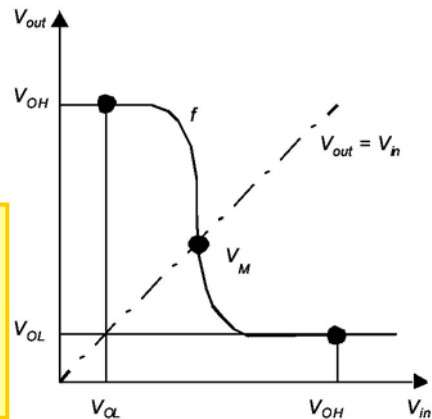


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

21

Simulated Gate Switching Threshold

 

Electrical Design Rule

$$W_p \approx 2.5 W_n$$

- Assumes $L_p = L_n$
- Should be applied consistently

■ Symmetrical VTC $\Rightarrow V_m \approx \frac{1}{2} V_{DD} \Rightarrow W_p/W_n \approx$

■ In practice: somewhat smaller

■ Why?

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

22

Inverter Switching Threshold Analytical Derivation



- V_M is V_{in} such that $V_{in} = V_{out}$
- $V_{DS} = V_{GS} \Leftrightarrow V_{GD} = 0 \Rightarrow$ saturation
 - Assume $V_{DSAT} < V_M - V_T$
 - (velocity saturation)
 - Ignore channel length modulation
- V_M follows from
 - $I_{DSATn}(V_M) = -I_{DSATp}(V_M)$

Inverter Switching Threshold Analytical Derivation (ctd)

$$I_{DSATn}(V_M) = -I_{DSATp}(V_M) \qquad I_D = kV_{DSAT}(V_{GS} - V_T - V_{DSAT}/2)$$

$$\Leftrightarrow k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2) = -k_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)$$


$$\Leftrightarrow \frac{k_p}{k_n} = \frac{-V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \qquad k = \frac{W}{L} k'$$

$$\Rightarrow \frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)}$$

- See Example 5.1:
- $(W/L)_p = 3.5 (W/L)_n$ for typical conditions and $V_M = \frac{1}{2} V_{DD}$
- Usually: $L_n = L_p$

Gate Switching Threshold w/o Velocity Saturation

 
- Long channel approximation
- Applicable with low V_{DD}



Exercise (Problem 5.1):
derive V_M for long-
channel approximation
as shown below

$$V_M = \frac{r(V_{DD} - V_{Tp} + V_{Tn})}{1+r} \text{ with } r = \sqrt{\frac{-k_p}{k_n}}$$


Noise in Digital Integrated Circuits

 

(a) Inductive coupling (b) Capacitive coupling (c) Power and ground noise

- Study behavior of static CMOS Gates with **noisy signals**

Noise Margins

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008

27

Noise Margins

 


- $NM_H = V_{OH} - V_{IH}$ = High Noise Margin
- $NM_L = V_{IL} - V_{OL}$ = Low Noise Margin

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 03 Inverter

2/20/2008


28

Noise Margin for Realistic Gates

 

Exercise: explain significance of slope = -1 for noise margin

Noise Margin Calculation

 

Piece-wise linear approximation of VTC

g = gain factor (slope of VTC)

We know how to compute V_M
Next: how to compute g

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$

