
 


Interconnect

 


Uien, Michael P. Giordano, October 2000.

Interconnect



- Wires are **not ideal** interconnections
- They may have non-negligible **capacitance, resistance, inductance**
- These are called **wire parasitics**
- Can **dominate** performance of chip
- Must be accounted for during **design**
- Using **approximate models**
- Detailed **post-layout verification** also necessary

Wires

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect


20-Feb-08

3 interconnect 3

Interconnect Hierarchy

 

Cross-section of IBM 0.13 μ process

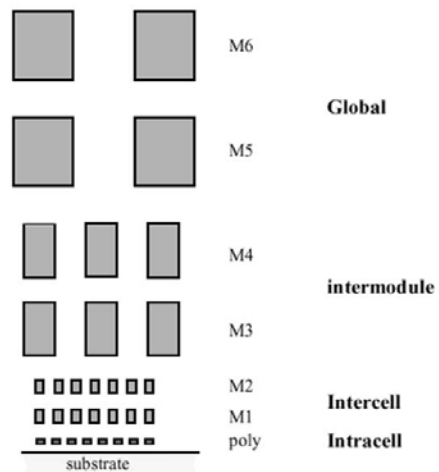

Example Interconnect Hierarchy for typical 0.25 μ process (Layer Stack)

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 4


Outline

- **Capacitance**
 - Area/perimeter model, coupling
- **Resistance**
 - Sheet resistance
- **Interconnect delay**
 - Delay metrics, rc delay, Elmore delay


Capacitance

- **Area/perimeter model, coupling**

Wire Capacitance - Parallel Plate

 
 
$$C = \frac{\epsilon_0 \epsilon_r w l}{d}$$




$$\frac{C}{l} = \epsilon_0 \epsilon_r \frac{w}{h}$$

$$\epsilon_0 = 8.85 \text{ pF/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

Wire Capacitance - Fringing Fields

 

$$C_{\text{wire}} = C_{\text{fringe}} + C_{\text{pp}} = \frac{2\pi\epsilon di}{\log(t_{di}/H)} + \frac{w\epsilon di}{t_{di}}$$

- Works reasonably well in practice
- Not directly applicable for interconnects with varying widths

Wire Capacitance – Area/Perimeter Model

- C_a was calculated with modified wire width
- Formula inapplicable for irregular interconnects (non-constant width)



- More practical approximation

$C = A \times C_a + P \times C_p$	units	alternative
A = Area	m^2	μm^2
C_a = Area capacitance	F / m^2	$aF / \mu m^2$
P = Perimeter	m	μm
C_p = Perimeter capacitance	F / m	$aF / \mu m$

$1\mu \updownarrow$

 10μ


$C = \square \times C_a + \square \times C_p$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 9

Area / Perimeter Capacitance Model

 

$$C = \square \times C_a + \square \times C_p$$


- **Question:** How to derive C_a, C_p ?

How accurate is this model?

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect


20-Feb-08

3 interconnect 10

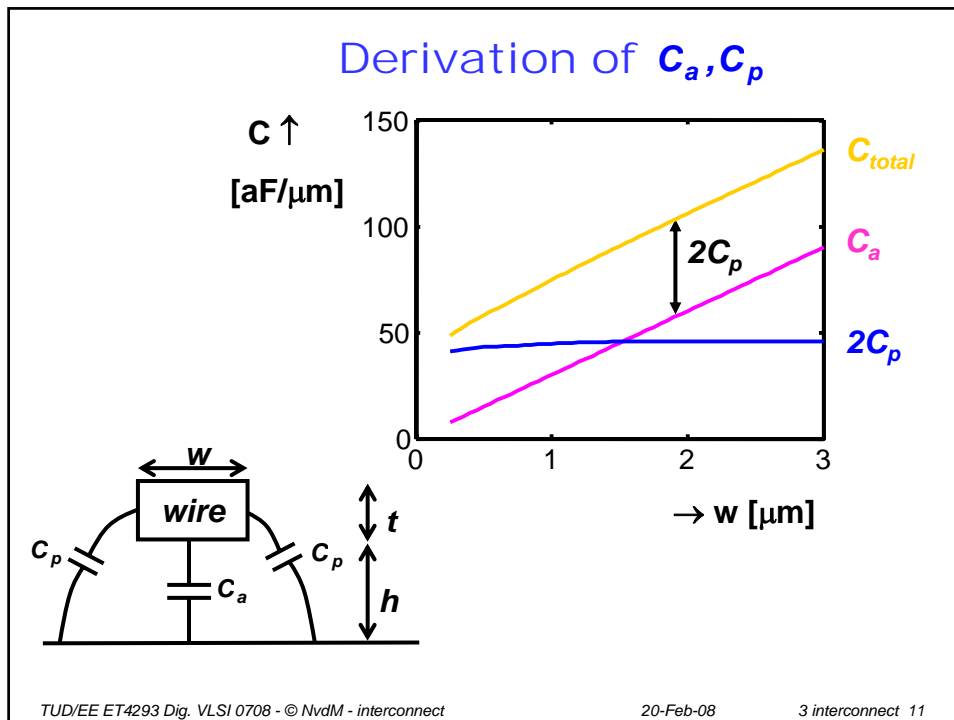

- ### Derivation of C_a, C_p
- 2D (cross-section) numerical computation (or measurement)
 - C_l : total wire capacitance per unit length
 - $C_a = \epsilon_0 \epsilon_r / h$
 - $C_p = 1/2 (C_l - C_a \times w)$
 - C_p depends on $t, h \rightarrow$ determined by technology, layer
 - C_p would depend slightly on w (see previous graph), this dependence is often ignored in practice
- TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect 20-Feb-08 3 interconnect 12

Area / Perimeter Capacitance

 

- C_p dominates for many wires
- C_p may not be neglected
- A constant value for C_p is usually a good approximation
- C_p is sometimes called C_f (fringe capacitance)


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 13

Interconnect Capacitance Design data

 - See Table 4.2 (or inside backside cover)
- Example: M1 over Field vs. M1 over Active (hypothetical)




M1 over Active	M1 over Field	Unit
$C_a = 41$	$C_a = 30$	$\text{aF}/\mu\text{m}^2$
$C_p = 47$	$C_p = 40$	$\text{aF}/\mu\text{m}$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 14

Coupling Capacitances

 


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 15

Coupling Capacitances (2)

 

- $C_T = C_{1g} + C_{12} = C_{2g} + C_{12}$ fairly constant
- Use that as first order model
- Interconnect capacitance design data (e.g. Table 4.3)

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect


20-Feb-08

3 interconnect 16

Resistance

- Sheet resistance

Wire Resistance

 


- Proportional to l
- Inversely proportional to w and t (cross-sectional area)
- Proportional to ρ : specific resistance, material property [Ωm]
- $R = \rho l / wt$
- Aluminum: $\rho = 2.7 \times 10^{-8} \Omega\text{m}$
- Copper: $\rho = 1.7 \times 10^{-8} \Omega\text{m}$

Sheet Resistance

- $R = \rho l/wt$
- t, ρ constant for layer, technology
- $R = R_s l/w$
- R_s : sheet resistance [Ω/\square]
resistance of a square piece of interconnect
other symbol: R_s
- Interconnect resistance design data e.g. Table 4.5 (or inside back-cover)

Interconnect Resistance

 - Assume $R_s = 40 \Omega$
- Estimate the resistance between A and B in the wire below.



Engineering is about making controlled approximations to something that is too complicated to compute exactly, while ensuring that the approximate answer still leads to a working (functional, safe, ...) system

Exercise


An interconnect line is made from a material that has a resistivity of $\rho = 4 \mu\Omega\text{-cm}$. The interconnect is 1200 \AA thick, where 1 Angstrom (\AA) is 10^{-10} m . The line has a width of $0.6 \mu\text{m}$.

- a) Calculate the sheet resistance R_{\square} of the line.
- b) Find the line resistance for a line that is $125 \mu\text{m}$ long.

Interconnect delay


- Delay metrics, rc delay, Elmore delay

Delay

 

- Model driver as linearized Thevenin source V , R_s , assume step input
- Model load as C_L
- Wire is an RC network (two-port)

Wire Capacitance

 


Assume wire behaves purely capacitive

$$(C_w + C_L) \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_s} = 0$$

$$V_{out} = V_{in} - \tau \frac{dV_{out}}{dt} \quad \tau = R_s(C_w + C_L)$$

$$V_{out} = (1 - e^{-t/\tau}) V_{in}$$


Wire Resistance

 


Now, assume wire capacitance *and* resistance

- $\tau = (R_s + R_w)(C_w + C_L)$
- Not a good model
- R and C are **distributed** along the wire


Uniform RC Line

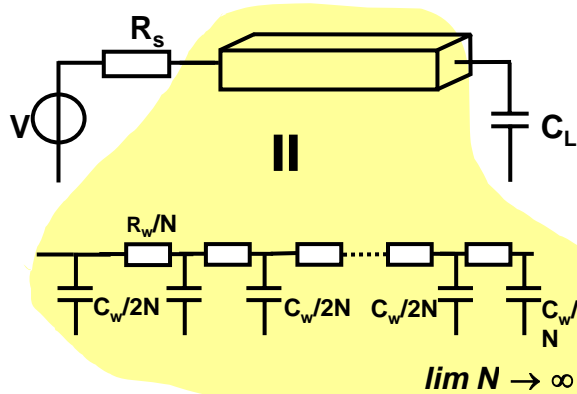


Symbol

 

[Always] use first order model

 

RC Delay (Uniform RC Line)

 


- Not 1τ
- Elmore delay: equivalent effective τ

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08

3 interconnect 27

Equivalent Time Constant

 

- Multiple time-constants
- Need for one “equivalent” number
- Offered by *Elmore Delay* T_D

$$T_D = R_S C_W / 2 + (R_S + R_W)(C_W / 2 + C_L)$$

- Effective “one number” model for delay



How to compute Elmore Delay?

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - interconnect

20-Feb-08


3 interconnect 28

Equivalent Time Constant

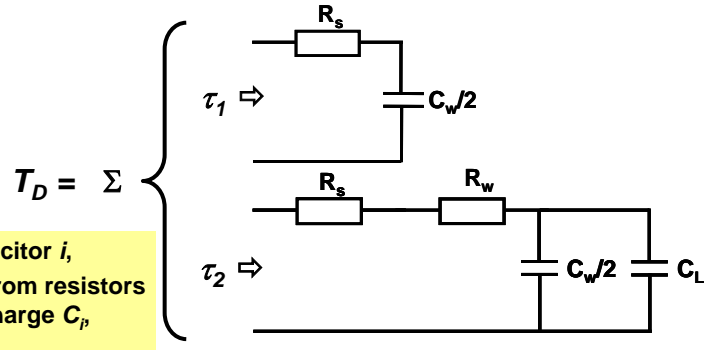 


For each capacitor i ,
 Determine τ_i from resistors
 that (dis)charge C_i ,
 Sum these τ_i

Shared Path Resistance

 

- Define: R_{ij} = Resistance from node i to input
- Example: $R_{11} = R_1$ $R_{22} = R_1 + R_2$ $R_{33} = R_1 + R_2 + R_3$
- Define: R_{ik} = Shared path resistance to input for node i and k
- $R_{12} = R_1$ $R_{13} = R_1$ $R_{23} =$

Elmore Delay for RC ladders

 

■ Define: $T_{Di} = \sum_{k=1}^N R_{ik} C_k$

Elmore Delay


We will use $0.69 \times T_{di}$ as approximation of wire delay ($t_{50\%}$)

■ $T_{D1} = R_{11}C_1 + R_{12}C_2 + R_{13}C_3 =$
 $= R_1C_1 + R_1C_2 + R_1C_3$


$T_{D3} = R_{31}C_1 + R_{32}C_2 + R_{33}C_3 =$
 $= R_1C_1 + (R_1 + R_2)C_2 + (R_1 + R_2 + R_3)C_3$

■ $T_{D2} =$


Elmore Delay for Distributed RC Lines

 

Symbol

 


Symmetric π -model

 

■ **Theorem:** For Elmore Delay calculations, each uniform distributed RC section is equivalent to a symmetric π -model

Canonical Driver-Line-Load

 


$$\begin{aligned} \blacksquare T_{D1} &= R_s \frac{cl}{2} + (R_s + rl) \left(C_L + \frac{cl}{2} \right) \\ &= R_s (cl + C_L) + rl C_L + \frac{1}{2} rcl^2 \end{aligned}$$

■ Delay quadratic in line length

Shared Path Resistance for Tree Structures

In order to compute Elmore Delay at node 3:

 
Exercise (for node 4):
Compute R_{41} , R_{42} , R_{43} , R_{44}



$R_{31}?$	R_1
$R_{32}?$	$R_1 + R_2$
$R_{33}?$	$R_1 + R_2 + R_3$
$R_{34}?$	$R_1 + R_2$


Off-path resistances don't count

Elmore Delay for Tree Structures

 

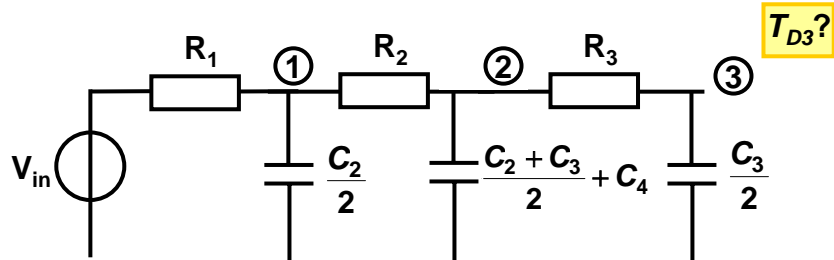Exercise: Compute T_{D1} , T_{D2} , T_{D3} , T_{D4}

- Replace RC lines by π -sections
- Given observation node i , then only resistances along the path from input to node i can possibly count
- Make others zero
- Compute as if RC ladder



Summary

- Capacitance
 - Area/perimeter model, coupling
- Resistance
 - Sheet resistance
- Interconnect delay
 - Delay metrics, rc delay, Elmore delay