

## Power

- Dynamic Power
- Static Power
- Metrics



[www.quitpc.com](http://www.quitpc.com)

24 hours audio  
playback time

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

1

## CMOS Power Dissipation

- Power dissipation is a **very important** circuit characteristic
- CMOS has relatively low static dissipation
- Power dissipation was the reason that CMOS technology won over bipolar and NMOS technology for digital IC's
- (Extremely) high clock frequencies increase dynamic dissipation
- Low  $V_T$  increase leakage
- Advanced IC design is a continuous struggle to contain the power requirements!



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

2

## Power Density



### Estimate

- Furnace: 2000 Watt,  $r=10\text{cm}$  →  $P \approx 6\text{Watt/cm}^2$
- Processor chip: 100 Watt,  $3\text{cm}^2$  →  $P \approx 33\text{Watt/cm}^2$

**Power-aware design, design for low power, is blossoming subfield of VLSI Design**

## Where Does Power Go in CMOS


- **Dynamic Power Consumption**  
Charging and discharging capacitors
- **Short Circuit Currents**  
Short circuit path between supply rails during switching (NMOS and PMOS on together)
- **Leakage**  
Leaking diodes and transistors  
May be important for battery-operated equipment

## Dynamic Power

### Dynamic Power

- $E_i$  = energy of switching event  $i$ 
  - independent of switching speed
  - depends on process, layout
- Power = Energy/Time
 
$$P = \frac{1}{T} \sum_i E_i$$
- $E_i$  = Power-Delay-Product P-D
  - important quality measure
- Energy-Delay-Product E-D
  - combines power\*speed performance

## Low-to-High Transition Energy

 


Equivalent circuit for **low-to-high** transition

$E_C$  - Energy stored on  $C$

$$\begin{aligned}
 E_C &= \int_0^{\infty} i v_0 dt & v_0 &= v_0(t) & i &= i(t) = C \frac{dv_0}{dt} \\
 &= \int_0^{\infty} C v_0 \frac{dv_0}{dt} dt \\
 &= \int_0^{V_{DD}} C v_0 dv_0 = \frac{1}{2} C v_0^2 \Big|_0^{V_{DD}} = \frac{1}{2} C V_{DD}^2
 \end{aligned}$$

## Low-to-High Transition Energy

 

$E_{V_{DD}}$  Energy delivered by supply


$$E_{V_{DD}} = \int_0^{\infty} i(t) V_{DD} dt = \int_0^{V_{DD}} C V_{DD} \frac{dv_0}{dt} dt = C V_{DD}^2$$

$$E_{V_{DD}} = C V_{DD}^2 \quad E_c = \frac{1}{2} C V_{DD}^2$$

Where is the rest?



## Low-to-High Transition Energy

 


$E_{diss}$  Energy dissipated in transistor

$$\begin{aligned} E_{diss} &= \int_0^{\infty} i(V_{DD} - v_0) dt \\ &= \int_0^{\infty} i V_{DD} dt - \int_0^{\infty} i v_0 dt \\ &= E_{V_{DD}} - E_c \end{aligned}$$



## High-to-Low Transition Energy

 


**Exercise:** Show that the energy that is dissipated in the transistor upon discharging C from  $V_{DD}$  to 0 equals  $E_{diss} = \frac{1}{2}CV_{DD}^2$

## CMOS Dynamic Power Dissipation

$$\begin{aligned} \text{Power} &= \frac{\text{Energy}}{\text{Time}} = \frac{\text{Energy}}{\text{transition}} \times \frac{\#\text{transitions}}{\text{time}} \\ &= CV_{DD}^2 \times f \end{aligned}$$


- Independent of transistor on-resistances
- Can only reduce C,  $V_{DD}$  or  $f$  to reduce power

## Short Circuit Current

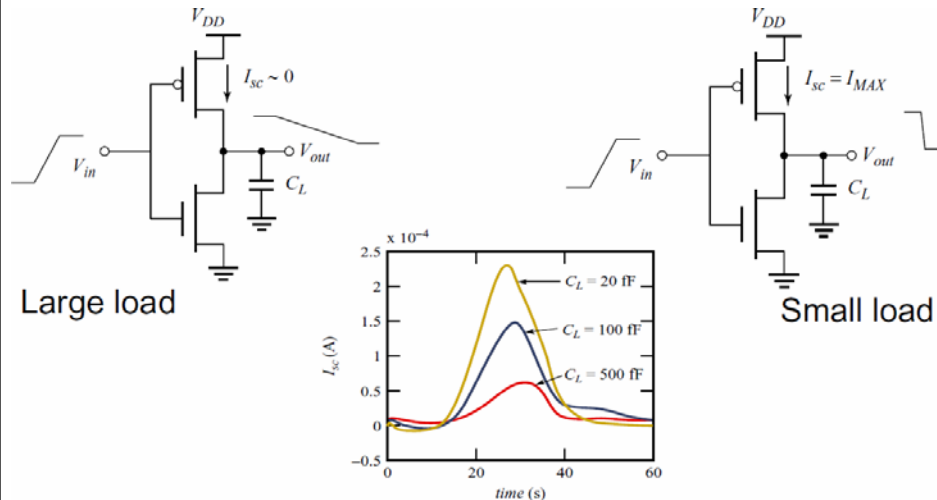

**Best to maintain approximately equal input/output slopes**

## Short Circuit Current

 


- **Input and output** waveforms of inverter loaded with a large capacitance (top) and with a small capacitance (bottom).
- **Shaded area** is where both pull-up and pull-down transistors are on (this is when short-circuit current can exist). This region is determined by crossings of input waveform with  $V_{Tn}$  and  $V_{DD} - |V_{Tp}|$ .
- Short-circuit current increases with  $|V_{Dsp}|$ . This is clearly much larger for small  $C_L$  compared to large  $C_L$ .
- Similarly, short-circuit current can exist for low-to-high transition at output.
 
# Leakage

- **Leakage current** of reverse biased S/D junctions
- **Sub-threshold current** of MOS devices
  - no channel → **parasitic bipolar device**:  
n+ (source) – p (bulk) – n+ (drain)
  - Important source of leakage



$$I_D = I_0 e^{\frac{qV_{GS}}{nkT}} \left( 1 - e^{-\frac{qV_{DS}}{kT}} \right) (1 + \lambda \cdot V_{DS})$$



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

13

## Sub-Threshold Current

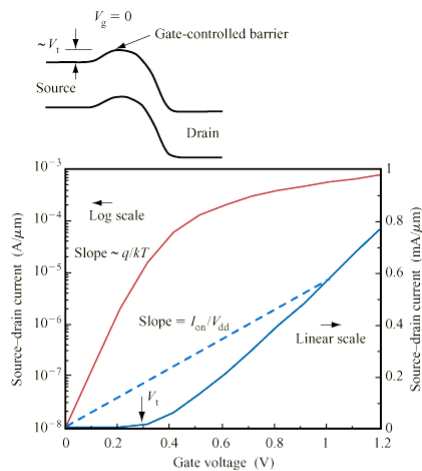


Figure 2

MOSFET current in both logarithmic (left) and linear (right) scales vs. gate voltage. The slope of the dotted line represents the large-signal transconductance for a digital circuit. Inset shows the band diagram of an n-MOSFET. The barrier height at  $V_g = 0$  is proportional to  $V_t$ .

- Rapidly becomes bottleneck with lowering threshold voltages
- Modern technologies offer low-Vt and hi-Vt devices  
Balance speed and power


Y. Taur, CMOS design near the limit of scaling, IBMJRD, Volume 46, Numbers 2/3, 2002

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

14

## Transistor Sizing for Minimum Energy

 

- Goal: Minimize Energy of whole circuit

- Design parameters:  $f$  and  $V_{DD}$

- $t_p \leq t_{pref}$  of circuit with  $f = 1$  and  $V_{DD} = V_{ref}$



$$t_p = t_{p0} \left( \left( 1 + \frac{f}{\gamma} \right) + \left( 1 + \frac{F}{f\gamma} \right) \right) \quad (\text{For this particular case of } N=2)$$

$$t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

See Eq. 5.21

$V_{TE} = V_T - \frac{1}{2}V_{DSAT}$  : Effective  $V_T$

## Transistor Sizing (2)

$$t_p = t_{p0} \left( \left( 1 + \frac{f}{\gamma} \right) + \left( 1 + \frac{F}{f\gamma} \right) \right) \quad t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

Performance Constraint ( $\gamma = 1$ ):

$$\frac{t_p}{t_{pref}} = \frac{t_{p0}}{t_{p0ref}} \frac{\left( 2 + f + \frac{F}{f} \right)}{(3 + F)} = \frac{V_{DD} V_{ref} - V_{TE}}{V_{ref} V_{DD} - V_{TE}} \frac{\left( 2 + f + \frac{F}{f} \right)}{(3 + F)} = 1$$


Energy for single Transition:

$$E = V_{DD}^2 \underbrace{C_{g1} + C_{int}}_{\text{Size of 1st + 2nd inverter}} \left[ (1 + \gamma)(1 + f) + F \right]$$

$$\frac{E}{E_{ref}} = \left( \frac{V_{DD}}{V_{ref}} \right)^2 \left( \frac{2 + 2f + F}{4 + F} \right) \quad C_L = FC_{G1}$$



## Transistor Sizing (3)

 

- Device sizing is effective
- Oversizing is expensive for power
- Optimal sizing for energy slightly different from sizing for performance

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

17

## Technology Scaling

Also see: IBM JRD, Vol 46, no 2/3, 2002

Scaling CMOS to the limit

<http://www.research.ibm.com/journal/rd46-23.html>




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

18

## Moore's Law

 

The number of transistors that can be integrated on a single chip will double every 18 months

Gordon Moore, co-founder of Intel  
[Electronics, Vol 38, No. 8, 1965]



## Why Scaling

- Reduce **price per function**:
  - Want to sell more functions (transistors) per chip for the same money → **better products**
  - Build same products cheaper, sell the same part for less money → **larger market**
  - Price of a transistor has to be reduced
- But also want to be **faster, smaller, lower power**

## Scaling Models

### Fixed Voltage Scaling

- most common model until 1990's
- only dimensions scale, voltages remain constant

### Full Scaling (Constant Electrical Field)

- ideal model — dimensions and voltage scale together by the same factor  $S$

### General Scaling

- most realistic for today's situation —
- voltages and dimensions scale with different factors

## Scaling for Velocity Saturated Devices

Constant Field Scaling:  $S = U$

Parameter	Relation	General Scaling
$W, L, t_{ox}$		$1/S$
$V_{DD}, V_T$		$1/U$
$N_{SUB}$	$V / W_{depl}^2$	$S^2/U$
Area / Device	$WL$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$
$C_{gate}$	$C_{ox} W L$	$1/S$
$k_n, k_p$	$C_{ox} W / L$	$S$
$I_{sat}$	$C_{ox} W V$	$1/U$
Current Density	$I_{sat} / \text{Area}$	$S^2/U$
$R_{on}$	$V / I_{sat}$	$1$
Intrinsic Delay	$R_{on} C_{gate}$	$1/S$
Power / Device	$I_{sat} V$	$1/U^2$
Power Density	$P / \text{Area}$	$S^2/U^2$

## IC Technology Scaling

Scaling improves density and **performance**

### ■ First order **scaling theory**

		<u>2008 / 1971</u>
■ dimensions,	1/S	0.007
■ voltages	1/S	0.007
■ intrinsic delay	1/S	0.007
■ power per transistor	1/S <sup>2</sup>	0.00004

### ■ Scaling **trend**



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

23

## Technology Practice & ITRS

### ■ Scaling – Technology Generations

■  $S \approx 1.4 \approx 2^{0.5}$  per generation

■ ... – 250 – 180 – 130 – 90 – 65 – 45 – 35 – 22 – ... nm

### ■ ITRS: International Technology Roadmap for Semiconductors

Industry-wide organization for forecasting technology developments – and (planning) requirements



<http://www.itrs.net/home.html>



Not really – it is more like science  
(and a self-fulfilling prophecy at the same time)

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling


3/5/2008

24



# International Technology Roadmap for Semiconductors
 
## 2007 ITRS Product Technology Trends - Functions per Chip




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

25


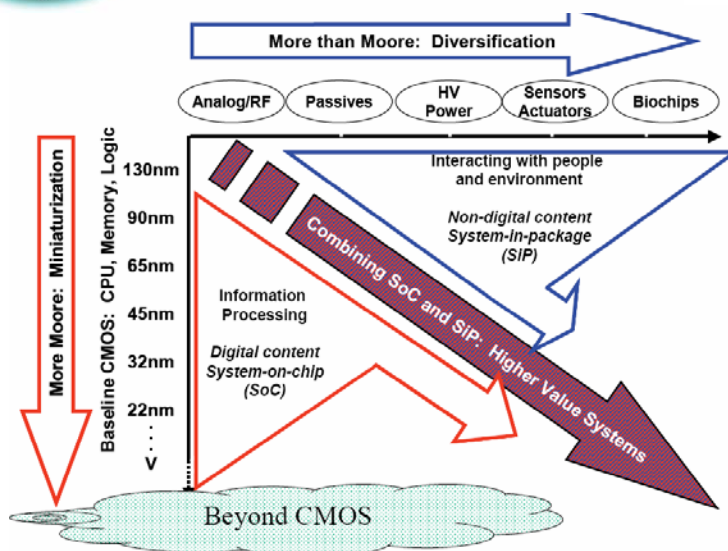
# International Technology Roadmap for Semiconductors



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 07 inverter power and scaling

3/5/2008

26

## Summary

- Digital Gate Characterization (§ 1.3)
- Static Behavior (Robustness) (§ 5.3)
  - VTC
  - Switching Threshold
  - Noise Margins
- Dynamic Behavior (Performance) (§ 5.4)
  - Capacitances
  - Delay
- Power (§ 5.5)
  - Dynamic Power, Static Power, Metrics
- Scaling (§ 5.6)