

COMBINATIONAL LOGIC

Exam

- April 3rd, 9am – 12am
- Written exam, open book, also printed slides with your notes on it.

Material	Topic	Remarks
Ch 1	Intro	Completely, pay attention to §1.3
Ch 2	Manufacturing	Only §2.1 - §2.3
Ch 3	Devices	Completely
Ch 4	Interconnect	Except §4.4.5, §4.5
Ch 5	Inverter	Completely
Ch 6	Combinational	Only §6.1, §6.2
Ch 7	Sequential	Only §7.1, §7.2

- **Final Lecture:**
March 25, 10:45-12:30
- **Room D** (*probably*)
- **§7.1 – 7.2**

March 2008			
Thu 20	Tue 25		
15:45-17:30	8:45-10:30	10:45-12:30	13:45-15:30
OK		OK	OK
OK	OK	OK	OK
	OK	OK	OK
		OK	
	OK	OK	OK
		OK	OK
	OK	OK	
	OK	OK	OK
	OK	OK	OK
		OK	
		OK	
	OK	OK	OK
OK		OK	
	OK	OK	OK
		OK	OK
		OK	
	OK	OK	OK
□	□	□	□
15:45-17:30	8:45-10:30	10:45-12:30	13:45-15:30

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

3

Combinational Logic - Outline

- **Conventional Static CMOS basic principles**
- **Complementary static CMOS**
 - **Complex Logic Gates**
 - **VTC, Delay and Sizing**
- **Ratioed logic**
- **Pass transistor logic**
- **Dynamic CMOS gates → only illustration**

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

4


Complementary Static CMOS Basic Principles

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

5

Combinational vs. Sequential Logic

 

(a) Combinational

(b) Sequential



§ 6.2

Output = $f(\text{In})$ Output = $f(\text{In}, \text{History})$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

6

Reminder

DeMorgan Transformations

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational


3/19/2008

7

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a **switch** controlled by its gate signal

 NMOS switch **closes** when switch control input is **high**



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational


3/19/2008

8


PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is **low**

$Y = X$ if ...

 

$Y = X$ if \bar{A} and \bar{B}

 


$Y = X$ if \bar{A} or \bar{B}

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

9

2-Input Nand

 

$Y = 1$ if \bar{A} OR \bar{B}
 $Y = 1$ if $\overline{A \text{ AND } B}$

DeMorgan

$Y = \overline{A \text{ AND } B}$



$Y = 0$ if $A \text{ AND } B$

B	A	Y
0	0	1
0	1	1
1	0	1
1	1	0


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

10

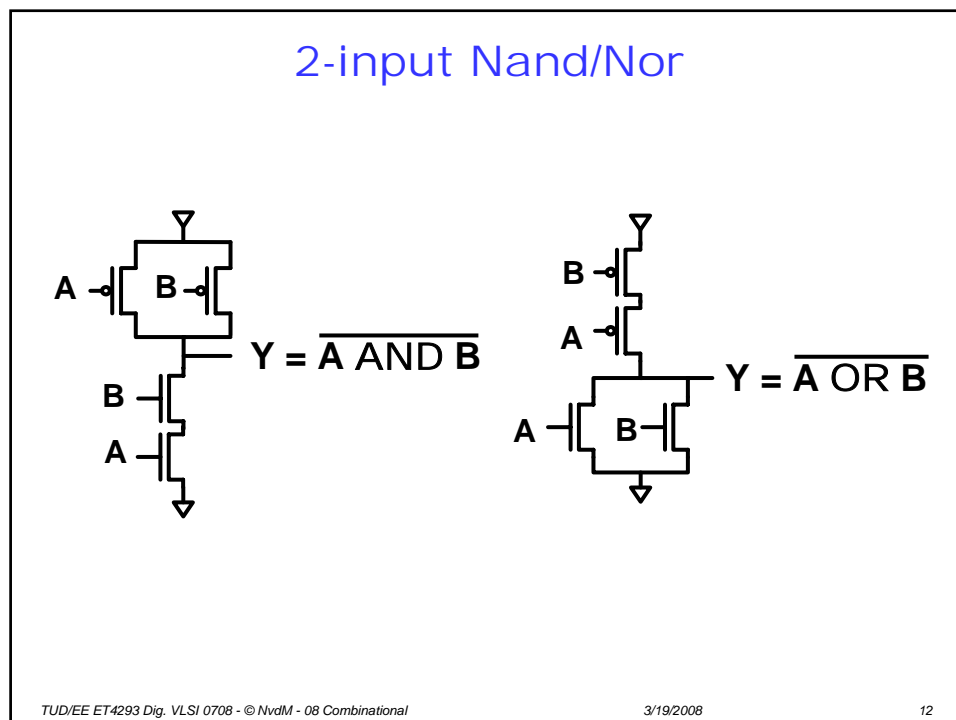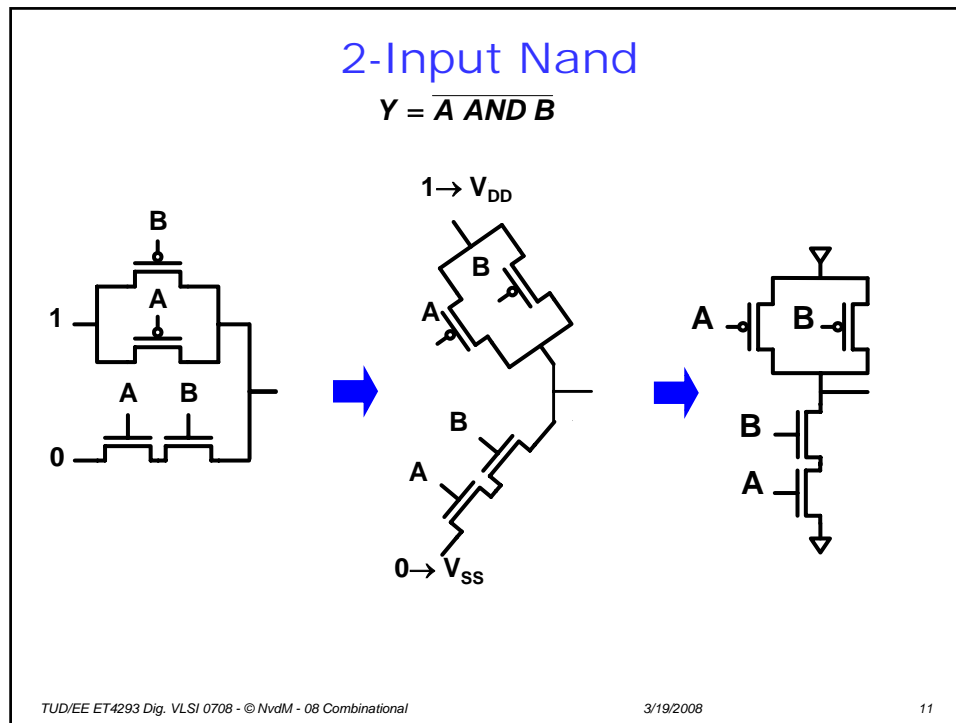

NMOS vs. PMOS, pull-down vs. pull-up

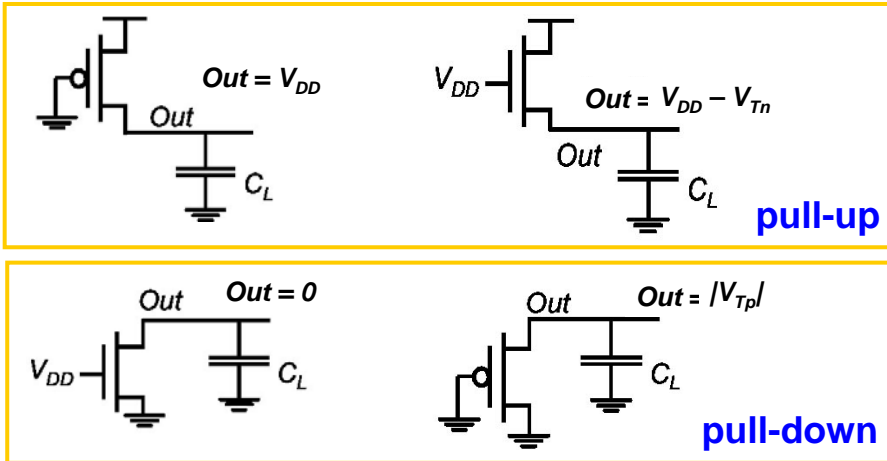


- PMOS is better pull-up
- NMOS is better pull-down

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

13

Bad Idea

 

Exercise: Determine logic function

Determine V_{out}
for $V_{in} = V_{DD}$ and $V_{in} = V_{SS}$

Why is this a bad circuit?

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

14

CMOS Gate is Inverting

Assume full-swing inputs (high = V_{DD} , low = V_{SS})

- Highest output voltage of NMOS is

$$V_{GS} - V_{Tn} = V_{DD} - V_{Tn}$$

- An 1 on **NMOS** gate can produce a **strong 0** at the drain, but not a strong 1

- Lowest output voltage of PMOS is

$$V_{DD} + V_{GS} - V_{Tp} = |V_{Tp}|$$

(with $V_{GS}, V_{Tp} < 0$ for PMOS)

- An 0 on **PMOS** gate can produce a **strong 1** at the drain, but not a strong 0

- Need NMOS for pull-down, PMOS for pull-up

A 1 at input can pull-down, 0 at input can pull-up

Inverting behavior

For a non-inverting Complementary CMOS Gate, you can only use 2 inverting gates

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

15

Complementary static CMOS


- Complex Logic Gates
- VTC, Delay and Sizing

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

16

Complementary Static CMOS

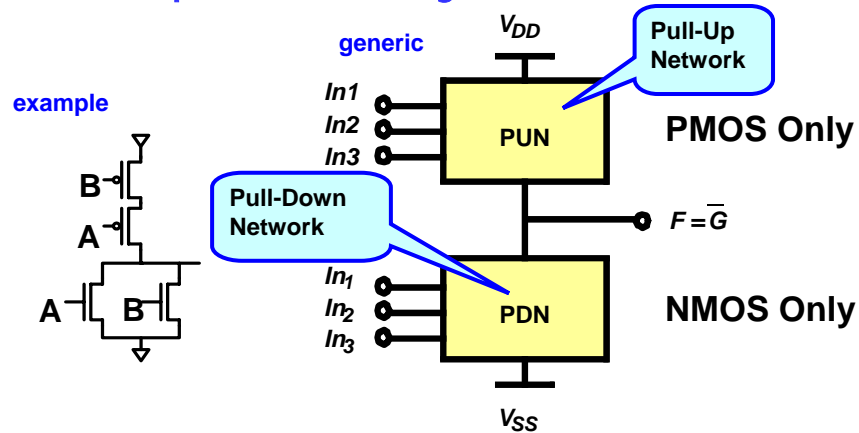

- Conduction of PDN and PUN must be mutually exclusive (Why?)
- Pull-up network (PUN) and pull-down network (PDN) are **dual**


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

17

Mutual Exclusive PDN and PUN

$$\text{Out} = (AB + C)'$$

 

C	B	A	P D N	P U N	Out
0	0	0	?	1	1
0	0	1	?	1	1
0	1	0	?	1	1
0	1	1	0	?	0
1	0	0	0	?	0
1	0	1	0	?	0
1	1	0	0	?	0
1	1	1	0	?	0

PUN Off
PDN On

PUN Off
PDN On

For all **Complementary Static CMOS Gates**, either the PUN or the PDN is conducting, but never both.

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

18

Complementary Static CMOS (2)

- Conduction of PUN and PDN must be **mutually exclusive**
- PUN is **dual (complement)** network of PDN
series \Leftrightarrow parallel
nmos \Leftrightarrow pmos
- Complementary gate is **inverting**
- No static power dissipation
- Need 2N transistors for N-input gate

Implementation of Combinational Logic

- How can we construct an arbitrary combinational logic network in general, using NMOS and PMOS transistors (using Complementary static CMOS)?

■ Example: $Y = \overline{(A + BC)}D$


- Remember: only inverting gates available



Ex. 6.2

Implementation of Combinational Logic

 - Example: $Y = \overline{(A + BC)}D$
- Remember: only inverting gates available
- Logic depth: number of gates in longest path \Rightarrow DELAY



transistors logic depth

- Q: Can this be improved?


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

21

Improved Gate Level Implementation

 - Using DeMorgan $A + BC = \overline{\overline{A} \cdot \overline{BC}}$



- Q: Can this be further improved?


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

22

Complex CMOS Logic Gates

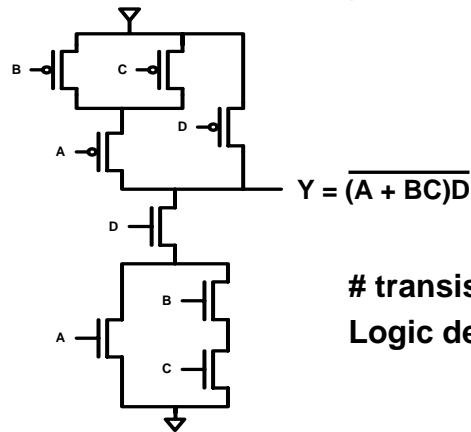- Restriction to basic NAND, NOR etc. **not necessary**
- Easy to synthesize **complex gates**



$$Y = (A + BC)D$$

transistors: 8

Logic depth: 1


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

23

How to Synthesize Complex Gates

$$Y = (A + BC)D$$

 

- Using tree representation of Boolean function

- **Operator** with branches for **operands**

- As a **series-parallel** network

	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008


24

Complex Gate Synthesis Example

$$\bar{Y} = (A + (BC))D$$

 

	PDN	PUN
AND	Series	Parallel
OR	Parallel	Series

 

Recipe



- Write $Y = f(\text{inputs})$
- Decompose f in tree form
- Realize tree branches according to table at bottom-left
- Use inverted inputs if necessary

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

25

And-Or-Invert Gate

  

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

26

And-Or-Invert Example


■ From a Truth-Table: take 0-outputs

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\rightarrow \bar{A}BC$

$\rightarrow A\bar{B}C$

$$\bar{Y} = \bar{A}BC + A\bar{B}C$$

 


\bar{A}, \bar{B} to be created with extra inverters (or by restructuring previous circuits)

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008


27

And-Or-Invert Improvement

 

$$Y = \overline{\bar{A}BC + A\bar{B}C}$$

12 transistors

 

$$Y = \overline{(\bar{A}B + A\bar{B})C}$$

10 transistors


2-level logic minimization: boolean algebra technique

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

28

CMOS Complex Gate Sizing

 

- Function of gate independent of transistor sizes: ratio-less
- But current-drive capability (timing) depends on transistor sizes
- Worst-case current-drive depends on number of transistors in series

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

29

CMOS Complex Gate Sizing


- Assume all transistors will have minimum length L
- Determine W_n for PDN transistor of inverter that would give the desired 'drive strength'
- For each transistor in PDN of complex gate do the following:
 - Determine the length l of the longest PDN chain in which it participates
 - Set $W = l W_n$
- Repeat this procedure for PUN, using W_p for PUN transistor of inverter.

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

30

Gate Sizing

 


- W/L ratios
 - what are the W/L of 2-input NAND for same drive strength?
- 0-th order calculation**

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational


3/19/2008

31

Exercise

 

(a)

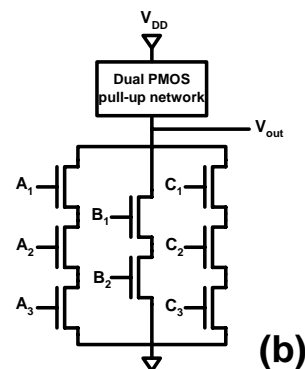

(b)

Exercise:


- Perform gate sizing of (a) for nominal drive strength equal to that of min size inverter, **assume $PU/PD = 3$**
- Determine PUN of (b)
- Perform gate sizing of (b) for same drive strength (same PU/PD)
- Compare sum of gate areas in (a) and (b). Note: area \sim width

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

32

Avoid Large Fan-In

 

C linear in N

R linear in N

Delay \propto RC **quadratic** in N

Empirical


Delay = $a_1 FI + a_2 FI^2 + a_3 FO$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

33


Data-Dependent Timing

 

$$t_{PHL} = 0.69R_N C_L$$

$$t_{PLH} = 0.69R_P C_L$$

 You should be able to identify the transistor paths that charge or discharge C_L , and calculate resulting RC delay model, including effects of wires and fan-out



$$t_{PHL} = 0.69(R_N \times 2)C_L$$

$$t_{PLH} = 0.69R_p C_L$$

$$t_{PLH} = 0.69(R_p/2)C_L$$

Series connection

One input goes low



Two inputs go low, **parallel** connection

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

34

Data-dependent VTC: 2nd order effects

  



- Charge at 'int'
- Body effect in M_2
- Short-circuit currents

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

35

Data-dependent Timing

  

Input Data Pattern	Delay (pS)
$A = B = 0 \rightarrow 1$	69
$A = 1, B = 0 \rightarrow 1$	62
$A = 0 \rightarrow 1, B = 1$	50
$A = B = 1 \rightarrow 0$	35
$A = 1, B = 1 \rightarrow 0$	76
$A = 1 \rightarrow 0, B = 1$	57

$A=1, B=\downarrow$: need to charge *int*
 $A=\downarrow, B=1$: *int* does not need to be charged
 $A=\downarrow, B=\downarrow$: twice the pull-up strength

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

36

Logical Effort Methodology

Inverter delay: $t_p = t_{p0} \left(1 + \frac{f}{\gamma} \right)$

Gate delay: $t_p = t_{p0} \left(p + \frac{gf}{\gamma} \right) = t_{p0} \left(p + \frac{h}{\gamma} \right)$

Logical Effort Methodology Definitions:

- p** ratio of intrinsic delay compared to inverter
- f** electrical effort – ratio between C_{load} and C_{in}
- g** logical effort – ratio of drive strength for same size
- h** gate effort – $h = f \cdot g$


[Logical Effort – Designing Fast CMOS Circuits,
Sutherland, Sproul, Harris]

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

37

Intrinsic Delay

 

- p** ratio of intrinsic delay compared to inverter
- p** is ratio of output capacitances if gate is sized for identical drive strength

p_{nand}
is $(2+2+2)/(2+1) = 2$


$$t_p = t_{p0} \left(p + \frac{gf}{\gamma} \right)$$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

38

Logical Effort

 

g logical effort – ratio of drive strength for same size

g same as ratio of input cap for same strength

g_{nand} is $(2+2)/(2+1) = 4/3$

$$t_p = t_{p0} \left(p + \frac{gf}{\gamma} \right)$$


- Logical effort: a multi-input gate has more input cap compared to inverter for same drive strength
- Needs to be corrected for in delay calculations
- Can be done by inclusion in electrical effort: replace f by $g \cdot f$

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

39

Logical Effort

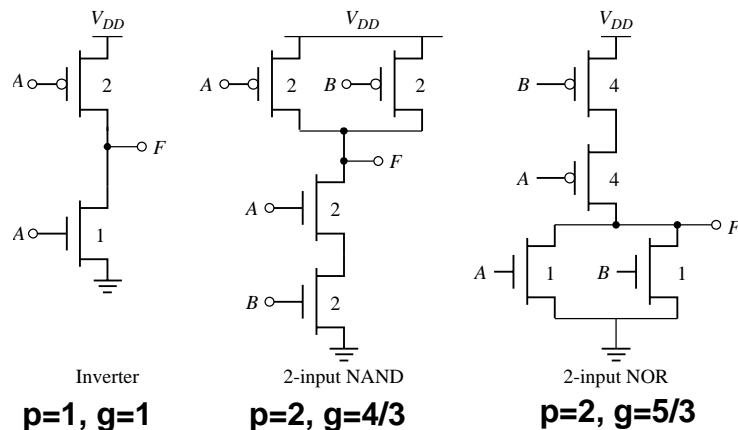

p ratio of intrinsic delay compared to inverter

g logical effort – ratio of drive strength for same size


p, g independent of sizing, only topology of circuit

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

40

Delay vs Fan-Out

 

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational


3/19/2008

41

Add Branching Effort

Branching effort:
 
$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$



TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

42

Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + g_i \cdot f_i)$$

Normalized w.r.t. unit delay

Stage effort:	$h_i = g_i f_i$
Path electrical effort:	$F = C_{out}/C_{in}$
Path logical effort:	$G = g_1 g_2 \dots g_N$
Branching effort:	$B = b_1 b_2 \dots b_N$
Path effort:	$H = GFB$
Path delay	$D = \sum d_i = \sum p_i + \sum h_i$

Optimum Effort per Stage

When each stage bears the same effort:

$$h^N = H$$

$$h = \sqrt[N]{H}$$

Stage efforts: $g_1 f_1 = g_2 f_2 = \dots = g_N f_N = h$

Effective fanout of each stage: $f_i = h/g_i$

larger fanout for simpler stages

Minimum path delay

$$\hat{D} = \sum (g_i f_i + p_i) = NH^{1/N} + P$$

Optimal Number of Stages

For a given load,
and given input capacitance of the first gate
Find optimal number of stages and optimal sizing


$$D = NH^{1/N} + Np_{inv}$$

$$\frac{\partial D}{\partial N} = -H^{1/N} \ln(H^{1/N}) + H^{1/N} + p_{inv} = 0$$

Substitute 'best stage effort' $h = H^{1/\hat{N}}$

Example: Optimize Path

a, b, c: gate sizes t.b.d.

 

Effective fanout, $F = 5$

$$G = \prod g_i = 25/9$$

$$H = GFB = 125/9 = 13.9$$

$$h = H^{1/4} = 1.93$$

$$a = 1.93$$

$$b = ha/g_2 = 2.23$$

$$c = hb/g_3 = 5g_4/f = 2.59$$

Ratioed logic


Pass transistor logic

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

47

Pseudo NMOS Ratioed Logic

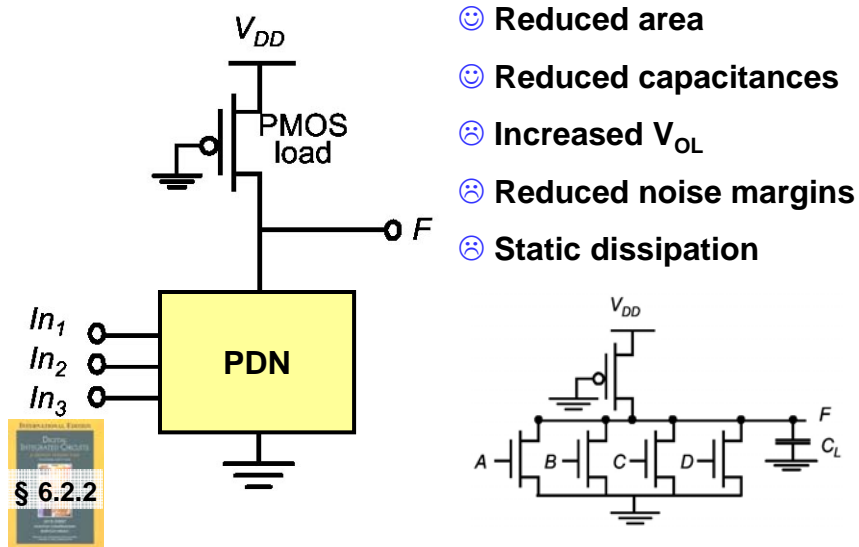

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

48

Ratioed Logic V_{OL} Computation

I_{Dn} (linear) = I_{Dp} (saturation)

Exercise: verify these assumptions/steps

$$k_n \left((V_{DD} - V_{Tn}) V_{OL} - \frac{V_{OL}^2}{2} \right) = k_p \left((-V_{DD} - V_{Tp}) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Ignore quadratic terms (they are relatively small)

$$k_n (V_{DD} - V_{Tn}) V_{OL} \approx k_p (-V_{DD} - V_{Tp}) V_{DSAT}$$


Ignore, because approximately equal

$$V_{OL} \approx \frac{k_p}{k_n} |V_{DSAT}| \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSAT}|$$

Pass-transistor and Pass-gate circuits

Pass Transistor Logic

 - Save area, capacitances
- Need complementary inputs (extra inverters)



But remember:

NMOS vs. PMOS, pull-down vs. pull-up

pull-up

pull-up

pull-down

pull-down

- PMOS is better pull-up
- NMOS is better pull-down

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational 08-May-06 5 combinational 12


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

51

Pass Transistor Logic

- Save **area, capacitances**
- Need complementary inputs (might mean extra inverters)
- Reduced V_{OH} , **noise margins**
- $$V_{OH} = V_{DD} - (V_{Tno} + \gamma((\sqrt{|2\phi_f| + V_{OH}}) - \sqrt{|2\phi_f|}))$$
- **Static dissipation** in subsequent static inverter/buffer
- Disadvantages (and advantages) may be reduced by **complementary pass gates** (NMOS + PMOS parallel)

 

Exercise: Why is there static dissipation in next conventional gate?


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

52

Pass Gates

 - Remedy: use an N-MOS and a P-MOS in parallel



- Pass gates **eliminate** some of the **disadvantages** of simple pass-transistors
- But also some of the **advantages**
- Design remains a **trade-off!**

Pass-gate a.k.a. Transmission-gate


TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

53

 Exercise

- Discuss what happens when you connect the output of a single pass-transistor (not a pass-gate) to the input of another pass-transistor stage (i.e. the gate of another pass-transistor). Why should you never use such a circuit?




TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008


54

Pass Transistor Logic

 - Most typical use: for multiplexing, or path selecting
- Assume in circuit below it is required to either connect A or B to Y, under control by S
- $Y = AS + BS'$ (S' is easier notation for $S\text{-bar} = S\text{-inverse} = \overline{S}$)
- $Y = ((AS)' (BS)')'$ allows realization with 3 NAND-2 and 1 INV: 14 transistors
- Pass gate needs only 6 (or 8) transistors (see also Katz, section 4.2)



 TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational



3/19/2008

55

Summary

- Conventional Static CMOS basic principles
- Complementary static CMOS
 - Complex Logic Gates
 - VTC, Delay and Sizing
- Ratioed logic
- Pass transistor logic

TUD/EE ET4293 Dig. VLSI 0708 - © NvdM - 08 Combinational

3/19/2008

56