

Module 1: Devices
Diodes, MOS transistors, models

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 1

Goal of this chapter

- Present intuitive understanding of device operation
- Introduction of basic device equations
- Introduction of models for manual analysis
- Introduction of models for SPICE simulation
- Analysis of secondary and deep-sub-micron effects
- Future trends

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 2

Outline

- Semiconductor Physics
- The diode
 - Depletion, I-V relations, capacitance,
- The MOS transistor
 - First glance, threshold, I-V relations, models
 - Dynamic behavior (capacitances), resistances,
- Process variations

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 3

Course Material for Devices

Chapter 3
P = primair, I = Illustratie, O = overslaan

C	3.1	Introduction	74
P	3.2-3.2.1	A first glance at the diode	74 – 77
P	3.2.2	Static Behavior	77 – 80
O	3.2.3	Dynamic, or Transient, Behavior	80 – 83 (1)
O	3.2.4	Secondary Effects	84 – 85
O	3.2.5	Spice Diode Model	85 – 87
P	3.3 – 3.3.2	The MOS(FET) Transistor	87 – 99
O		Subthreshold Conduction	99 – 101
P		Models for Manual Analysis	101 – 106
O	3.3.2	Dynamic Behavior, etc.	106 – 113 (1)
P		Junction Capacitances	110 – 111
O	3.3.3	Some Secondary Effects	114 – 117
O	3.3.4	Spice Model for the MOS Transistor	117 – 120
O	3.4	A word on process variations	120 – 122
I	3.5	Perspective: Technology Scaling	122 – 128
P	3.6	Summary	128 – 129

(1) Vervangend studiemateriaal voor dynamisch gedrag in syllabus

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 4

Modeling

- An **abstraction** of (the properties) of something to help **understanding** and **predicting** its behavior
- **Domain Specific**: weather, climate, economy, stock market, ...
- Different models for something to **answer different questions**
- **Black-Box** modeling vs. **Physically Based**
- After Einstein: **a model should be as simple as possible, but not simpler**

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 5

Semiconductor Physics

- All electrical behavior is determined by underlying physics
- This course is not about the physics
- But some small amount of background information helps built intuition
- Intuition is what an engineer/designer needs most

TU/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 6

Periodic System

Legend

- Li Solid
- Cs Liquid
- Ar Gas
- Sb Synthetic
- Alkali metals
- Alkali earth metals
- Transition metals
- Rare earth metals
- Other metals
- Noble gases
- Halogens
- Other nonmetals

<http://www.chemcool.com/>

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 7

Periodic System

B	C	N	O	Name	Symbol	#	Valence
Al	Si	P	S	Silicon	Si	14	4
Ga	Ge	As	Se	Boron	B	5	3
In	Sn	Sb	Te	Phosphor	P	15	5
Tl	Pb	Bi	Po	Arsenic	As	33	5
				Germanium	Ge	32	4

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 8

Semiconductor Physics

See also Tipler (BKV) 38.5

■ Intrinsic Si
■ Ideal crystal structure
■ Valence 4
■ almost no free carriers
■ almost no conduction

$[n] = [p] = n_i = 1,5 \cdot 10^{10} / cm^3$
at 300 K for silicon

■ doping with valence 5 atoms (Phosphor, Arsenic) introduces "loose electrons"
■ electron donor
■ conductivity depends on doping level

$n, p = n_i^2$ (in equilibrium)

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 9

Semiconductor Physics

■ doping with valence 5 atoms (Phosphor, Arsenic) introduces "loose electrons"
■ electron donor
■ conductivity depends on doping level

■ doping with valence 3 atoms (Boron) introduces "loose holes"
■ electron acceptors
■ hole conductivity lower than electron conductivity

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 10

Semiconductor Physics

Si in equilibrium : $n, p = n_i^2 = 2,25 \times 10^{20}$ at 300K
Intrinsic Si : $n = p = n_i$

<p style="text-align: center;">$N_D \gg N_A$</p> <p>Electron donors: As, P n-type Si $n \approx N_D, p = n_i^2 / n$ Electrons: majority carriers Holes: minority carriers Resistive material Conductivity depends on N_D</p>	<p style="text-align: center;">$N_A \gg N_D$</p> <p>Electron acceptors: B p-type Si $p \approx N_A, n = n_i^2 / p$ Holes: majority carriers Electrons: minority carriers Hole conductivity lower than electron conductivity</p>
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 11

The diode

■ Depletion, I-V relations, capacitance,

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 12

The diode: non-linear resistance

$I = \frac{V}{R}$

$R = \cotan(\alpha)$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 13

The Diode

See also Tipler (BKV) 38.6

Cross-section of pn-junction in an IC process

One-dimensional representation

Anode

Cathode

Diode symbol

Diode is abundant as MOS source/drain

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 14

Ideal Diode, Abrupt pn junction Intuitive Description

Join n-Si with p-Si

Concentration gradient of free carriers

Diffusion current

Space charge (depletion) region

Electric field

Drift current opposite to diffusion

equilibrium

Electron diffusion, hole diffusion, Hole drift, Electron drift

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 15

Depletion Region

(a) Current flow.

(b) Charge density.

(c) Electric field.

(d) Electrostatic potential.

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 16

Conduction

Typical N_A, N_D : $10^{15} \dots 10^{17}/\text{cm}^3$, ϕ_0 around 0.6 V

Built-in Potential $\phi_0 = \phi_T \ln \left[\frac{N_A N_D}{n_i^2} \right]$

Thermal voltage $\phi_T = \frac{kT}{q} = 26\text{mV at } 300\text{K}$

By applying an external voltage, width of depletion region can be changed

- Forward: becomes smaller and smaller, finally conduction
- Reverse: becomes wider and wider => no conduction

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 17

Diode Current

$I_D = I_S (e^{V_D/\phi_T} - 1)$

- I_S : Saturation current
- Proportional to diode area
- Depends on doping levels, and widths of neutral regions
- Usually determined empirically

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 18

Models for Manual Analysis

$I_D = I_S \left(e^{\frac{V_D}{\phi_T}} - 1 \right)$

(a) Ideal diode model

(b) First-order diode model

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 19

Diode Model Example

Determine I_D and V_D

$I_D = I_S (e^{V_D/\phi_T} - 1)$ (diode model)

$V_D = \phi_T (1 + \ln(I_D/I_S))$

$V_D = V_s - R_s I_D$ (Kirchof)

$V_D = V_s - R_s I_S (e^{V_D/\phi_T} - 1)$ ☹️

Iteration

start: $V_D = 1.0V$

$\Rightarrow I_D = (V_s - V_D)/R_s = 0.600 \text{ mA}$

$\Rightarrow V_D = \phi_T (1 + \ln(I_D/I_S)) = 0.663 \text{ V}$

$\Rightarrow I_D = 0.937 \text{ mA}$

$\Rightarrow V_D = 0.674 \text{ V}$

$\Rightarrow I_D = 0.926 \text{ mA}$

$\Rightarrow V_D = 0.674 \text{ V}$ 😊

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 20

Diode Model Example

$I_s = 0.5e^{-16} \text{ A}$

$kT/q = 25 \text{ mV}$

$V_s = 1.6 \text{ V}$

$R_s = 1 \text{ k}\Omega$

First order solution

$V_D = 0.6 \text{ V} \Rightarrow I_D = 1 \text{ mA}$ error = 8 %

Now, take $V_s = 10.6 \text{ V}$ $R_s = 10 \text{ K}\Omega$

The error will be

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 21

Capacitance

$Q = CV$

$C = \tan \alpha$

$C = \epsilon \frac{A}{t}$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 22

Relevance of Capacitance

- Capacitance: amount of stored charge depends on applied voltage
- Changing voltages (switching!) implies change of charge.
- Change of stored charge requires current
- Amount of current is limited
- (Dis)Charging takes time
- This is the main reason for 'limited' speed of IC's

- Speeding up requires improving ratio of current to amount of charge needed -> miniaturization helps!

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 23

Linearized Large-Signal Diode Capacitances


Summary:

- Diode capacitances highly non-linear
- Difficult with manual calculation
- We are ultimately interested in amount of charge being stored on (or removed from) capacitor
 - Since it takes time for this to happen, this determines the final switching speed of the circuit: more charge means more time!
- Linear capacitance: $\Delta Q = C\Delta V$: easy to work with
- Small-signal capacitance: $dQ = C_d V$: for analog appl.
- Non-linear capacitance: $\Delta Q = f(V_{low}, V_{high})$

Work with C_{eq} for standardized voltage swings

See the syllabus!

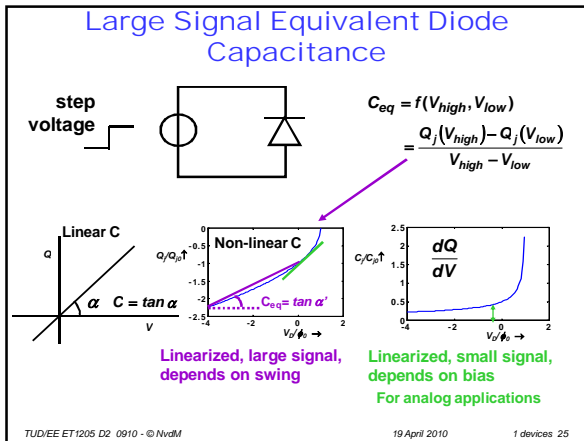TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 24



The MOS Transistor




- First glance, threshold, I-V relations, models
- Dynamic behavior (capacitances), resistances, more Second-Order effects, models

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 26

The MOS Field Effect Transistor – compared to Storey (Storey § 17.3-17.5)

- MOSFET transistor is not a JFET
- Other operating regions compared to saturation region (linear, velocity saturation) also important
- Include more effects (channel length modulation)
- Short-channel devices
 - bad for some analog circuits,
 - good for (most) digital circuits
- We will develop understanding of basic device equations

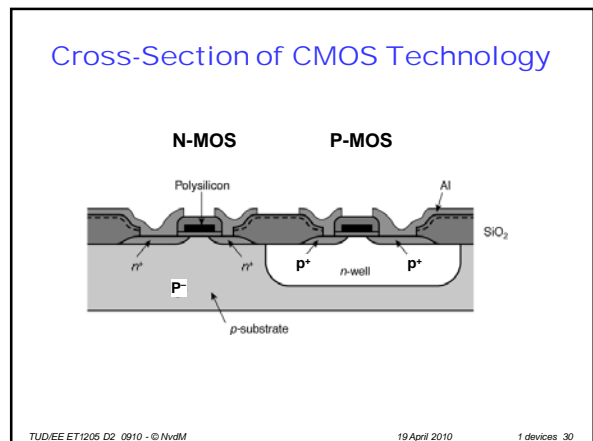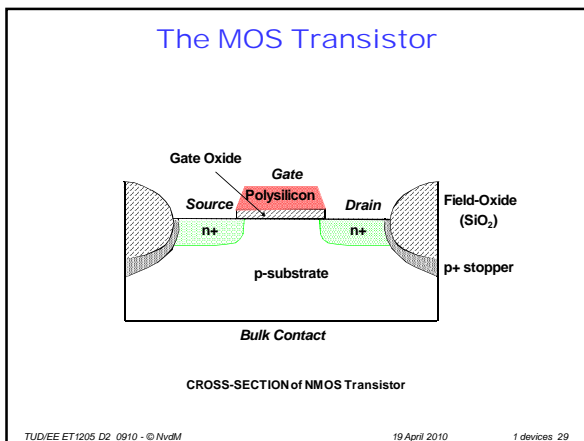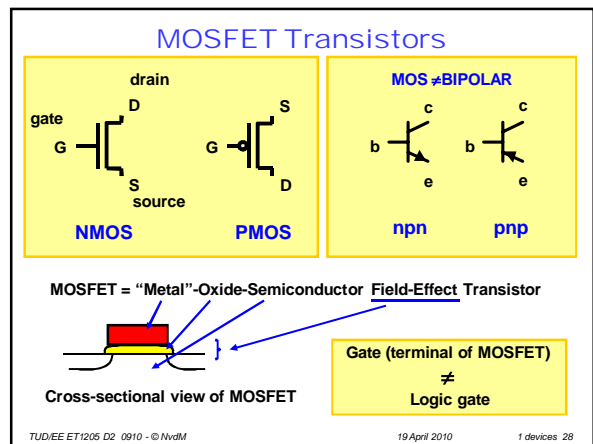TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 27



MOS Transistors

3-terminal model
bulk assumed to be connected to appropriate supply

4-terminal model
B = bulk (substrate)

NMOS **PMOS**

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 31

MOS Transistor Switch Level Models

Position of switch depends on gate voltage

V_G	NMOS	PMOS
hi	closed	open
lo	open	closed

Simplest possible useful model

- Connection between source and drain depends on gate voltage, current can flow from **source to drain and vice versa** if closed
- No **static** current flows into gate terminal

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 32

Mos Switch Model (2)

Position of switch depends on gate voltage

V_G	NMOS	PMOS
hi	closed	open
lo	open	closed

NMOS
A = 0: (a) Open, $y = ?$
A = 1: (b) Closed, $y = x$

PMOS
A = 1: (a) Open, $y = ?$
A = 0: (b) Closed, $y = x$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 33

CMOS Inverter Operation Principle

inverter

equiv. ckt. with input 1

equiv. ckt. with input 0

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 34

From Logic to Voltages

(a) Power supply connection

(b) Logic definitions

Ideal logic 0 corresponds to $V_x = 0V$
Ideal logic 1 corresponds to $V_x = V_{DD}$

Not all actual voltages in circuit necessarily correspond to ideal logic levels, see figure (b) above

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 35

From Logic to Voltages

Logic view

Voltage view

Note:

- GND = GROUND = 0V
- Sometimes also called V_{SS}
- V_{DD} is highest voltage level in circuit
- V_{DD} value depends on technology, has been **reduced** from 5V to 1V and lower over the years
- All voltages V_x in ckt: $0 \leq V_x \leq V_{DD}$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 36

Source and Drain Terminals

	NMOS	PMOS
Source	Lowest potential	Highest potential
Drain	Highest potential	Lowest potential

Note 1: Polarities of PMOS voltage reversed when compared to NMOS
 Note 2: MOS transistor is **completely symmetrical!** Can interchange source and drain, without any effect. Source/drain is only a **naming convention**.

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 37

nFET Threshold Voltage (drempelspanning)

(a) Gate-source voltage (b) Logic translation

nFET is off when $V_{GSn} \leq V_{Th}$
 nFET is on when $V_{GSn} > V_{Th}$

$V_{Th} \sim 0.5 \dots 0.7V$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 38

pFET Threshold Voltage

nFET is off when $V_{GSn} \leq V_{Th}$
 nFET is on when $V_{GSn} > V_{Th}$

pFET and nFET behave complementary

Equivalent conditions

pFET is off when $V_{GSp} \geq V_{Tp}$
 pFET is on when $V_{GSp} < V_{Tp}$

pFET is off when $-V_{GSp} \leq -V_{Tp}$
 pFET is on when $-V_{GSp} > -V_{Tp}$

pFET is off when $|V_{GSp}| \leq |V_{Tp}|$
 pFET is on when $|V_{GSp}| > |V_{Tp}|$

$V_{Tp} \sim -0.5 \dots -0.7V$ (negative!)
 Often most useful

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 39

Excercise

transistor on the left using
 nFET is off when $V_{GSn} \leq V_{Th}$
 nFET is on when $V_{GSn} > V_{Th}$
 corresponds to diagram on right

Draw same diagram for PMOS using
 pFET is off when $-V_{GSp} \leq -V_{Tp}$
 pFET is on when $-V_{GSp} > -V_{Tp}$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 40

MOS Transistor Treshold Voltage

Treshold voltage V_T : point at which transistor turns on

Position of switch depends on gate voltage (relative to source)

V_{GS}	NMOS	PMOS
$V_{GS} > V_T$	closed	open
$V_{GS} < V_T$	open	closed


TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 41

Is this all there is?

- You don't believe that (CMOS) life can be so simple, do you?
- Think of some of the things that you would expect to be non-idealities of CMOS as a switch
- Discuss with your neighbor
- Share with us
- Since we want to design CMOS circuits, we need a deeper understanding of CMOS circuits
- Next slide shows where we are going

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 42

MOS Models for Manual Analysis

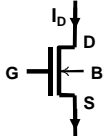

determined by circuit

 V_{DS}, V_{GS}, V_{SB}

determined by technology

 $k, \lambda, V_{DSAT}, V_{T0}, \gamma, \phi_F$

MOS model for manual analysis

$$I_D = k(V_{GT} V_{MIN} - 0.5V_{MIN}^2)(1 + \lambda V_{DS}) \quad \text{for } V_{GT} \geq 0$$



$$= 0 \quad \text{for } V_{GT} \leq 0$$

$$V_{MIN} = \text{MIN}(V_{DS}, V_{GT}, V_{DSAT})$$

$$V_{GT} = V_{GS} - V_T, \quad V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 43


nMOS Transistor Operation

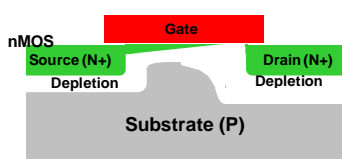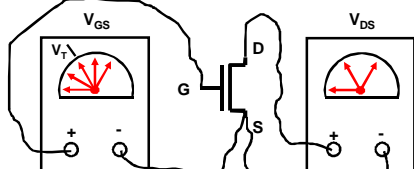TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 44

MOSFET gate as capacitor

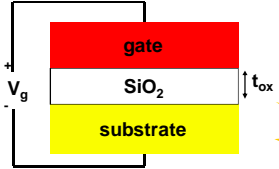- Gate capacitance helps determine charge in channel which forms **inversion region**.
- Basic structure of gate is **parallel-plate capacitor**:



$$C_{ox} = \epsilon_{ox} / t_{ox}$$

$$\epsilon_{ox} = \epsilon_0 \epsilon_r$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

Note: [F] vs. [F/m²]

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 45

$I_D(V_{GS}, V_{DS}, V_{BS})$

MOS model for manual analysis

$$I_D = k(V_{GT} V_{MIN} - 0.5V_{MIN}^2)(1 + \lambda V_{DS}) \quad \text{for } V_{GT} \geq 0$$

$$= 0 \quad \text{for } V_{GT} \leq 0$$


$$V_{MIN} = \text{MIN}(V_{DS}, V_{GT}, V_{DSAT})$$

- Different operation regions
- Different behavior for each region:
 - off
 - resistive
 - saturation
 - velocity saturation

← NEXT

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 46

Current-Voltage Relations

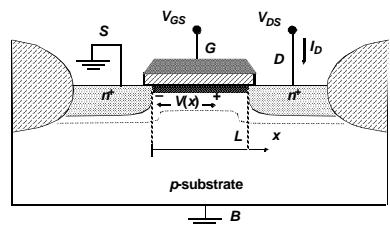

MOS transistor and its bias conditions

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 47

I-V In Resistive Region

$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$


$Q_i(x) = -C_{ox}[V_{GS} - V(x) - V_T]$ **Inversion Charge**

$I_D = -\mu_n \frac{dV}{dx} Q_i(x) W$ **I_D Drain Current**

$v_n = -\mu_n E(x) = \mu_n \frac{dV}{dx}$ **μ_n mobility (n-Si)**

$I_D L = \mu_n C_{ox} W \left[(V_{GS} - V_T) V - \frac{1}{2} V^2 \right]_0^{V_{DS}}$

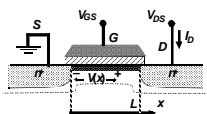$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$



TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 48

Process Gain and Device Gain

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$k'_n = \mu_n C_{ox} = \mu_n \frac{\epsilon_{ox}}{t_{ox}} \quad \text{Process transconductance parameter}$$

$$k = k'_n \frac{W}{L} \quad \text{Gain factor of device}$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad \text{(resistive regime)}$$


Note 1: we use k , many others β , but $k = \beta$

Note 2: resistive regime a.k.a. triode regime

Storey uses $K = \frac{1}{2} k$
Storey: Ohmic region

I-V Relation

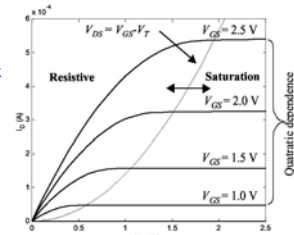
This and similar graphs to follow are from the book



$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad \text{(resistive regime)}$$

This formula **only valid in resistive regime**. This corresponds to the region to the left of the $V_{DS} = V_{GS} - V_T$ curve. There is another regime called 'saturation'. See following slides.

I-V Relation

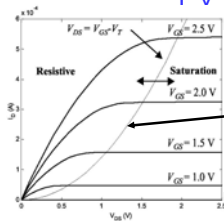

This curve is where I_D curves begin to run flat: I_D does not anymore depend on V_{DS}


$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

The curve is given by

$$\frac{dI_D}{dV_{DS}} = k \left[(V_{GS} - V_T) - V_{DS} \right] = 0 \Rightarrow V_{DS} = V_{GS} - V_T$$

The value $V_{DS} = V_{GS} - V_T$ is special: it is the boundary between resistive regime and saturation regime (pinch-off)

Transistor in Saturation

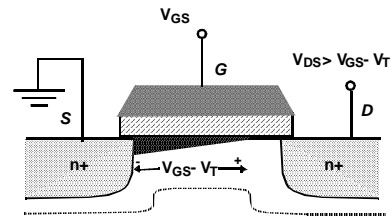

I-V in saturation

$$V_{DS} < V_{GS} - V_T$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


Saturation: $V_{DS} > V_{GS} - V_T$

Current does not increase when $V_{DS} > V_{GS} - V_T$

$$I_{DSAT} = I_D \Big|_{V_{DS} = V_{GS} - V_T} \quad \text{Saturation current}$$

$$I_{DSAT} = k \left[(V_{GS} - V_T)(V_{GS} - V_T) - \frac{1}{2} (V_{GS} - V_T)^2 \right] = \frac{1}{2} k (V_{GS} - V_T)^2$$


I-V Relation

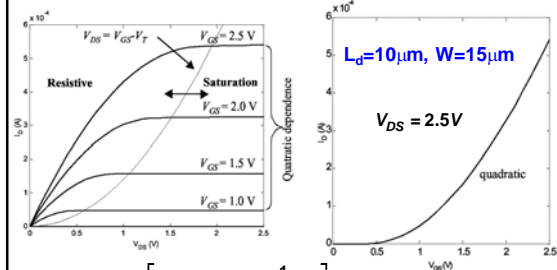

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad \text{(resistive regime)}$$

$$= \frac{1}{2} k (V_{GS} - V_T)^2 \quad \text{(saturation)}$$

Output Impedance

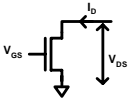

Definition: $Z_{out} = \frac{dV_{ds}}{dI_d}$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2$$


What is the output impedance?

Is this plausible?

What is happening?

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 55

Channel Length Modulation

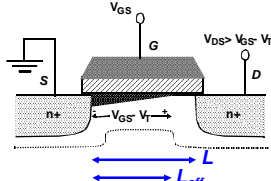

Empirical Model for Effective Channel Length

$$L_{eff} = \frac{L}{1 + \lambda V_{DS}}$$

$$I_{DSAT} = \frac{1}{2} k_n \frac{W}{L_{eff}} (V_{GS} - V_T)^2$$

$$= \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$= \frac{1}{2} k (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$


TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 56

Velocity Saturation (1)

1. Still model not complete: need to include effects of limited carrier velocity

2. Carrier velocity (ideal model):
Linear with field
 $v_n = -\mu_n \xi(x) = \mu_n \frac{dV}{dx}$

3. Reality

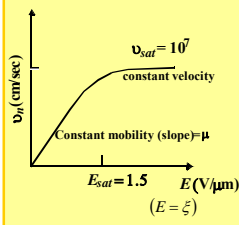

4. Simple v_{sat} Model:

$$v_n = \mu_n \xi \quad \text{for } \xi \leq \xi_c$$

$$= \mu_n \xi_c = v_{sat} \quad \text{for } \xi \geq \xi_c$$

ξ_c **Critical Field**
 v_{sat} **Saturation Velocity**

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 57

Velocity Saturation (2)

Onset of velocity saturation can be translated into a critical voltage $V_{DS} = V_{DSAT}$. This value depends on L.

Velocity saturation parameters

$$V_{DSAT} = L \xi_c = \frac{L v_{sat}}{\mu_n}$$

voltage velocity

L	V _{DSAT}
2	3
1	1.5
0.25	0.375
0.18	0.27
...	...

First order, empirical model


$$I_{DSAT} = I_D(V_{DS} = V_{DSAT})$$

$$= k \left[(V_{GS} - V_T) V_{DSAT} - \frac{1}{2} V_{DSAT}^2 \right] \quad \text{Velocity Saturation}$$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 58


I_D as a function of V_{DS}

L_d = 10 μm

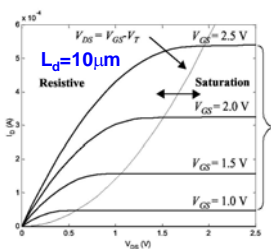

Resistive Saturation

L_d = 0.25 μm

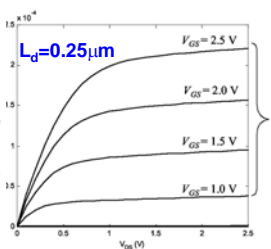


Quadratic dependence Linear dependence

W = 1.5L

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 59


I_D as a function of V_{GS}

L_d = 10 μm

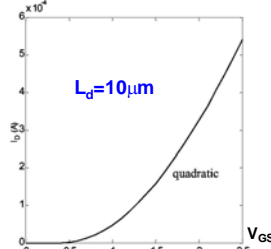

quadratic

L_d = 0.25 μm

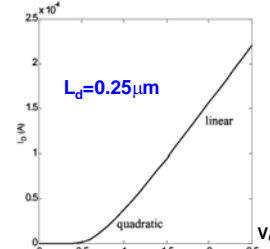

quadratic linear

Long channel device w/o velocity saturation

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2$$

Short channel device with velocity saturation

$$I_D = k \left[(V_{GS} - V_T) V_{DSAT} - 0.5 V_{DSAT}^2 \right]$$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 60

Overview

$$I_D = \begin{cases} k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & \text{resistive regime} \\ & \text{base equation} \\ \frac{1}{2} k (V_{GS} - V_T)^2 & \text{when } V_{DS} > V_{GS} - V_T: \text{ saturation} \\ & \text{replace } V_{DS} \text{ by } V_{GS} - V_T \text{ in base equation} \\ k \left[(V_{GS} - V_T) V_{DSAT} - \frac{1}{2} V_{DSAT}^2 \right] & \text{when } V_{DS} > V_{DSAT}: \text{ velocity saturation} \\ & \text{replace } V_{DS} \text{ by } V_{DSAT} \text{ in base equation} \end{cases}$$

$$I_D = I_D' (1 + \lambda V_{DS}) \quad \text{Channel Length Modulation}$$

Smallest of V_{DSr} , $V_{GS} - V_T$, V_{DSAT} determines operating region

→ Velocity saturation

→ Saturation

→ Resistive

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 61

Body Effect

- V_T is **not constant**
- Depends on V_S vs V_B
- Our wish is to understand & predict behavior of CMOS devices
- We will start with V_T

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 62

MOSFET gate as capacitor

- Gate capacitance helps determine charge in channel which forms **inversion region**.
- Basic structure of gate is **parallel-plate capacitor**:

$$C_{ox} = \epsilon_{ox} / t_{ox}$$

$$\epsilon_{ox} = \epsilon_0 \epsilon_r$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

$$\epsilon_r = 3.9 \text{ (SiO}_2\text{)}$$

Note: [F] vs. [F/m²]

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 63

The Threshold Voltage

$V_T = \phi_{ms} - 2\phi_F - \frac{Q_{ss}}{C_{ox}} - \frac{Q_f}{C_{ox}}$

Labels: Contact Potential, Fermi Potential, Depletion Layer Charge, Surface Charge, Implants

$Q_{ss} = \gamma (\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$

Labels: Body Effect Coefficient

Forget all this

$V_T = V_{T0} + \gamma (\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$
But be able to use this

and this

$$V_{T0} = \phi_{ms} - 2\phi_F - \frac{Q_{ss}}{C_{ox}} - \frac{Q_f}{C_{ox}}$$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 64

MOS Models for Manual Analysis

Region Specific Models

Channel length modulation added to resistive region, in order to enforce continuity

$$I_D = k(V_{GT} V_{DS} - 0.5 V_{DS}^2) \quad \text{Resistive region}$$

$$I_D = k(V_{GT} V_{GT} - 0.5 V_{GT}^2) \quad \text{Saturation}$$

$$I_D = k(V_{GT} V_{DSAT} - 0.5 V_{DSAT}^2) \quad \text{Velocity Saturation}$$

$$I_D = I_D' (1 + \lambda V_{DS}) \quad \text{Channel Length Modulation}$$

Comprehensive model

$$I_D = k(V_{GT} V_{MIN} - 0.5 V_{MIN}^2) (1 + \lambda V_{DS}) \quad \text{for } V_{GT} \geq 0$$

$$= 0 \quad \text{for } V_{GT} \leq 0$$

$V_{MIN} = \text{MIN}(V_{DS}, V_{GT}, V_{DSAT})$

$V_{GT} = V_{GS} - V_T, \quad V_T = V_{T0} + \gamma (\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 65

MOS Model Comparison



- Many more far more advanced models do exist (BSIM4 - 20k lines of C)
- Are only suited for computer simulation
- The SPICE simulator is the 'good old' workhorse of the industry
- Reliable, but low speed

Solid line: simple model

Dotted line: SPICE simulation

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 66



NMOS vs. PMOS

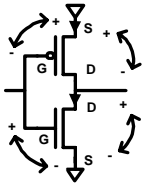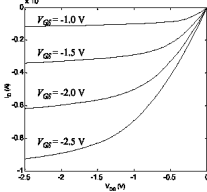- PMOS (V_{DS}, V_{GS}, I_D, V_T) < 0
- Can calculate as if NMOS using absolute values
- PMOS device not as strong as NMOS

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 67

NMOS vs. PMOS (2)

Zero-field mobility (bulk) **Velocity vs. Field**
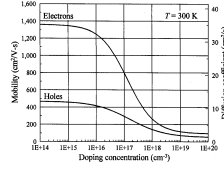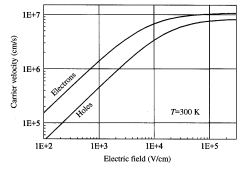
$$\mu_p < \mu_n \Rightarrow k'_p < k'_n$$

$$v_{sat_p} \approx v_{sat_n} \Rightarrow |V_{DSAT_p}| > |V_{DSAT_n}|$$

	V_{th} (V)	γ (V ^{0.5})	v_{sat} (V)	k' (A/V ²)	λ (V ⁻¹)
NMOS	0.43	0.4	0.63	115×10^{-4}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-4}	-0.1

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 68

Alternative Saturation Expression

- Saturation if $V_{DS} > V_{GS} - V_T$
- Show that $V_{DS} > V_{GS} - V_T \Leftrightarrow V_{GD} < V_T$
- Proof:
 - $V_{DS} > V_{GS} - V_T$
 - $\Leftrightarrow V_D - V_S > V_G - V_S - V_T$
 - $\Leftrightarrow V_D > V_G - V_T$
 - $\Leftrightarrow V_G - V_T < V_D$
 - $\Leftrightarrow V_G - V_D < V_T$
 - $\Leftrightarrow V_{GD} < V_T$

Physically this relates to 'amount of inversion' at drain side
If inversion at drain side disappears: pinch-off

- This is an alternative expression for the saturation region
- Can be handy

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 69

MOS Device Symmetry


- MOS transistors are **symmetrical**
- Strong inversion at source if $V_{GS} > V_T$
- Strong inversion at drain if $V_{GD} > V_T$ } **Independent!**
- You should check the I-V relations when interchanging drain and source
- Identification of source drain only by **convention**
- Determined by circuit-environment

	NMOS	PMOS	General
Source	V_{SS} -side	V_{DD} -side	Strongest inversion
Drain	V_{DD} -side	V_{SS} -side	Weakest inversion

V_{SS} : low supply voltage, V_{DD} = high supply voltage


TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 70

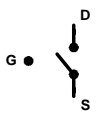Improved MOS Transistor Switch Level Model



Position of switch depends on gate to source voltage

V_{GS}	NMOS	PMOS
hi	closed	open
lo	open	closed


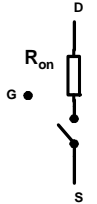


More detailed model may include R_{on}

- R_{on} is highly non-linear
- Make linear approximation R_{eq}
- Model with (linear) R_{eq} less detailed than previous equation based model, but often useful for first estimates of behavior

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 71

Switch Model R_{on}

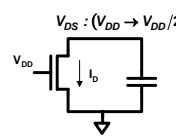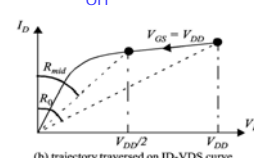(a) Schematic (b) trajectory traversed on ID-VDS curve.

$$R_{eq} = \frac{1}{2} \left[\frac{V_{DD}}{I_{DSAT} (1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} (1 + \lambda V_{DD}/2)} \right]$$

$$\frac{1}{1 + \lambda V_{DD}} \approx 1 - \lambda V_{DD} + O(\lambda^2 V_{DD}^2) \quad \text{2.3\% error with } \lambda = 0.06 \text{ V}^{-1}, V_{DD} = 2.5 \text{ V}$$

$$R_{eq} \approx \frac{1}{2} \frac{V_{DD}}{I_{DSAT}} \left[1 - \lambda V_{DD} + \frac{1}{2} (1 - \lambda V_{DD}/2) \right]$$

$$= \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left[1 - \frac{5}{6} \lambda V_{DD} \right]$$

Theory!

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 72

MOS Transistor Switch Level Model (Empirical).

Position of switch depends on gate to source voltage

V_{GS}	NMOS	PMOS
hi	closed	open
lo	open	closed

R_{eq} : Practice!

$R_{eq} \setminus V_{dd} (V)$	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 73

The MOS Transistor Summary

Cross-sectional View

Schematic symbols, very often w/o bulk contact

Switch closed if $V_{GS} > V_T$
Simplest possible equiv. ckt.

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 74

The MOS Transistor Summary ctd.

- Need to **analyze** speed, power, noise etc of MOS circuits
- Simple switch-level model **not sufficient**
- Study exact operation to derive **more precise IV relations**

$$I_D = k(V_{GT} V_{MIN} - 0.5 V_{MIN}^2)(1 + \lambda V_{DS}) \quad \text{for } V_{GT} \geq 0$$

$$= 0 \quad \text{for } V_{GT} \leq 0$$

$$V_{MIN} = \text{MIN}(V_{DS}, V_{GT}, V_{DSAT})$$

$$V_{GT} = V_{GS} - V_T, \quad V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 75

Summary

- Semiconductor Physics
- The diode
 - Depletion, I-V relations, capacitance, secondary effects, models
- The MOS transistor
 - First glance, threshold, I-V relations, models
 - Dynamic behavior (capacitances), resistances, more Second-Order effects, models

TUD/EE ET1205 D2 0910 - © NvdM 19 April 2010 1 devices 76